



---

# A-LEVEL PHYSICS 7408/3BE

Paper 3 Section B Electronics

---

Mark scheme

June 2020

---

Version: 1.0 Final



206A7408/3BE/MS

Mark schemes are prepared by the Lead Assessment Writer and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation events which all associates participate in and is the scheme which was used by them in this examination. The standardisation process ensures that the mark scheme covers the students' responses to questions and that every associate understands and applies it in the same correct way. As preparation for standardisation each associate analyses a number of students' scripts. Alternative answers not already covered by the mark scheme are discussed and legislated for. If, after the standardisation process, associates encounter unusual answers which have not been raised they are required to refer these to the Lead Examiner.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of students' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Further copies of this mark scheme are available from [aqa.org.uk](http://aqa.org.uk)

#### **Copyright information**

AQA retains the copyright on all its publications. However, registered schools/colleges for AQA are permitted to copy material from this booklet for their own internal use, with the following important exception: AQA cannot give permission to schools/colleges to photocopy any material that is acknowledged to a third party even for internal use within the centre.

Copyright © 2020 AQA and its licensors. All rights reserved.

---

## Physics – Mark scheme instructions to examiners

### 1. General

The mark scheme for each question shows:

- the marks available for each part of the question
- the total marks available for the question
- the typical answer or answers which are expected
- extra information to help the Examiner make his or her judgement and help to delineate what is acceptable or not worthy of credit or, in discursive answers, to give an overview of the area in which a mark or marks may be awarded.

The extra information is aligned to the appropriate answer in the left-hand part of the mark scheme and should only be applied to that item in the mark scheme.

At the beginning of a part of a question a reminder may be given, for example: where consequential marking needs to be considered in a calculation; or the answer may be on the diagram or at a different place on the script.

In general the right-hand side of the mark scheme is there to provide those extra details which confuse the main part of the mark scheme yet may be helpful in ensuring that marking is straightforward and consistent.

### 2. Emboldening

- 2.1** In a list of acceptable answers where more than one mark is available ‘any **two** from’ is used, with the number of marks emboldened. Each of the following bullet points is a potential mark.
- 2.2** A bold **and** is used to indicate that both parts of the answer are required to award the mark.
- 2.3** Alternative answers acceptable for a mark are indicated by the use of **or**. Different terms in the mark scheme are shown by a / ; eg allow smooth / free movement.

### 3. Marking points

#### 3.1 Marking of lists

This applies to questions requiring a set number of responses, but for which candidates have provided extra responses. The general principle to be followed in such a situation is that ‘right + wrong = wrong’.

Each error / contradiction negates each correct response. So, if the number of errors / contradictions equals or exceeds the number of marks available for the question, no marks can be awarded.

However, responses considered to be neutral (often prefaced by ‘Ignore’ in the mark scheme) are not penalised.

#### 3.2 Marking procedure for calculations

Full marks can usually be given for a correct numerical answer without working shown unless the question states ‘Show your working’. However, if a correct numerical answer can be evaluated from incorrect physics then working will be required. The mark scheme will indicate both this and the credit (if any) that can be allowed for the incorrect approach.

However, if the answer is incorrect, mark(s) can usually be gained by correct substitution / working and this is shown in the ‘extra information’ column or by each stage of a longer calculation.

A calculation must be followed through to answer in decimal form. An answer in surd form is never acceptable for the final (evaluation) mark in a calculation and will therefore generally be denied one mark.

### 3.3 Interpretation of ‘it’

Answers using the word ‘it’ should be given credit only if it is clear that the ‘it’ refers to the correct subject.

### 3.4 Errors carried forward, consequential marking and arithmetic errors

Allowances for errors carried forward are likely to be restricted to calculation questions and should be shown by the abbreviation ECF or *conseq* in the marking scheme.

An arithmetic error should be penalised for one mark only unless otherwise amplified in the marking scheme. Arithmetic errors may arise from a slip in a calculation or from an incorrect transfer of a numerical value from data given in a question.

### 3.5 Phonetic spelling

The phonetic spelling of correct scientific terminology should be credited (eg fizix) **unless** there is a possible confusion (eg defraction/refraction) with another technical term.

### 3.6 Brackets

(.....) are used to indicate information which is not essential for the mark to be awarded but is included to help the examiner identify the sense of the answer required.

### 3.7 Ignore / Insufficient / Do not allow

‘Ignore’ or ‘insufficient’ is used when the information given is irrelevant to the question or not enough to gain the marking point. Any further correct amplification could gain the marking point.

‘Do **not** allow’ means that this is a wrong answer which, even if the correct answer is given, will still mean that the mark is not awarded.

### 3.8 Significant figure penalties

Answers to questions in the practical sections (7407/2 – Section A and 7408/3A) should display an appropriate number of significant figures. For non-practical sections, an A-level paper may contain up to 2 marks (1 mark for AS) that are contingent on the candidate quoting the **final** answer in a calculation to a specified number of significant figures (sf). This will generally be assessed to be the number of sf of the datum with the least number of sf from which the answer is determined. The mark scheme will give the range of sf that are acceptable but this will normally be the sf of the datum (or this sf -1).

An answer in surd form cannot gain the sf mark. An incorrect calculation **following some working** can gain the sf mark. For a question beginning with the command word ‘Show that...’, the answer should be quoted to **one more** sf than the sf quoted in the question eg ‘Show that X is equal to about 2.1 cm’ – answer should be quoted to 3 sf. An answer to 1 sf will not normally be acceptable, unless the answer is

an integer eg a number of objects. In non-practical sections, the need for a consideration will be indicated in the question by the use of ‘Give your answer to an appropriate number of significant figures’.

### 3.9 Unit penalties

An A-level paper may contain up to 2 marks (1 mark for AS) that are contingent on the candidate quoting the correct unit for the answer to a calculation. The need for a unit to be quoted will be indicated in the question by the use of ‘State an appropriate SI unit for your answer’. Unit answers will be expected to appear in the most commonly agreed form for the calculation concerned; strings of fundamental (base) units would not. For example, 1 tesla and 1 Wb m<sup>-2</sup> would both be acceptable units for magnetic flux density but 1 kg m<sup>2</sup> s<sup>-2</sup> A<sup>-1</sup> would not.

### 3.10 Level of response marking instructions

Level of response mark schemes are broken down into three levels, each of which has a descriptor. The descriptor for the level shows the average performance for the level. There are two marks in each level.

Before you apply the mark scheme to a student’s answer read through the answer and annotate it (as instructed) to show the qualities that are being looked for. You can then apply the mark scheme.

#### Determining a level

Start at the lowest level of the mark scheme and use it as a ladder to see whether the answer meets the descriptor for that level. The descriptor for the level indicates the different qualities that might be seen in the student’s answer for that level. If it meets the lowest level then go to the next one and decide if it meets this level, and so on, until you have a match between the level descriptor and the answer. With practice and familiarity you will find that for better answers you will be able to quickly skip through the lower levels of the mark scheme.


When assigning a level you should look at the overall quality of the answer and not look to pick holes in small and specific parts of the answer where the student has not performed quite as well as the rest. If the answer covers different aspects of different levels of the mark scheme you should use a best fit approach for defining the level and then use the variability of the response to help decide the mark within the level. i.e. if the response is predominantly level 2 with a small amount of level 3 material it would be placed in level 2.

The exemplar materials used during standardisation will help you to determine the appropriate level. There will be an answer in the standardising materials which will correspond with each level of the mark scheme. This answer will have been awarded a mark by the Lead Examiner. You can compare the student’s answer with the example to determine if it is the same standard, better or worse than the example. You can then use this to allocate a mark for the answer based on the Lead Examiner’s mark on the example.


You may well need to read back through the answer as you apply the mark scheme to clarify points and assure yourself that the level and the mark are appropriate.

Indicative content in the mark scheme is provided as a guide for examiners. It is not intended to be exhaustive and you must credit other valid points. Students do not have to cover all of the points mentioned in the indicative content to reach the highest level of the mark scheme.

An answer which contains nothing of relevance to the question must be awarded no marks.

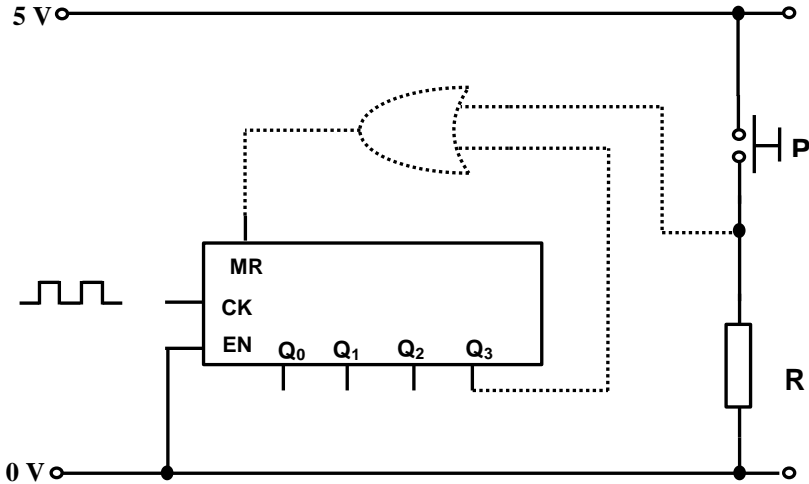Question	Answers	Additional comments/Guidelines	Mark	AO
01.1	 <p>Correct logic gate to MR ✓          Q<sub>3</sub> to logic gate input ✓          Midpoint of switch chain to logic gate input ✓</p> <p>OR</p> <p>Accept 2 diodes in correct position ✓✓          Correct orientation ✓</p>	<p>2 marks only for both resets in correct positions but no logic gate.</p> <p>1 mark only for any correct single reset circuit.</p>	3	AO3.2a AO3.2a AO3.2a
01.2	$(A \cdot C) \checkmark + (B \cdot \bar{C}) \checkmark$	<p>Second mark includes the (+)</p>	2	AO2.1h AO2.1h

		Also allow commutative equivalents such		
		as $(\mathbf{B} \cdot \overline{\mathbf{C}}) + (\mathbf{A} \cdot \mathbf{C})$		

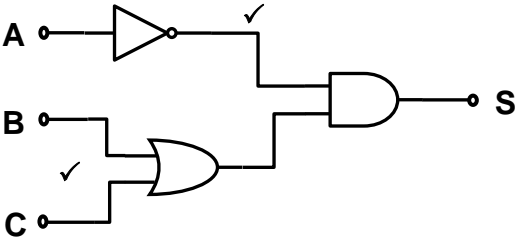Question	Answers								Additional comments/Guidelines	Mark	AO
01.3	Decimal number	C	B	A	D	E	F	W		1	AO2.1f
	0	0	0	0	1	0	0	0			
	1	0	0	1	1	0	0	0			
	2	0	1	0	1	0	1	1			
	3	0	1	1	1	0	1	1			
	4	1	0	0	0	0	0	0			
	5	1	0	1	0	1	0	1			
	6	1	1	0	0	0	0	0			
7	1	1	1	0	1	0	1				
01.4	numbers 2, 4 and 6 ✓								accept even numbers	1	AO2.1h
01.5									<p>NOT A into the AND gate ✓</p> <p>(B OR C) into the AND gate ✓</p> <p>Only 1 mark if AND gate is incorrect .....</p> <p>Do not accept use of NAND, NOR, EXOR / EXNOR gates to generate equivalent functions.</p>	2	AO2.1b AO2.1b
<b>Total</b>										<b>9</b>	



Question	Answers	Additional comments/Guidelines	Mark	AO
02.1	Numerical value for capacitor = 6.9 pF ✓	Substitution of values into formula alone – not sufficient for mark.	1	AO1.1b
02.2	Y and X most suitable / (W and Z out of range) ✓ Y better than X as value falls within centre of range. ✓	implied choice – 1 mark reason – 1 mark	2	AO3.1a AO3.1a
02.3	Evidence of reading at 0.7 V <sub>max</sub> (350 mV) ✓ Bandwidth 20 kHz ✓ Allow range (19–21 kHz)	1 mark only for: Evidence of reading at 0.5 V <sub>max</sub> (250 mV) Bandwidth 25 kHz ✓ Allow range (24–26 kHz)	2	AO2.1b AO2.1b
02.4	$Q = f_0 / f_B = 198 \text{ kHz} / 20 \text{ kHz} = 9.9$ ✓ <b>1 mark</b>	Allow ecf from 02.3	1	AO1.1b
02.5	<b>Either:</b> Listener hears overlapping stations - due to increase in bandwidth. ✓ <b>Or</b> Listener hears station more faintly - due to energy loss / wider energy distribution ✓	Accept S/N argument as weaker stations become more prominent and can be considered as noise.	1	AO1.1a
<b>Total</b>			<b>7</b>	

Question	Answers	Additional comments/Guidelines	Mark	AO
03.1	Audio range (bandwidth) is 20 kHz ✓  The sampling frequency should be at least <b>twice</b> the maximum frequency / bandwidth ✓	Reference to Nyquist theorem without reference to numerical data – 1 mark only	2	AO1.1a AO1.1b
03.2	$6.5536 \times 10^4$	Allow other correct numbers eg 65536	1	AO1.1b
03.3	For one channel: $44.1 \times 10^3 \times 16 \times 3.5 \times 60 = 148.175$ megabits. ✓  For Stereo: $(2 \times 148.175) \div 8 = 37.04$ megabytes ✓ (Accept 37 megabytes)	<b>Two</b> marks for 37 megabytes with no working shown.	2	AO2.1b AO2.1b
03.4	Lower quality music over telephone line due to: telephone call has lower bandwidth than original audio file ✓ loss of high and low frequencies from music ✓	<b>One</b> mark for general comment relating to ratio of bandwidths of the two systems where CD bandwidth has been taken to be in region of 15 kHz – 20 kHz	2	AO3.1b AO3.1b
<b>Total</b>			<b>7</b>	

Question	Answers	Additional comments/Guidelines	Mark	AO
04.1	comparator <input checked="" type="checkbox"/> differential amplifier <input type="checkbox"/> inverting amplifier <input type="checkbox"/> non-inverting amplifier <input type="checkbox"/>		1	AO1.1a
04.2	Photodiode current from graph = $80 \mu\text{A}$ ✓  Voltage across resistor $V_R$ $V_R = I \times R = 80 \times 10^{-6} \times 39 \times 10^3$ $V_R = 3.12 \text{ V}$ ✓  Voltage at non-inverting pin ( $V_+$ ) = $(5 - 3.12) = 1.88 \text{ V}$ ✓	Allow $\pm 5 \mu\text{A}$ in reading from the graph  Allow a $V_R = 2.93 \text{ V}$ to $3.32 \text{ V}$  Allow a $V_+$ value of $2.07 \text{ V}$ to $1.68 \text{ V}$	3	AO3.1a AO2.1d AO2.1d
04.3	Voltage at inverting pin ( $V_-$ ) is $2.2 \text{ V}$ ✓ $V_- > V_+$ so output is low / $0 \text{ V}$ so LED will light / on ✓	<b>First mark</b> is for correct value of ( $V_-$ )  <b>Second mark</b> is for correct application / conclusion using $V_+ = 1.9 \text{ V}$ together with their value for ( $V_-$ )	2	AO3.1a AO3.1a
<b>Total</b>			<b>6</b>	

Question	Answers	Additional comments/Guidelines				Mark	AO																	
05	<p>The mark scheme gives some guidance as to what statements are expected to be seen in a 1 or 2 mark (L1), 3 or 4 mark (L2) and 5 or 6 mark (L3) answer. Guidance provided in section 3.10 of the 'Mark Scheme Instructions' document should be used to assist in marking this question.</p> <table border="1" data-bbox="277 627 1079 1401"> <thead> <tr> <th data-bbox="277 627 416 660">Level</th> <th data-bbox="416 627 1079 660">Criteria</th> </tr> </thead> <tbody> <tr> <td data-bbox="277 660 416 906"> <b>L3</b> 6 marks                             </td> <td data-bbox="416 660 1079 906">                                 The candidate shows a good knowledge of the <b>three</b> general properties of copper wire and optic fibre. They use technical terms correctly, the answer has structure and clearly conveys the information required. They reach a conclusion based on the supporting evidence.                             </td> </tr> <tr> <td data-bbox="277 906 416 1152"> <b>L3</b> 5 marks                             </td> <td data-bbox="416 906 1079 1152">                                 The candidate shows a good knowledge of the <b>three</b> general properties of copper wire and optic fibre. However, there may be minor gaps in knowledge OR the style / structure may lead to a lack of clarity in some of the information being presented. There is a supported conclusion.                             </td> </tr> <tr> <td data-bbox="277 1152 416 1401"> <b>L2</b> 4 marks                             </td> <td data-bbox="416 1152 1079 1401">                                 The candidate shows a good understanding of <b>two</b> general properties of copper wire and optic fibre. Technical terms will be used correctly and the information will generally be presented in a structured and coherent manner. A conclusion will be drawn from the information presented.                             </td> </tr> </tbody> </table>	Level	Criteria	<b>L3</b> 6 marks	The candidate shows a good knowledge of the <b>three</b> general properties of copper wire and optic fibre. They use technical terms correctly, the answer has structure and clearly conveys the information required. They reach a conclusion based on the supporting evidence.	<b>L3</b> 5 marks	The candidate shows a good knowledge of the <b>three</b> general properties of copper wire and optic fibre. However, there may be minor gaps in knowledge OR the style / structure may lead to a lack of clarity in some of the information being presented. There is a supported conclusion.	<b>L2</b> 4 marks	The candidate shows a good understanding of <b>two</b> general properties of copper wire and optic fibre. Technical terms will be used correctly and the information will generally be presented in a structured and coherent manner. A conclusion will be drawn from the information presented.	<table border="1"> <thead> <tr> <th data-bbox="1093 284 1267 443">Physical</th> <th data-bbox="1267 284 1451 443">Corrosion</th> <th data-bbox="1451 284 1617 443">Copper</th> <th data-bbox="1617 284 1816 443">Optic fibre</th> </tr> </thead> <tbody> <tr> <td></td> <td></td> <td data-bbox="1451 443 1617 568">                     Will corrode unless well protected                 </td> <td data-bbox="1617 443 1816 568">                     Glass doesn't corrode                 </td> </tr> <tr> <td></td> <td data-bbox="1267 443 1451 568"> <b>Weight / connectivity</b> </td> <td data-bbox="1451 443 1617 568">                     Heavier, easier to join                 </td> <td data-bbox="1617 443 1816 568">                     Lightweight, more difficult to join sections                 </td> </tr> </tbody> </table>	Physical	Corrosion	Copper	Optic fibre			Will corrode unless well protected	Glass doesn't corrode		<b>Weight / connectivity</b>	Heavier, easier to join	Lightweight, more difficult to join sections	6	AO1.1a x5  AO3.1b x1
		Level	Criteria																					
		<b>L3</b> 6 marks	The candidate shows a good knowledge of the <b>three</b> general properties of copper wire and optic fibre. They use technical terms correctly, the answer has structure and clearly conveys the information required. They reach a conclusion based on the supporting evidence.																					
		<b>L3</b> 5 marks	The candidate shows a good knowledge of the <b>three</b> general properties of copper wire and optic fibre. However, there may be minor gaps in knowledge OR the style / structure may lead to a lack of clarity in some of the information being presented. There is a supported conclusion.																					
		<b>L2</b> 4 marks	The candidate shows a good understanding of <b>two</b> general properties of copper wire and optic fibre. Technical terms will be used correctly and the information will generally be presented in a structured and coherent manner. A conclusion will be drawn from the information presented.																					
Physical	Corrosion	Copper	Optic fibre																					
		Will corrode unless well protected	Glass doesn't corrode																					
	<b>Weight / connectivity</b>	Heavier, easier to join	Lightweight, more difficult to join sections																					
<table border="1"> <thead> <tr> <th data-bbox="1093 596 1267 756">External interference</th> <th data-bbox="1267 596 1451 756">Security</th> <th data-bbox="1451 596 1617 756">External access</th> <th data-bbox="1617 596 1816 756"></th> </tr> </thead> <tbody> <tr> <td></td> <td data-bbox="1267 756 1451 911">                     Can be tapped without breaking cable                 </td> <td data-bbox="1451 756 1617 911">                     Can pick up noise / cross talk                 </td> <td data-bbox="1617 756 1816 911">                     Cannot be tapped unless broken into  Immune from noise – can be used in noisy environments                 </td> </tr> </tbody> </table>	External interference	Security	External access			Can be tapped without breaking cable	Can pick up noise / cross talk	Cannot be tapped unless broken into  Immune from noise – can be used in noisy environments																
External interference	Security	External access																						
	Can be tapped without breaking cable	Can pick up noise / cross talk	Cannot be tapped unless broken into  Immune from noise – can be used in noisy environments																					
<table border="1"> <thead> <tr> <th data-bbox="1093 935 1267 1094">Signal-carrying properties</th> <th data-bbox="1267 935 1451 1094">Signal degradation / attenuation</th> <th data-bbox="1451 935 1617 1094">Bandwidth / info carrying capacity</th> <th data-bbox="1617 935 1816 1094"></th> </tr> </thead> <tbody> <tr> <td></td> <td data-bbox="1267 1094 1451 1430">                     High attenuation                 </td> <td data-bbox="1451 1094 1617 1430">                     Relatively low bandwidth / fewer channels                 </td> <td data-bbox="1617 1094 1816 1430">                     Low attenuation / Possible pulse smearing  Greater bandwidth / capacity / more channels / possibility of sending multiple types of signal eg data + talk                 </td> </tr> </tbody> </table>	Signal-carrying properties	Signal degradation / attenuation	Bandwidth / info carrying capacity			High attenuation	Relatively low bandwidth / fewer channels	Low attenuation / Possible pulse smearing  Greater bandwidth / capacity / more channels / possibility of sending multiple types of signal eg data + talk																
Signal-carrying properties	Signal degradation / attenuation	Bandwidth / info carrying capacity																						
	High attenuation	Relatively low bandwidth / fewer channels	Low attenuation / Possible pulse smearing  Greater bandwidth / capacity / more channels / possibility of sending multiple types of signal eg data + talk																					

Question	Answers		Additional comments/Guidelines	Mark	AO
05	<b>Level</b>	<b>Criteria</b>			
	<b>L2 3 marks</b>	The candidate shows a good knowledge of <b>two</b> general properties of copper wire and optic fibre. There may be minor gaps in knowledge / detail which may lead to a lack of clarity. There will be a conclusion which draws some support from the information presented.			
	<b>L1 2 marks</b>	The candidate shows some knowledge of <b>two</b> general properties of copper wire and optic fibre. There may be significant gaps in knowledge / detail which may lead to a lack of clarity. There may be no supported conclusion.			
	<b>L1 1 mark</b>	The candidate shows some understanding of <b>one</b> of the general properties of copper wire and optic fibre. Overall, this will be a limited answer with significant detail missing. There may be a lack of structure and clarity. There may be no supported conclusion.			
	<b>L1 0 marks</b>	The work contains no significant analysis of the question asked.			
<b>Total</b>				<b>6</b>	