

Surname	Centre Number	Candidate Number
Other Names		2



**GCE AS – NEW**

B490U10-1



S18-B490U10-1



**ELECTRONICS – AS component 1**  
**Principles of Electronics**

MONDAY, 21 MAY 2018 – MORNING

2 hours 30 minutes

For Examiner's use only		
Question	Maximum Mark	Mark Awarded
1.	5	
2.	8	
3.	15	
4.	9	
5.	10	
6.	16	
7.	10	
8.	5	
9.	17	
10.	13	
11.	12	
<b>Total</b>	<b>120</b>	

**ADDITIONAL MATERIALS**

In addition to this examination paper, you will require a calculator and a **Data Booklet**.

**INSTRUCTIONS TO CANDIDATES**

Use black ink or black ball-point pen.

Answer **all** questions.

Write your name, centre number and candidate number in the spaces at the top of this page.

Write your answers in the spaces provided in this booklet.

**INFORMATION FOR CANDIDATES**


The number of marks is given in brackets at the end of each question or part-question.

The assessment of the quality of extended response (QER) will take place in questions **5(a)** and **11(b)**.


Answer **all** questions.

Examiner  
only

 1. The symbol for the 2-input EXOR gate is shown below.



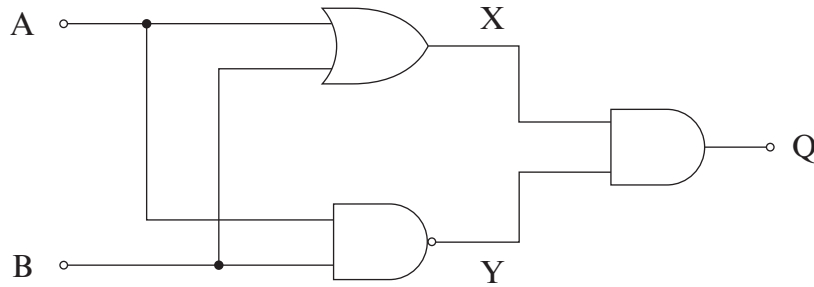
(a) An EXOR gate can be built from other logic gates. Complete the truth table to show that the following circuit produces the same output as an EXOR gate. [3]



B	A	X	Y	Q
0	0			
0	1			
1	0			
1	1			

(b) Multiplexers can be used in place of logic gates.

 (i) Show on the diagram how the output Q could be generated using a multiplexer. [1]



(ii) State **one** advantage of using a multiplexer for this purpose. [1]

.....  
 .....

2. (a) Simplify the following expressions. [2]

(i)  $\overline{B} \cdot 0$  .....

(ii)  $A \cdot B + \overline{B} =$  .....

(b) A logic system produced the following Karnaugh map.

		BA			
	DC	00	01	11	10
00		1	1	0	0
01		1	0	1	1
11		0	0	1	1
10		1	1	0	0

On the map show all the groups. Hence give the simplest Boolean expression for the output of this logic system. [3]

.....  
 .....

(c) Apply DeMorgan's theorem to the following expression **and** simplify the result. [3]

$$Q = \overline{\overline{A + B} + \overline{A}}$$

.....  
 .....

3. A design brief for an electronic safety warning system in a car uses the following information regarding the inputs and outputs of the system.

- sensor, A, outputs a logic 1 when the ignition key is turned.
- microswitch, B, on the seatbelt outputs a logic 1 when the belt is fastened.
- microswitch, C, on the door outputs a logic 1 if the door is opened.
- the buzzer sounds when Q is logic 1.

The truth table for the logic system is shown below.

Door switch C	Seatbelt switch B	Key sensor A	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

(a) (i) Use the truth table to write down the **unsimplified** (3 term) Boolean expression for output Q in terms of C, B and A. [1]

Q = .....

(ii) Simplify the expression using either a Karnaugh map or the rules of Boolean algebra. [3]

.....  
 .....  
 .....  
 .....  
 .....  
 .....

		B.A			
		00	01	11	10
C	0				
	1				

- (b) Complete the following diagram to show how the output **Q** can be generated using logic gates. [3]

A ○ ———

B ○ ———


C ○ ———

————— ○ **Q**

- (c) Redraw the system using NAND gates only. Cross out any redundant gates. [4]

(d) The system is replaced by a microcontroller. Part of the system is shown in the flow chart. Explain what is happening whilst the flow chart is run. [4]

Examiner only

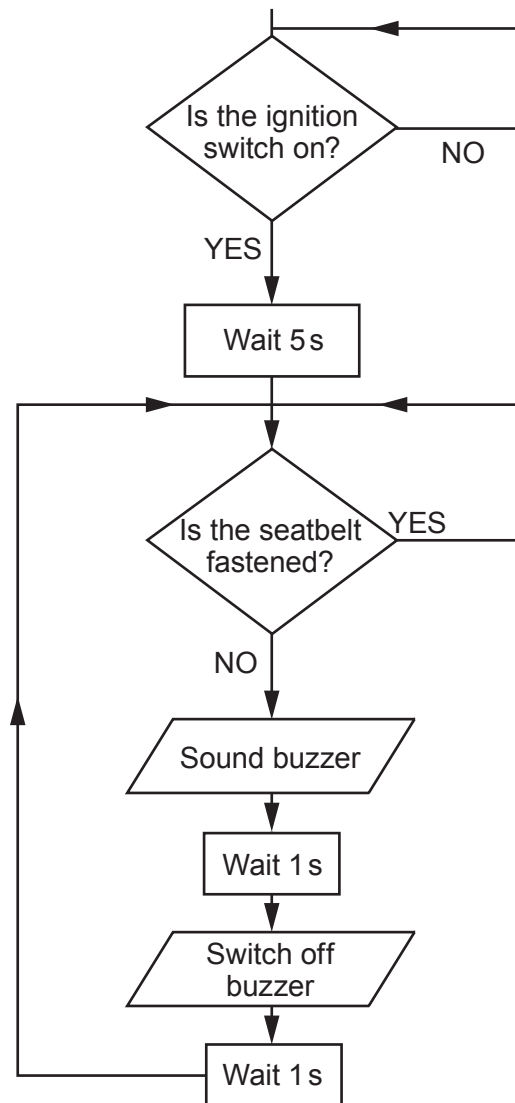

.....

.....

.....

.....

.....

.....

.....

.....

.....


.....

.....

.....

.....

 4. The following circuit is used as a voltage source.



(a) Thevenin's theorem is used to produce an equivalent circuit. Calculate the open circuit voltage  $V_{OC}$  and the equivalent resistance  $R_O$ . [4]

.....

.....

.....

.....

.....

.....

(b) (i) Draw the labelled equivalent circuit with two  $240\ \Omega$  resistors connected in parallel across the output terminals. [2]

(ii) Use the equivalent circuit to calculate the voltage drop across the output terminals. [3]

.....

.....


.....

.....

5. An electronic control system has the following circuit specification:

- a solenoid should operate when either a light beam is broken or a switch is pressed
- when the light beam is broken point A should be at logic 1
- when the switch SW1 is pressed point B should be at logic 1
- a diode is required to protect the transistor from back emf.

A design for the system is shown below.

 

(a) Evaluate the function of the design shown in the diagram against the circuit specification and suggest any improvements required to meet the specification fully. [6 QER]

.....

.....

.....

.....

B490U101  
09

(b) (i) The logic system output is 11.6V and the current through the solenoid is 200 mA when the transistor is **just saturated**. The transistor has a current gain,  $h_{FE}$ , of 80. Calculate the ideal value for base resistor,  $R_B$ . [3]

.....

.....

.....


.....

.....

(ii) Choose a suitable preferred value resistor from the E24 series. [1]


.....

 6. A student designs a control system to keep the temperature of a tropical fish tank at  $25^{\circ}\text{C}$ . The circuit diagram shows part of the control system.



$V_{\text{OUT}}$  saturates at  $12\text{V}$  and  $0\text{V}$ .

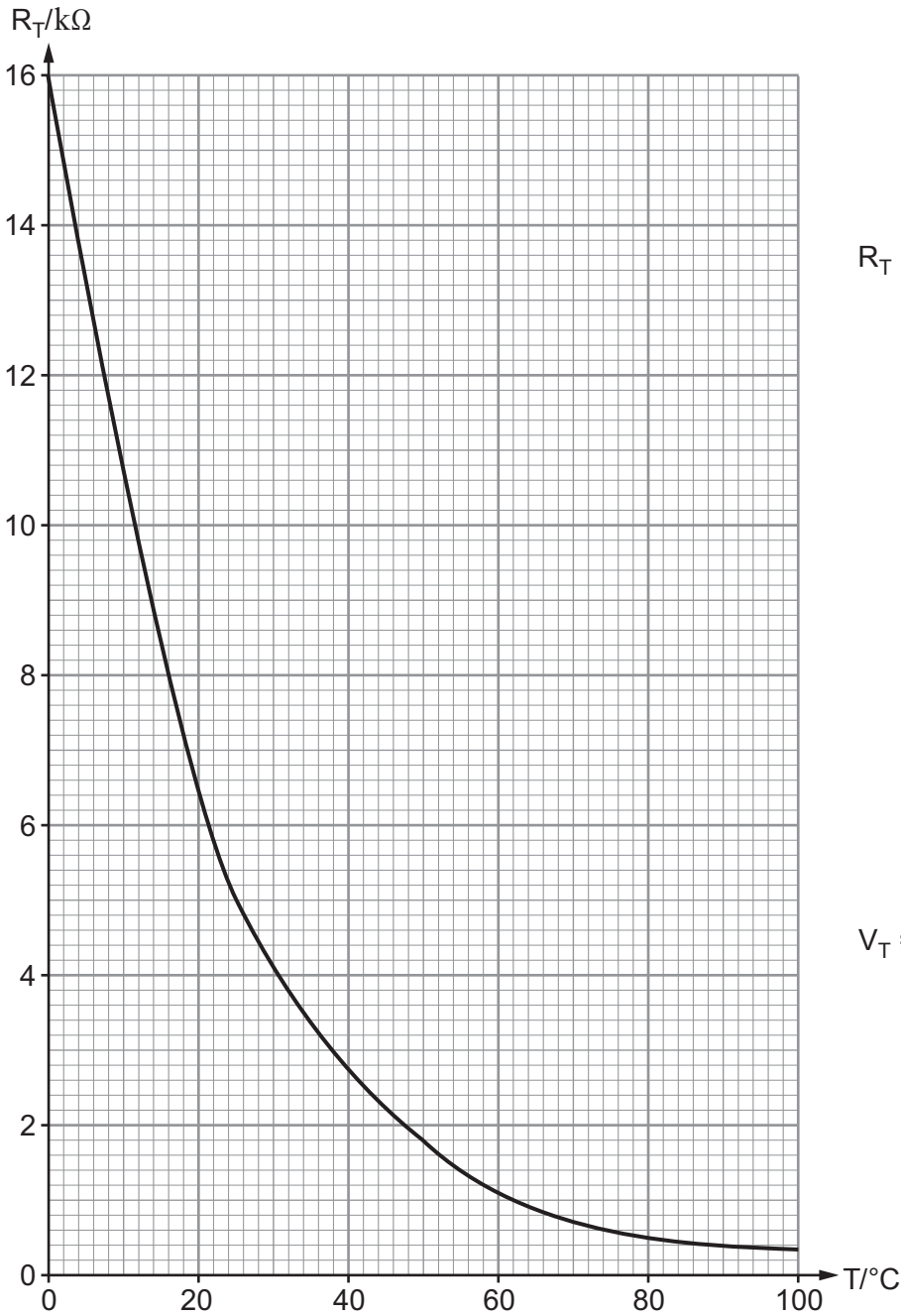- (a) (i) Use the resistance-temperature graph to determine the resistance of the thermistor ( $R_T$ ) at  $25^\circ\text{C}$  and hence calculate the value of  $V_T$  at this temperature. [3]



$R_T = \dots\dots\dots$

$V_T = \dots\dots\dots$

- (ii) Calculate the resistance of  $R_V$  that would cause the output voltage of the comparator to switch at just over  $25^\circ\text{C}$ . [2]

.....

.....

(b) The water is changed and is heated up from cold. With reference to  $V_T$  and  $V_X$  explain how  $V_{OUT}$  changes when the temperature increases from  $20^\circ\text{C}$  to over  $25^\circ\text{C}$ . [4]

.....

.....

.....

.....

.....

.....

(c) The student decides to use a MOSFET to operate the heater which is rated at 12V, 48W. Draw a suitable circuit below. [2]

12V ○—————

Output of  
comparator —○

0V ○—————

(d) The MOSFET has a maximum power dissipation of 60W and  $r_{DSon} = 0.08\Omega$ .

Calculate:

(i) the minimum value of  $g_m$  to allow the heater to operate at its rated current. [3]

.....

.....

.....

.....


(ii) the power dissipated in the MOSFET when the heater is operating at its rated current. [2]

.....

.....

.....

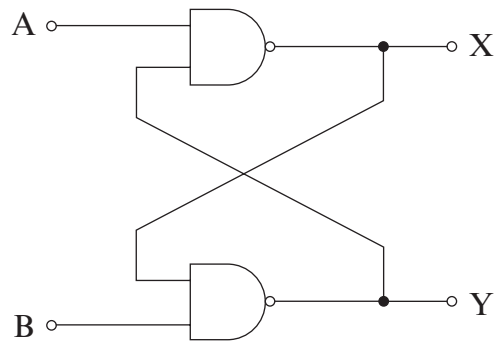
7. (a) The following circuit shows a NAND gate bistable.




Complete the truth table to show the sequence of outputs at X and Y, for the given sequence of inputs A and B. [3]

A	B	X	Y
1	1	0	1
0	1		
1	1		
1	0		
1	1		
0	0		

 - (b) The logic gates have a propagation delay of 10 ns. Explain what is meant by propagation delay. Then draw a transition gate in the space below constructed from NAND gates that produces the following pulse at its output when the input changes from logic 0 to logic 1. [4]




 (c) The D-type shown in the diagram is rising-edge triggered.



The signals applied to the clock and data inputs are shown below. Complete the timing diagram for the Q and  $\bar{Q}$  and outputs.


[3]

 



**BLANK PAGE**

 8. The circuit diagram shows a summing amplifier. The output saturates at  $\pm 16\text{V}$ .



- (a) Calculate  $V_{\text{OUT}}$  when  $S = 2.0\text{V}$  and  $T = 1.8\text{V}$ .

[2]



.....

.....

.....


- (b) Input S is kept at 2V DC but input at T is replaced with the following AC signal. Draw the graph for  $V_{OUT}$ .

[3]

  

**BLANK PAGE**

 9. The following diagram shows a 555 timer being used for an astable.



- (a) (i) Calculate the value for capacitor C to produce an output signal with a frequency of 1 Hz. [3]

.....

.....

.....


- (ii) Calculate the mark/space ratio for this astable. [2]

.....


.....

.....

 - (iii) Use your answer to part (ii) to sketch **two** cycles of the output waveform from this astable. [2]




 - (b) This diagram shows *rising-edge* triggered D-type flip-flops. Complete the diagram to make a 4-bit up-counter where A is the least significant bit. [3]



- (c) A student designs a light sequencer using a dedicated binary counter with the 1 Hz astable feeding pulses into the counter.

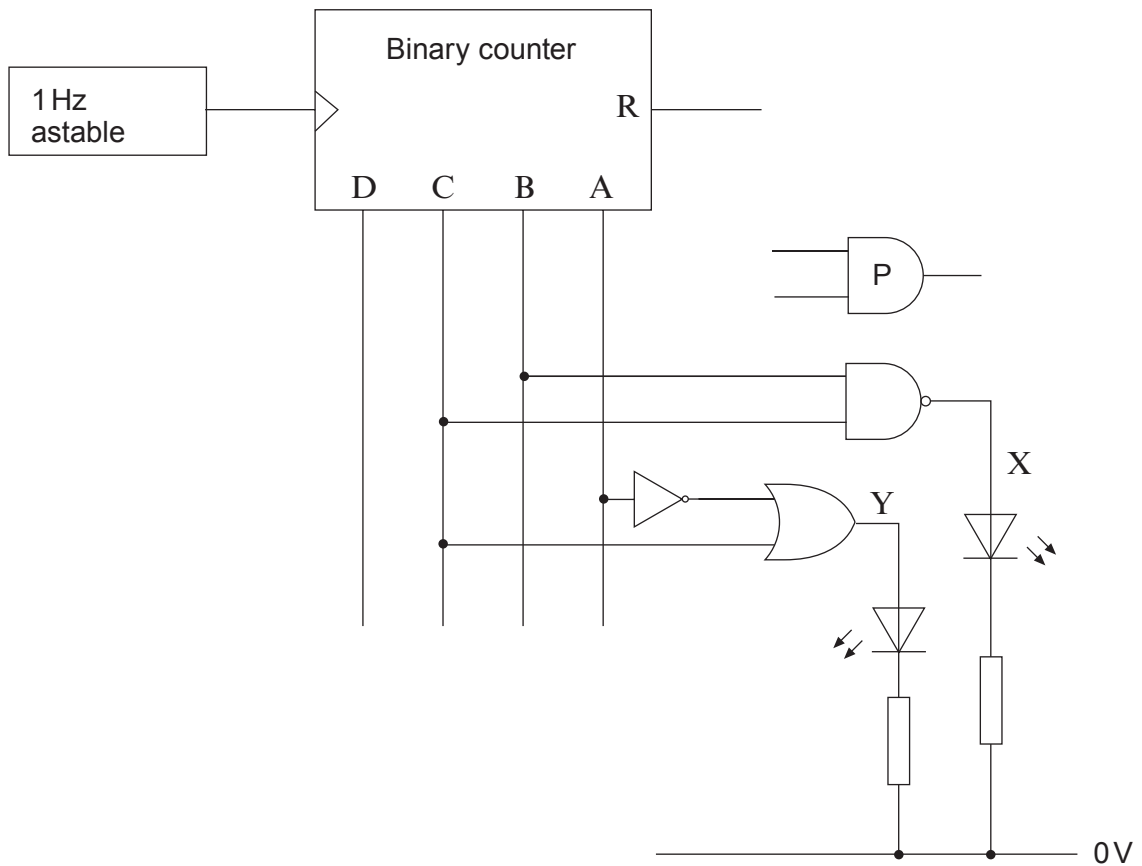- (i) Complete the diagram to make a counter that resets on the 9<sup>th</sup> pulse (modulo-9) using logic gate P. [2]



(ii) Complete the truth table for the light sequencer.

[3]

Examiner  
only

Clock pulse	D	C	B	A	X	Y
0	0	0	0	0		
1	0	0	0	1		
2	0	0	1	0		
3	0	0	1	1		
4	0	1	0	0		
5	0	1	0	1		
6	0	1	1	0		
7	0	1	1	1		
8	1	0	0	0		
9						

(iii) The system is reset. Describe what happens to LED X over a period of 8 seconds.

[2]

.....


.....

.....

.....

.....

 10. The following diagram shows an incomplete circuit for a full-wave rectified power supply.



(a) Add the components and connections necessary to complete the circuit. [3]

(b) The rms secondary voltage of the transformer is 8.5V. Calculate the peak value of the secondary voltage and hence the peak value of the output voltage. [3]

.....


.....

.....

.....

 (c) On the axes provided below, sketch a graph to show the voltage  $V_{OUT}$  when switch S is open. Label the axes with any relevant voltages. [2]


The voltage across the secondary windings of the transformer ( $V_S$ ) is shown as a dotted waveform.






 (d) Switch S is now closed.



Use the next set of axes to sketch the voltage  $V_{OUT}$  when a large current flows through the load resistor, R. [2]



 (e) The power supply is to be used to provide a regulated DC output. Draw a design for a Zener diode voltage regulator that can be added to the power supply to provide a steady 5.6V output across a load resistor R. Complete the circuit clearly labelling all components added. No calculations are required. [3]



  11. An op-amp voltage amplifier is required that produces the output signal  $V_{OUT}$  shown in the graph when signal  $V_{IN}$  is connected to its input.



- (a) Use this op-amp to design an amplifier that will produce the output  $V_{OUT}$ . Your design should include a circuit diagram labelled with suitable resistor values. [6]



.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

**END OF PAPER**