



---

# **GCE MARKING SCHEME**

---

**SUMMER 2018**

**GCE (LEGACY)  
ELECTRONICS - ET1  
1141/1**

## **INTRODUCTION**

This marking scheme was used by WJEC for the 2018 examination. It was finalised after detailed discussion at examiners' conferences by all the examiners involved in the assessment. The conference was held shortly after the paper was taken so that reference could be made to the full range of candidates' responses, with photocopied scripts forming the basis of discussion. The aim of the conference was to ensure that the marking scheme was interpreted and applied in the same way by all examiners.

It is hoped that this information will be of assistance to centres but it is recognised at the same time that, without the benefit of participation in the examiners' conference, teachers may have different views on certain matters of detail or interpretation.


WJEC regrets that it cannot enter into any discussion or correspondence about this marking scheme.

GCE (LEGACY)

ELECTRONICS - ET1


SUMMER 2018 MARK SCHEME

Question		Marking detail	Marks available	
1.	(a)	$D = B + \bar{A}$ $E = C.B$ $Q = \overline{C.B.(B + \bar{A})}$ or $\overline{(B + \bar{A}) + C.B}$ or $\bar{B}.A + \bar{C}.\bar{B}$ ( $\bar{C}.\bar{B}$ can be replaced by $\bar{C} + \bar{B}$ in either alternative answer)	1 1 1	
	(b)	(i) $(A.\bar{C}).(B + A)$ DeMorgan's theorem correctly applied Allow double bar over each term $A.B.\bar{C} + A.\bar{C}$ allow $A.B.\bar{C} + A.\bar{C}.A$ $A.\bar{C}(B + 1)$ either or both simplifications $A.\bar{C}$ Simplest expression stated  Input B is redundant (mark can only be awarded if results from correct analysis)	1 1 1  1	
			<b>7</b>	
2.	(a)	(i)	$P = \bar{C}.B.\bar{A} + C.\bar{B}.\bar{A} + C.B.\bar{A}$	1
		(ii)	<p>Correct transfer to Karnaugh map</p> $P = B.\bar{A} + C.\bar{A}$ or $P = \bar{A}.(B + C)$ 1 mark for each correctly identified group from table drawn (max. 2)	1 2
	(iii)	Input A connected to input of NOT gate. Then either Inputs B and C connected in inputs of OR gate Outputs of NOT and OR connected to P using AND gate  OR Inputs B and C each to a separate AND gate with output of NOT A Outputs of AND gates to P via an OR gate	1 1 1  OR 1 1	

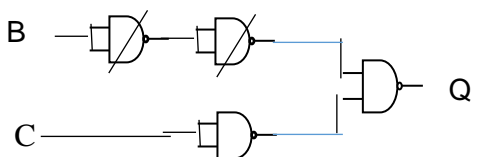Question		Marking detail	Marks available
	(b)	 <p>Input B shown with redundant gates or as a direct connection to final NAND gate. Input C connected through NAND inverter to final NAND gate.</p>	1 1
			9

Question			Marking detail	Marks available																																				
3.	(a)	(i)	<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>C</th> <th>B</th> <th>A</th> <th>Q</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table> <p>Column Q correct</p>	C	B	A	Q	0	0	0	0	0	0	1	1	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	1	1	1	0	0	1	1	1	0	1
		C	B	A	Q																																			
		0	0	0	0																																			
		0	0	1	1																																			
		0	1	0	0																																			
0	1	1	0																																					
1	0	0	1																																					
1	0	1	1																																					
1	1	0	0																																					
1	1	1	0																																					
(ii)	$Q = \bar{C}.\bar{B}.A + C.\bar{B}.\bar{A} + C.\bar{B}.A$ or $C.\bar{B} + \bar{B}.A$ or $\bar{B}.(C + A)$	1																																						
(b)	D <sub>0</sub> , D <sub>2</sub> , D <sub>3</sub> , D <sub>6</sub> and D <sub>7</sub> to 0 V D <sub>1</sub> , D <sub>4</sub> , and D <sub>5</sub> to 5 V Completely correct 1 mark (allow ecf from (a))	1																																						
(c)	LED (correct orientation) and series resistor connected between power rail and Q Between Q and 0 V	1																																						
			<b>5</b>																																					

Question			Marking detail	Marks available																																													
4.	(a)		All 3 clock inputs correctly connected $\bar{Q}$ outputs to D (all 3 correct) Q outputs to correct terminals	1 1 1																																													
	(b)	(i)	<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>C</th> <th>B</th> <th>A</th> <th>X</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> </tbody> </table> <p style="text-align: center;">One mark each correct column X and Y</p>	C	B	A	X	Y	0	0	0	1	1	0	0	1	1	0	0	1	0	0	1	0	1	1	0	0	1	0	0	1	0	1	0	1	1	1	1	1	0	0	0	1	1	1	0	1	2
		C	B	A	X	Y																																											
0	0	0	1	1																																													
0	0	1	1	0																																													
0	1	0	0	1																																													
0	1	1	0	0																																													
1	0	0	1	0																																													
1	0	1	1	1																																													
1	1	0	0	0																																													
1	1	1	0	1																																													
(ii)	A pulses twice clock duration starting on the first falling edge of the clock. Both pulses B and C correct duration Both pulses B and C correct timing. X inverse of B Y logic 1 for first two <b>spaces</b> of A and then logic 1 for last two <b>pulses</b> of A. Allow bod if X or Y starting from first falling edge of A. (X and Y ecf from table)	1 1 1 1 1																																															
(c)	Convert frequency to time period using $T=1/f = 1/0.2 = 5 \text{ s}$ C has a duration of 4 pulses. $4 \times 5 = 20 \text{ s}$	1 1																																															
				<b>12</b>																																													

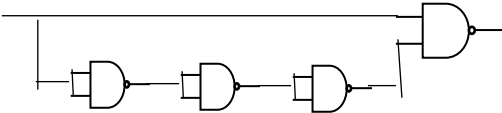Question		Marking detail	Marks available																											
5	(a)	The transition gate produces edge-triggering /produces a <u>very short</u> pulse.	1																											
	(b)	An odd number of NAND's as series NOT gates Correct connections to the final NAND gate (Final NAND inverter is neutral) e.g.	1 1																											
	(c)	 <table border="1" data-bbox="518 616 949 1008"> <thead> <tr> <th>A</th> <th>B</th> <th>X</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> </tbody> </table> <p>X has correct response to SET (when A=0 initially) Y has correct response to RESET (when B=0 initially) (mark for 1<sup>st</sup> four lines only) Correct last line</p>	A	B	X	Y	1	1	0	1	0	1	1	0	1	1	1	0	1	0	0	1	1	1	0	1	0	0	1	1
A	B	X	Y																											
1	1	0	1																											
0	1	1	0																											
1	1	1	0																											
1	0	0	1																											
1	1	0	1																											
0	0	1	1																											
			<b>6</b>																											
6.	(a)	(i)	S (no mark) ' <u>as it has the higher slew rate</u> ' (or <b>both</b> time calculations shown)	1																										
		(ii)	$3.6 \times 10^6/400$ (correct substitution and re-arrangement) 9000 (Hz) or 9 k(Hz) or 0.009M(Hz)	1 1																										
	(b)	Downward sloping line starting at 2 $\mu$ s Correct gradient (passes through 4,-9) Saturates at -18 V	1 1 1																											
	(c)	(i)	$12.5/2.5 = (-) 5$	1																										
		(ii)	Resistor connected between output and inverting input Resistor connected between $V_{IN}$ and inverting input Non-inverting input connected to 0V (NIA = 1 mark)	1 1 1																										
		(iii)	Ratio $R_F/R_{IN} = 5$ <b>and</b> both 1 k $\Omega$ or greater (ecf (i) and (ii)) Clearly labelled on diagram (accept in written answer if unambiguous). Full credit for NIA values if correct wrt earlier parts.	1 1																										
			<b>12</b>																											

Question		Marking detail	Marks available	
7.	(a)	Max. gain = 41 Min. gain = 1	1 1	
	(b)	Bandwidth measured at $20/\sqrt{2}$ or $0.7 \times 20 (\cong 14)$ (indicated on graph or implied) 125 (kHz) range 125-127	1	
			1	
	(c)	14/30 or 14000/30 (correct substitution) 0.466 or 0.46 or 0.466 mV (rounded-up answers e.g. 0.467 award 1-mark total as this will go over saturation voltage)	1	
			1	
	(d)	(i)	Voltage gain <b>reduces</b>	1
		(ii)	Input voltage <b>increases</b>	1
(iii)		Gain- bandwidth product <b>remains constant / unchanged</b>	1	
			<b>9</b>	