



GCE MARKING SCHEME

SUMMER 2019

**ELECTRONICS - ET5 (LEGACY)
1145/01**

INTRODUCTION

This marking scheme was used by WJEC for the 2019 examination. It was finalised after detailed discussion at examiners' conferences by all the examiners involved in the assessment. The conference was held shortly after the paper was taken so that reference could be made to the full range of candidates' responses, with photocopied scripts forming the basis of discussion. The aim of the conference was to ensure that the marking scheme was interpreted and applied in the same way by all examiners.

It is hoped that this information will be of assistance to centres but it is recognised at the same time that, without the benefit of participation in the examiners' conference, teachers may have different views on certain matters of detail or interpretation.


WJEC regrets that it cannot enter into any discussion or correspondence about this marking scheme.

GCE ELECTRONICS - ET5

SUMMER 2019 MARK SCHEME

1. (a) (i) Time delay between change at input of system and resulting change at output.
(or equivalent answer.) 1 mark
- (ii) All stages receive clock pulses simultaneously, and so all change at the same time when a clock pulse is received. 1 mark

- (b) (i)

 

- Correct **clock** connections 1 mark
- Use of **EXNOR** gate with correct inputs for D_C or use of NOT gate 1 mark
- Use of **EXOR** gate with correct inputs for D_B or use of NOT gate 1 mark
- Use of \overline{Q}_A 1 mark

- (ii)

State	C	B	A	D_C	D_B	D_A
0	0	1	0	0	1	1
1	0	1	1	1	0	0
2	1	0	0	1	0	1
3	1	0	1	0	1	0


1 mark per transition x 3 3 marks

- (iii)

State	C	B	A	C	B	A
4	0	0	0	1	0	1
5	0	0	1	0	1	0
6	1	1	0	0	1	1
7	1	1	1	1	0	0

1 mark per transition x 4 4 marks

(iv)

 

Main sequence

1 mark


Unused states

1 mark

Total for Q1 15

2. (a) Use of variable resistor in one limb 1 mark
 Any bridge arrangement with T_{IN} and T_{OUT} 1 mark
 Correct orientation 1 mark

(b)

 

- (i) Correct connections to inverting input 1 mark
 Correct connections to non-inverting input 1 mark
- (ii) Resistor ratio = 50:1 1 mark
- (c) (i) Voltage at R = 40mV 1 mark
 Voltage at Q = 80mV 1 mark
 Voltage at P = 120mV 1 mark

(ii)

Output of Diff amplifier	V_W	V_X	V_Y	Binary output	
				B	A
0.03V	0	0	0	0	0
0.10V	12	12	0	1	0

- Correct op-amp outputs for 0.03V 1 mark
 Correct binary output for 0.03V 1 mark
 Correct op-amp outputs for 0.10V 1 mark
 Correct binary output for 0.10V 1 mark
- (iii) Indicate when input exceeds input voltage range, or equivalent 1 mark
- (iv) Resolution is reduced equivalent 1 mark
- (v) No. of comparators = 256 1 mark

Total for Q2 16

3. (a) Active filters can have gain >1 (or equivalent) 1 mark
- (b) Filter **D** = Treble cut 1 mark
- Filter **B** = Bass boost 1 mark
- (c) Reactance = $24\text{k}\Omega$ at the break frequency (= 200Hz), or equivalent 1 mark
- (d) (i) Amplitude at output of A = **200mV** 1 mark
- (ii) Frequency at output of A = **500Hz** 1 mark
- (e) (i) Resistor 1 = **$200\text{k}\Omega$** 1 mark
- Resistor 2 = **$10\text{k}\Omega$** 1 mark
- (ii) Capacitor = **1nF** 1 mark
- Use of $200\text{k}\Omega$ resistor in break frequency formula** (allow ecf) 1 mark

Total for Q3 10


4. (a) If monitoring the stop button were part of the main program, the response would be delayed if the main program were executing one of the delay subroutines when the stop button was pressed. or equivalent answer 1 mark
- (b) `movlw b'10010000'`
`movwf INTCON`
 Global interrupt AND Port B0 interrupt enabled 1 mark
 All other bits correct 1 mark
- (c) (i) Instruction protects the contents of the working register as it enters the ISR so that they can be recovered when the program returns to the main program on completing the ISR. or equivalent answer 1 mark
- (ii) `movf tempstore` 1 mark
- (d) **repeat** `bsf PORTA,0`
`bcf PORTA,1`
`call oneseq`
`bsf PORTA,1`
`bcf PORTA,0`
`call oneseq`
 Correct control of lamp X 1 mark
 Correct control of lamp Y 1 mark
 Correct timing 1 mark
- (e) **btfss** PORTB,2 1 mark
goto repeat 1 mark

Total for Q4 10

5. (a) (i) Best input impedance = 1600k Ω 1 mark
(ii) Best output impedance = 16 Ω 1 mark
- (b) (i) Overall gain = product of gains = 625 1 mark
(ii) Bandwidth = 240kHz (allow ecf from (i)) 1 mark
Use of gain-bandwidth product 1 mark
- (c) (i) Voltage at P = 6.0V 1 mark
(ii) Output voltage = 5.3V (allow ecf from (i)) 1 mark
(iii) Voltage across transistor = 6.7V (allow ecf from (ii)) 1 mark
(iv) Power dissipation = 1.3W (allow ecf from (iii)) 1 mark
(v) Max. power dissipated in speaker = 1.125W 1 mark
Use of 12V in max. power formula 1 mark

Total for Q5 11

 6. (a) Thyristor added correctly 1 mark
Diac added correctly 1 mark
- (b) Phase angle = **72.3 $^{\circ}$** 1 mark
Use of X_C 1 mark
Re-arranged formula 1 mark



- (c) Switching at 25V 1 mark
 V_T correct 1 mark
 V_L correct 1 mark

Total for Q6 8