

Surname	Centre Number	Candidate Number
Other Names		0



**GCSE**

4161/01

**ELECTRONICS**

**UNIT E1 – Paper replacement test**

A.M. WEDNESDAY, 22 May 2013

1 hour

For Examiner's use only		
Question	Maximum Mark	Mark Awarded
1.	3	
2.	3	
3.	3	
4.	3	
5.	2	
6.	4	
7.	3	
8.	3	
9.	4	
10.	3	
11.	3	
12.	4	
13.	2	
14.	1	
15.	2	
16.	4	
17.	2	
18.	1	
19.	5	
20.	5	
Total	60	

### ADDITIONAL MATERIALS

In addition to this paper you may require a calculator.

### INSTRUCTIONS TO CANDIDATES

Use black ink or black ball-point pen.

Write your name, centre number and candidate number in the spaces at the top of this page.

Answer **all** questions in the spaces provided in this booklet.

### INFORMATION FOR CANDIDATES

The number of marks is given in brackets at the end of each question or part-question.

## INFORMATION SHEET FOR UNIT E1

This information may be of use in answering the questions.

### 1. Resistor Colour Codes

<b>BLACK</b>	<b>0</b>	<b>GREEN</b>	<b>5</b>
<b>BROWN</b>	<b>1</b>	<b>BLUE</b>	<b>6</b>
<b>RED</b>	<b>2</b>	<b>VIOLET</b>	<b>7</b>
<b>ORANGE</b>	<b>3</b>	<b>GREY</b>	<b>8</b>
<b>YELLOW</b>	<b>4</b>	<b>WHITE</b>	<b>9</b>

The fourth band colour gives the tolerance as follows:

**GOLD**     $\pm$     **5%**

**SILVER**    $\pm$     **10%**

### 2. Preferred Values for Resistors – E24 series


10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91.

3. **Resistance** =  $\frac{\text{voltage}}{\text{current}}$  ;  $R = \frac{V}{I}$ .

4. **Effective resistance**,  $R$ , of two resistors  $R_1$  and  $R_2$  in series is given by  $R = R_1 + R_2$ .

5. **Effective resistance**,  $R$ , of two resistors  $R_1$  and  $R_2$  in parallel is given by  $R = \frac{R_1 R_2}{R_1 + R_2}$ .

### 6. Voltage Divider

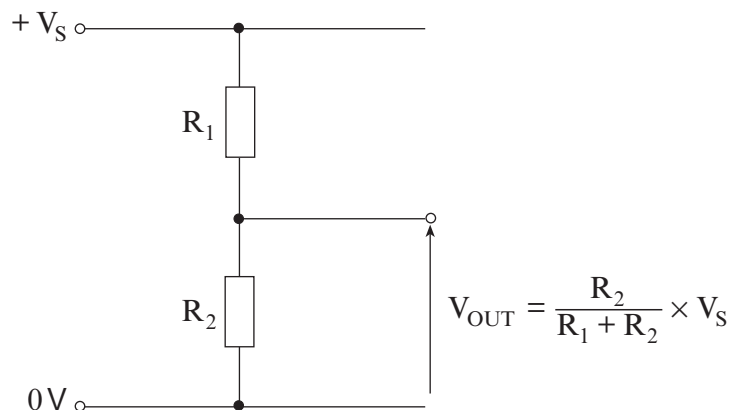

7. **Power** = voltage  $\times$  current;  $P = VI = I^2 R = \frac{V^2}{R}$ .

8. **LED** The forward voltage drop across an LED is 2V.

9. **NPN Transistors**      (i) **Current gain** =  $\frac{\text{Collector current}}{\text{Base current}}$ ;  $h_{FE} = \frac{I_C}{I_B}$ .

(ii) The forward voltage drop across the base emitter junction is 0.7 V.

Answer **all** questions.

1. Here is a list of electronic output components.

*buzzer*


*lamp*

*LED*


*motor*

*solenoid*

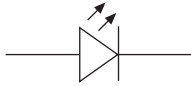Select the correct name for **each** component.





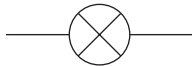


[3]

2. The following electronic sub-systems can be used to build larger systems.

*AND gate*

*delay unit*

*lamp unit*

*latch unit*

*pulse generator*

Select the names of the sub-systems above that answer the questions below.


- (a) Which of these sub-systems is an output sub-system?

- (b) Which of these sub-systems will keep an output on for a fixed period of time?

- (c) Which of these sub-systems can be used to produce a flashing light?

[3]

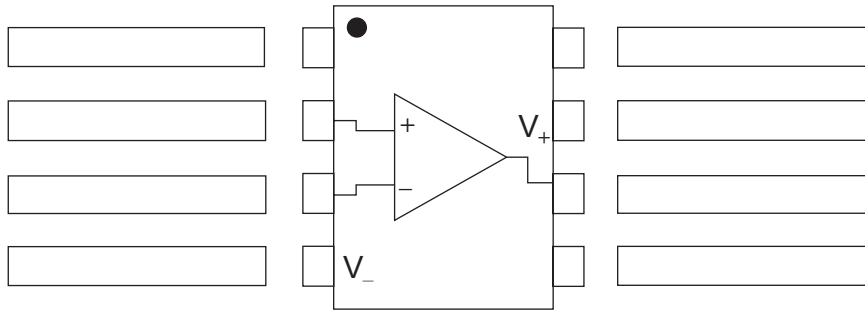3. The following diagram shows the pinout of a comparator IC.



Label the pins on the comparator IC which connect to the:


positive supply

negative supply

non-inverting input

[3]

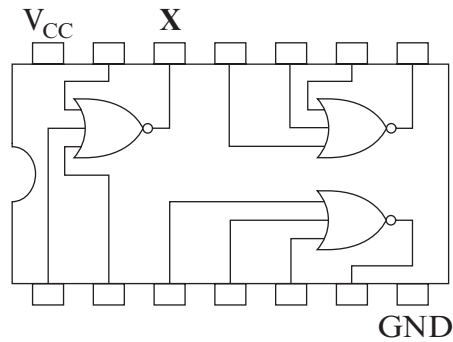4. Here is the pinout for a logic gate IC.



- (a) What type of logic gate is contained in this IC? (**Circle** the correct answer.)

AND gate

OR gate

NAND gate

NOR gate

NOT gate

[1]

- (b) How many inputs does each gate have?

.....

[1]

- (c) What is the pin number of the terminal labelled 'X'?

.....

[1]

5. Choose from the following logic gates to answer both parts of this question.

AND      NAND      NOR      NOT      OR

- (a) What is the logic gate that has the following truth table?

Inputs		Output
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

Logic gate .....


[1]

- (b) Which logic gate outputs a logic 0 signal only when both inputs are at logic 0?

[1]

.....

6. Here are some resistor networks.

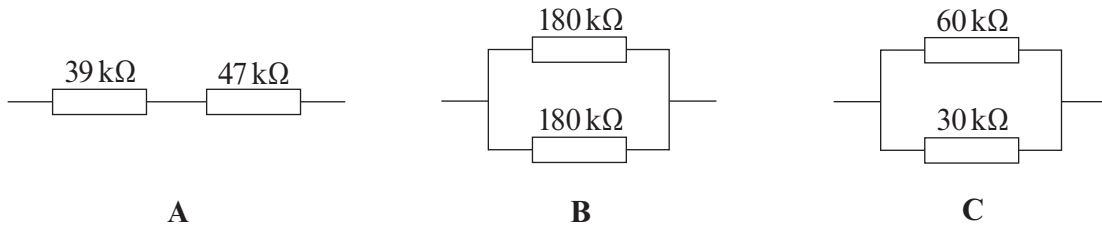

(a) The resistors in networks **B** and **C** are connected in

Series

Parallel

(Circle the correct answer.)

[1]

(b) Which network **A**, **B** or **C** has the lowest total resistance? .....

[1]

(c) What is the total resistance of network **A**? .....

kΩ


[1]

(d) What is the total resistance of network **C**? .....

kΩ

[1]

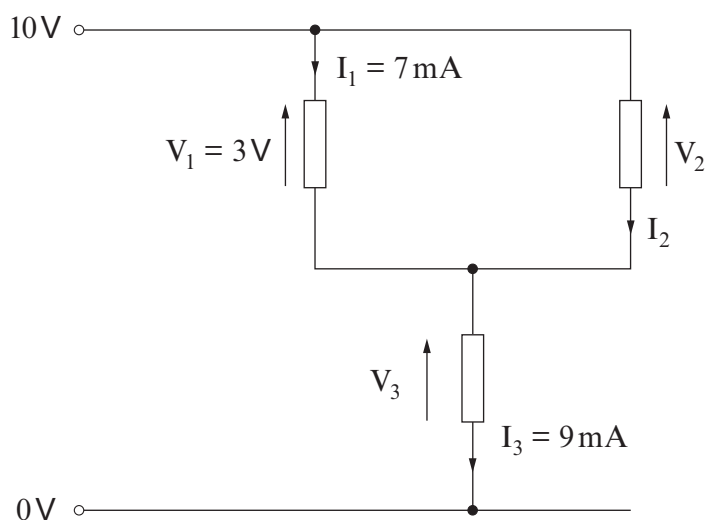7. Study the following circuit containing three resistors.



- (a) What is the value of  $V_2$  in volts? (**Circle** the correct answer.)

[1]

0 1 2 3 4 5 6 7 8 9 10

- (b) What is the value of  $V_3$  in volts? (**Circle** the correct answer.)

[1]


0 1 2 3 4 5 6 7 8 9 10

- (c) What is the value of  $I_2$  in mA? (**Circle** the correct answer.)

[1]

0 1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16

8. Here are four motors.

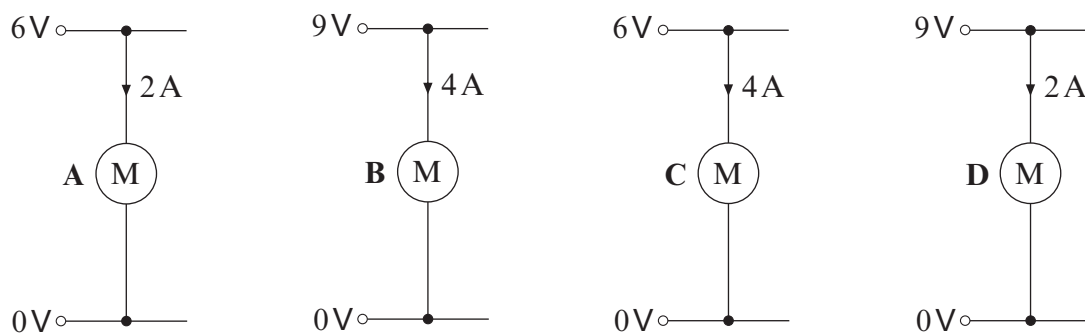

(a) Which motor is using the least power? .....

[1]

(b) (i) Tick (✓) the correct equation to calculate the power of Motor **B**.

[1]

☐

$P = 9 + 4$

☐

$P = \frac{9}{4}$

☐

$P = 9 \times 4$

☐

$P = 9 - 4$

☐

$P = 4 + 9$

☐

$P = \frac{4}{9}$

(ii) Calculate the power of Motor **B**.

[1]


Power = ..... W



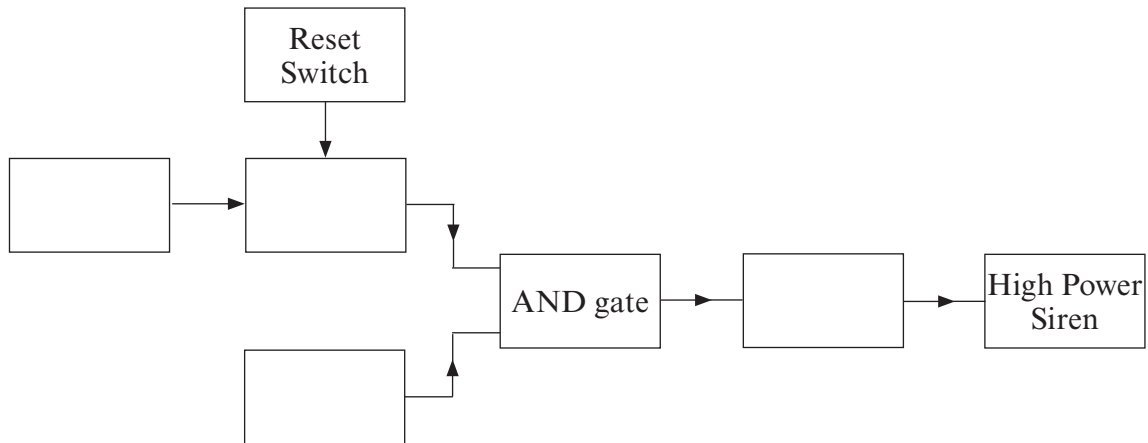9. A shopkeeper wants to install a burglar alarm in his shop to protect his business. The alarm should provide a pulsed output, and once activated the alarm must remain on until reset manually.

*Delay Unit      Latch Unit      Magnetic Switch Unit      MOSFET*  
*OR Gate      Pulse Generator      Thyristor*


Complete the block diagram for the alarm system.



[4]

4161  
010009

10. The diagram shows a resistor.

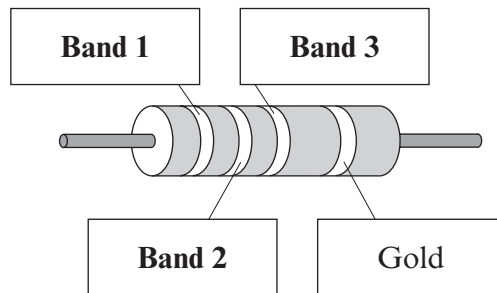

The resistor has a value of  $91\ \Omega$ ,  $\pm 5\%$ .

Use the information sheet to write down the correct colour for bands 1, 2 and 3 present on this resistor.

**Band 1**

**Band 2**

**Band 3**

.....


.....

.....

[3]

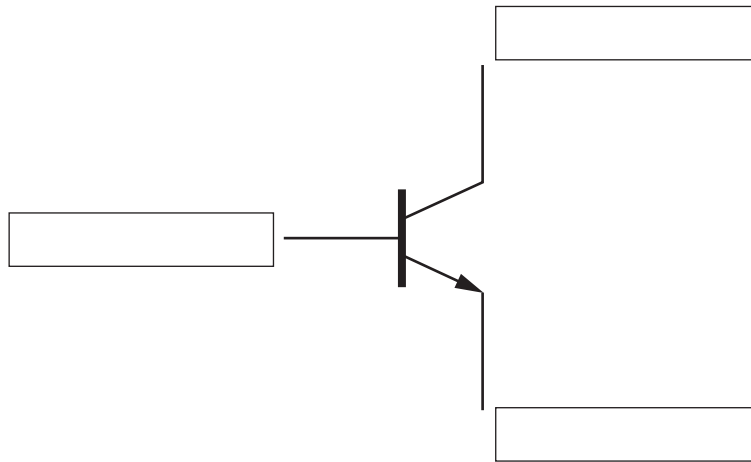11. Here are some labels:


Base      Collector      Drain      Source      Emitter      Gate



Use the labels to complete the diagram of a transistor.

[3]

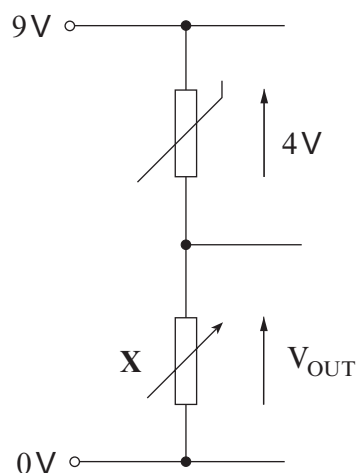12. Here is the circuit diagram for a temperature sensing unit.



(a) **Circle** the name of the component labelled X.

Resistor

Variable resistor

LDR

Thermistor

[1]

(b) What is the value of  $V_{OUT}$ ? ..... V

[1]

(c) (i) What happens to the resistance of the thermistor as the temperature increases? (Tick (✓) the correct answer.)

☐

It increases

☐

It is not affected by temperature

☐

It stays the same

☐

It decreases

[1]

(ii) What happens to the value of  $V_{OUT}$  when the temperature increases? (Tick (✓) the correct answer.)

☐

It increases

☐

It stays the same

☐


It decreases

☐

It depends on how good the power supply is

[1]

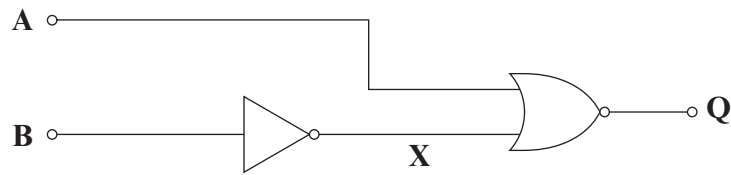
13. Complete the truth table for the following logic system.



A	B	X	Q
0	0		
0	1		
1	0		
1	1		

[2]

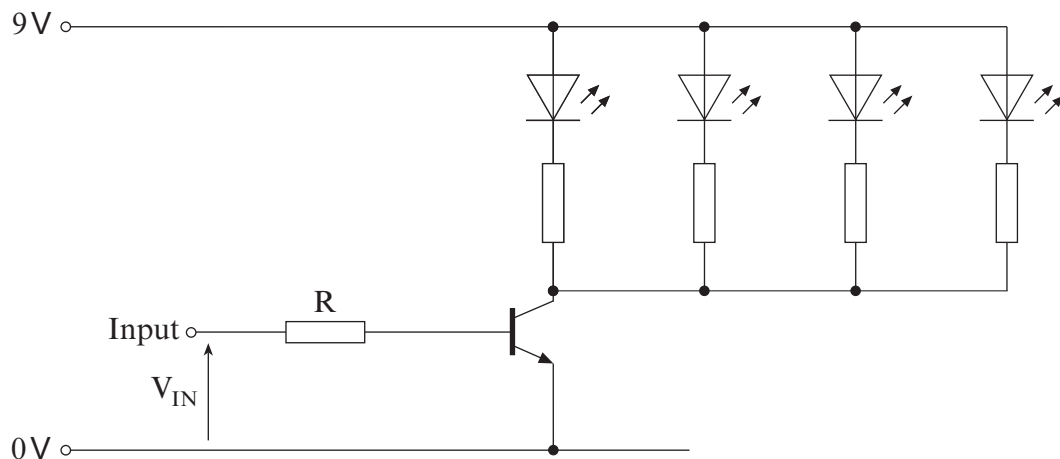14. The circuit diagram shows part of a system used to switch on an array of LEDs.



Complete the table with the word 'ON' or 'OFF' to show what happens to the LEDs for each value of  $V_{IN}$ .

$V_{IN}$	LEDs ON/OFF?
0.4V	
2.5V	

[1]

15. (a) Circle the correct Boolean Equation that represents an OR gate.

$A.B$

$A + B$

$\overline{A}.B$

$A.\overline{B}$

[1]

- (b) Select the correct Boolean Equation that represents the function described by the truth table. (Tick (✓) the correct answer.)

Input A	Input B	Output Q
0	0	0
0	1	0
1	0	1
1	1	0

☐

$Q = A \text{ AND } B$

☐

$Q = A \text{ OR } B$

☐



$Q = \text{NOT } A \text{ AND } B$

☐

$Q = A \text{ AND NOT } B$


[1]

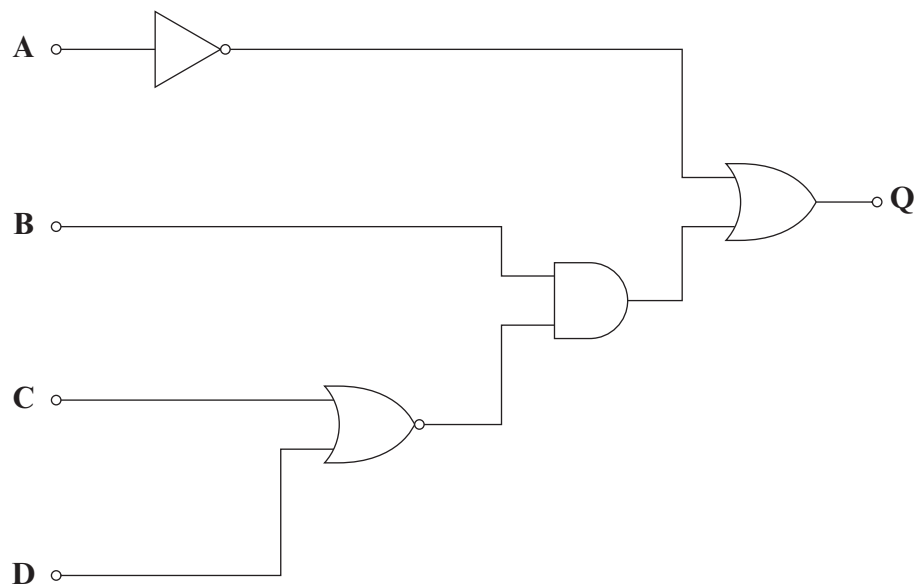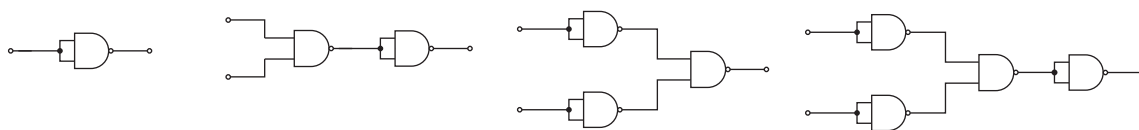16. The following show the NAND equivalent circuits of a number of standard gates.




The circuit above is constructed from standard logic gates.

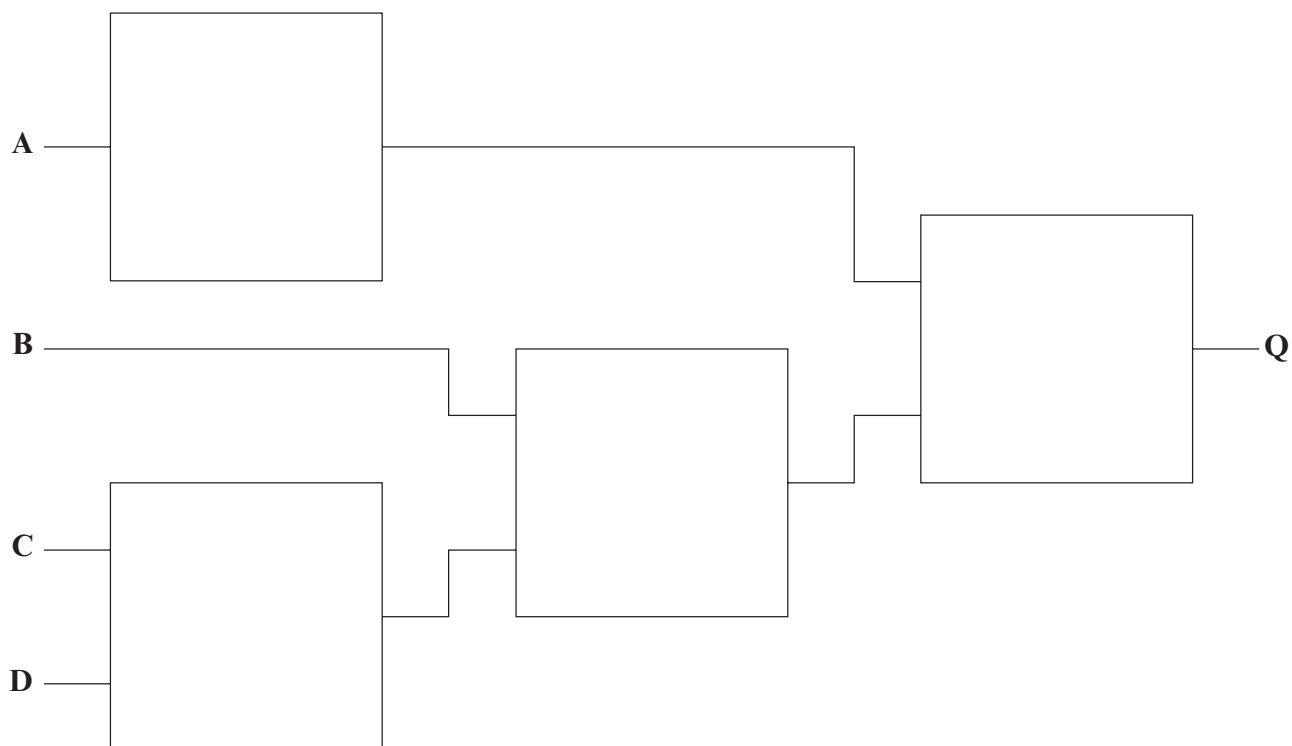Complete the circuit below to show how the same circuit can be made using NAND gates only.



[4]

17. Look at the following circuit.

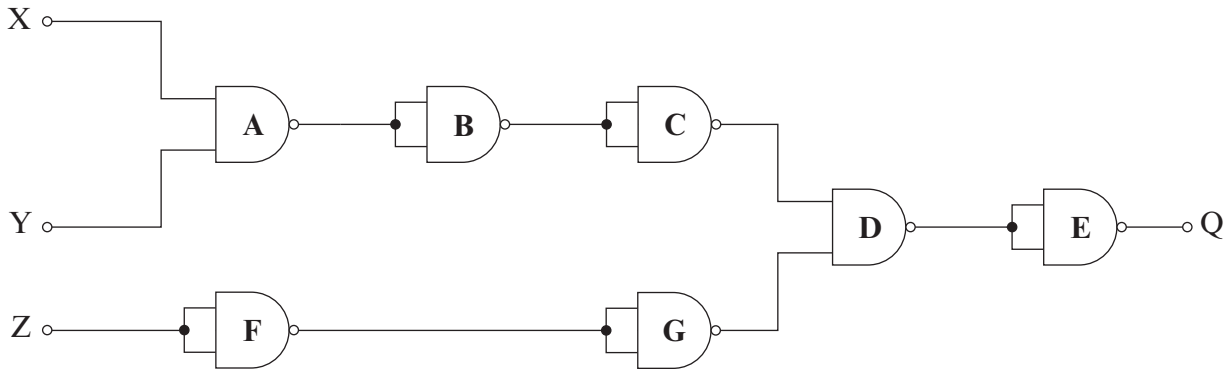


Which of the following pairs of gates are redundant? (Tick (✓) the correct answers.)

- |                                |                                |                                |                                |
|--------------------------------|--------------------------------|--------------------------------|--------------------------------|
| <input type="checkbox"/> A & B | <input type="checkbox"/> B & C | <input type="checkbox"/> C & D | <input type="checkbox"/> D & E |
| <input type="checkbox"/> A & F | <input type="checkbox"/> F & G | <input type="checkbox"/> C & G | <input type="checkbox"/> G & D |

[2]

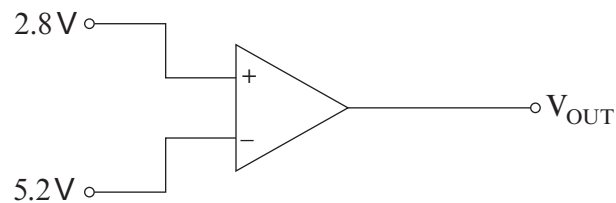18. The following diagram shows a comparator. The output  $V_{OUT}$  of the comparator saturates at 0V and 9.0V.




The output of the comparator is: (Tick (✓) the correct answer.)

- ☐ 0V
- ☐ 2.8V
- ☐ 3.4V
- ☐ 5.2V
- ☐ 8.0V
- ☐ 9.0V

[1]

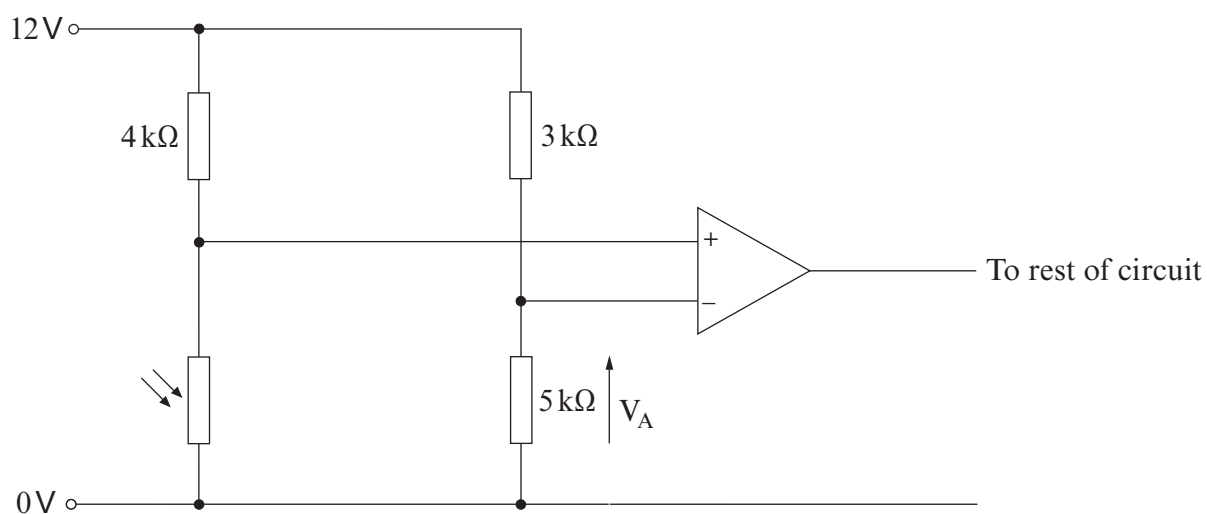19. The following **incomplete** circuit shows a comparator used to switch on a floodlight when it gets dark.



- (a) (i) Which of the following is the correct formula to calculate the voltage  $V_A$ ?  
(Tick (✓) the correct answer.)

[1]

☐  $V_A = \frac{3}{3+5} \times 12$

☐  $V_A = \frac{4}{3+5} \times 12$

☐  $V_A = \frac{5}{3+5} \times 12$

☐  $V_A = \frac{5}{3+4} \times 12$

- (ii) Calculate the voltage  $V_A$  at the inverting input of the comparator.

$$V_A = \dots\dots\dots \text{ V}$$



[1]



- (b) The following **incomplete** circuit shows a comparator used to switch on a floodlight when it gets dark.

When the light level gets too dark the floodlight comes on, and then switches off automatically when it gets light.

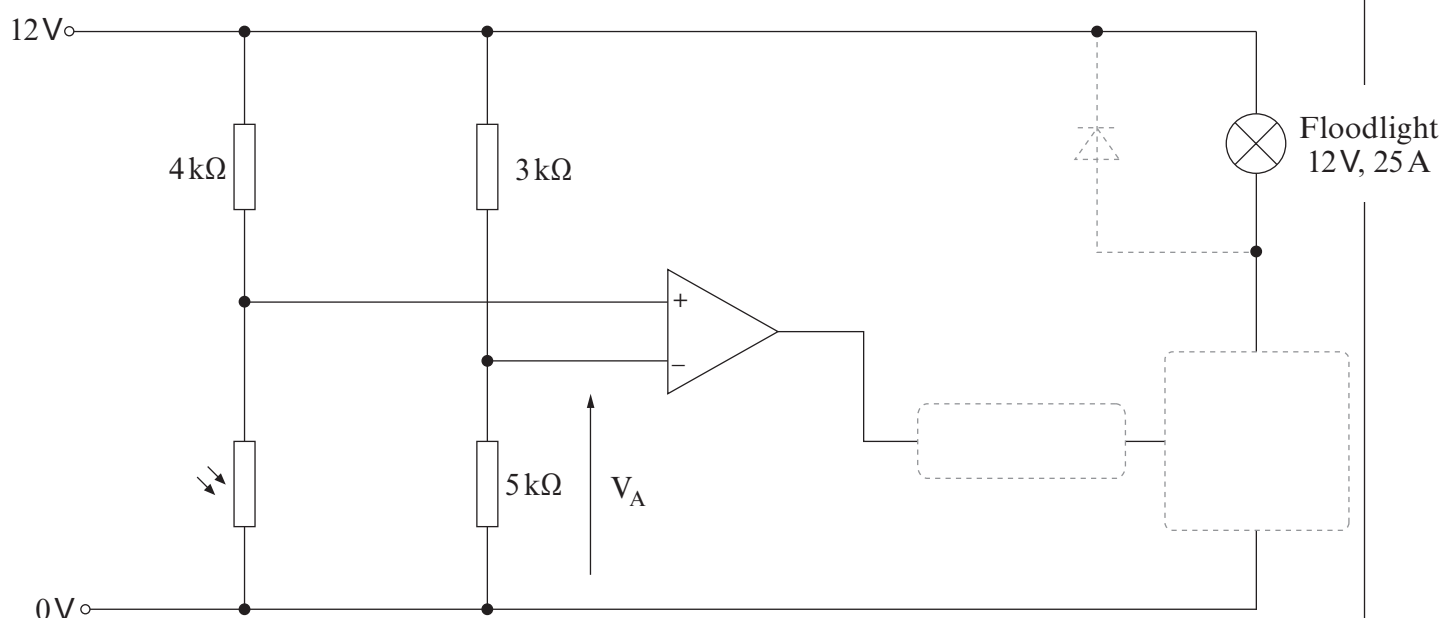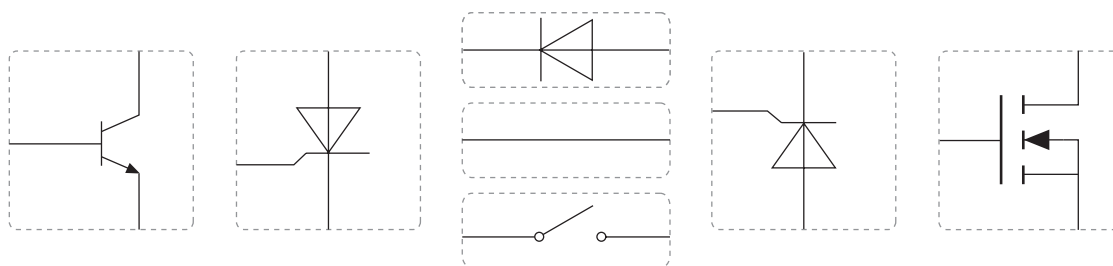- (i) Complete the output circuit using the components shown below.



[2]


- (ii) A diode is shown 'dotted' around the floodlight. The diode is **not** required in this circuit. Give a reason why.

[1]

.....

.....

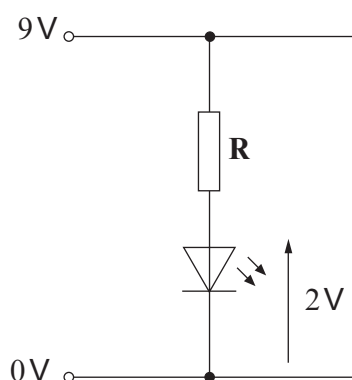20. An LED is to be used as a power-on indicator as shown below.  
The LED requires a current of 14 mA.



- (a) What is the current through resistor **R** when the LED is lit? ..... mA [1]
- (b) What is the voltage drop across the resistor **R** when the LED is lit? ..... V [1]
- (c) (i) Select the correct formula to calculate the ideal resistance of resistor **R** (in kΩ).  
(Tick (✓) the correct answer.)

☐

$R = 2 \times 14$

☐

$R = \frac{2}{14}$

☐

$R = \frac{7}{14}$

☐

$R = 7 \times 14$

☐

$R = 9 \times 2$

☐

$R = \frac{9}{14}$

☐

$R = \frac{9}{2}$

☐

$R = 9 \times 14$

[1]

- (ii) What is the ideal resistance of resistor **R**? ..... kΩ [1]
- (d) Use the E24 resistor series on the information sheet to select the preferred value for resistor **R** to ensure that the current through the LED is no more than 14 mA. [1]

..... kΩ

**END OF PAPER**

**BLANK PAGE**