

Surname	Centre Number	Candidate Number
Other Names		0



**GCSE**

4162/01

**ELECTRONICS**

**UNIT E2**

**(Paper version of on-screen assessment)**

A.M. WEDNESDAY, 5 June 2013

1 hour

For Examiner's use only		
Question	Maximum Mark	Mark Awarded
1.	2	
2.	2	
3.	3	
4.	2	
5.	3	
6.	1	
7.	2	
8.	2	
9.	2	
10.	4	
11.	2	
12.	2	
13.	1	
14.	3	
15.	4	
16.	5	
17.	2	
18.	1	
19.	3	
20.	3	
21.	4	
22.	3	
23.	1	
24.	1	
25.	2	
Total	60	

### ADDITIONAL MATERIALS

In addition to this paper you may need a calculator.

### INSTRUCTIONS TO CANDIDATES

Use black ink or black ball-point pen.

Write your name, centre number and candidate number in the spaces at the top of this page.

Answer **all** questions in the spaces provided in this booklet.

### INFORMATION FOR CANDIDATES

The number of marks is given in brackets at the end of each question or part-question.

## INFORMATION SHEET FOR UNIT E2

This information may be of use in answering the questions.

### 1. Resistor Colour Codes

<b>BLACK</b>	<b>0</b>	<b>GREEN</b>	<b>5</b>
<b>BROWN</b>	<b>1</b>	<b>BLUE</b>	<b>6</b>
<b>RED</b>	<b>2</b>	<b>VIOLET</b>	<b>7</b>
<b>ORANGE</b>	<b>3</b>	<b>GREY</b>	<b>8</b>
<b>YELLOW</b>	<b>4</b>	<b>WHITE</b>	<b>9</b>

The fourth band colour gives the tolerance as follows:

**GOLD**     $\pm$     **5%**

**SILVER**    $\pm$     **10%**

### 2. Preferred Values for Resistors – E24 series


10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91.

3. **Resistance** =  $\frac{\text{voltage}}{\text{current}}$  ;  $R = \frac{V}{I}$ .

4. **Effective resistance**,  $R$ , of two resistors  $R_1$  and  $R_2$  in series is given by  $R = R_1 + R_2$ .

5. **Effective resistance**,  $R$ , of two resistors  $R_1$  and  $R_2$  in parallel is given by  $R = \frac{R_1 R_2}{R_1 + R_2}$ .

### 6. Voltage Divider

 

7. **Power** = voltage  $\times$  current;  $P = VI = I^2 R = \frac{V^2}{R}$ .

8. **LED** The forward voltage drop across an LED is 2V.

9. **NPN Transistors**    (i) **Current gain** =  $\frac{\text{Collector current}}{\text{Base current}}$ ;  $h_{FE} = \frac{I_C}{I_B}$ .

(ii) The forward voltage drop across the base emitter junction is 0.7V.

**10. Amplifiers**

Voltage gain:  $A = \frac{V_{\text{OUT}}}{V_{\text{IN}}}$

Non-inverting amplifier:  $A = 1 + \frac{R_F}{R_1}$


Inverting amplifier:  $A = -\frac{R_F}{R_{\text{IN}}}$

Summing amplifier:  $V_{\text{OUT}} = -R_F \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots \right)$

Answer **all** questions.

 1. The diagram shows a 7-segment display.

A logic 1 signal makes a segment light up.



- (a) Identify the character generated by the following signals.

[1]


Segments							Character displayed
a	b	c	d	e	f	g	
1	1	1	1	0	0	1	

- (b) Complete the signals needed to display the letter 'L'.

[1]

Segments							Character displayed
a	b	c	d	e	f	g	
							L

 2. (a) Select the name of the sub-system shown in the diagram. (Tick (✓) the correct answer.) [1]




- ☐ Astable  
☐ Monostable  
☐ Latch  
☐ Counter

 - (b) This sub-system is *falling-edge triggered*.

The pulse shown below is applied to the trigger input.


Select the point A, B, C, D or E at which the sub-system will be triggered. (Tick (✓) the correct answer.) [1]



- ☐ A  
☐ B  
☐ C  
☐ D  
☐ E

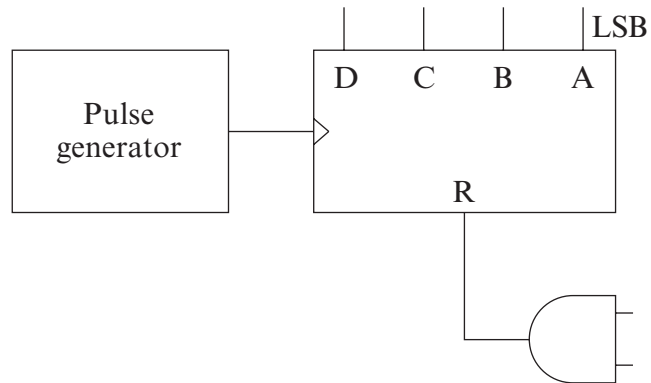3. A system counts up to 5 and then resets on the 6<sup>th</sup> pulse.

Output A is the least significant bit (LSB).



- (a) What is the output when the count equals 5?

[1]


	D	C	B	A
Output				

- (b) Select the **two** counter outputs which must be connected to the AND gate to make the counter reset every sixth pulse. (Tick (✓) the correct answers.)

[2]

D	C	B	A
<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

 4. The circuit diagram shows an **RC network** connected to an inverting buffer to create a time delay.



- (a) Which combination gives the **shortest** time delay? (Tick (✓) the correct answer.) [1]

	Resistor R	Capacitor C
<input type="checkbox"/>	5.6 kΩ	10 μF
<input type="checkbox"/>	560 kΩ	10 μF
<input type="checkbox"/>	5.6 kΩ	100 μF
<input type="checkbox"/>	560 kΩ	100 μF

- (b) The buffer inverts the signal from the RC network.


Select the **other** function of the buffer in this circuit. (Tick (✓) the correct answer.) [1]

- ☐ It acts as a NOT gate.
- ☐ It ensures that the maximum possible current is taken from the RC network.
- ☐ It ensures that the time delay is not affected by the current taken by the load.
- ☐ It reduces the time delay produced by the RC network.

5. A rising-edge triggered D-type flip-flop is used in data transfer.

Complete the graphs to show the Q and  $\bar{Q}$  outputs.

[3]

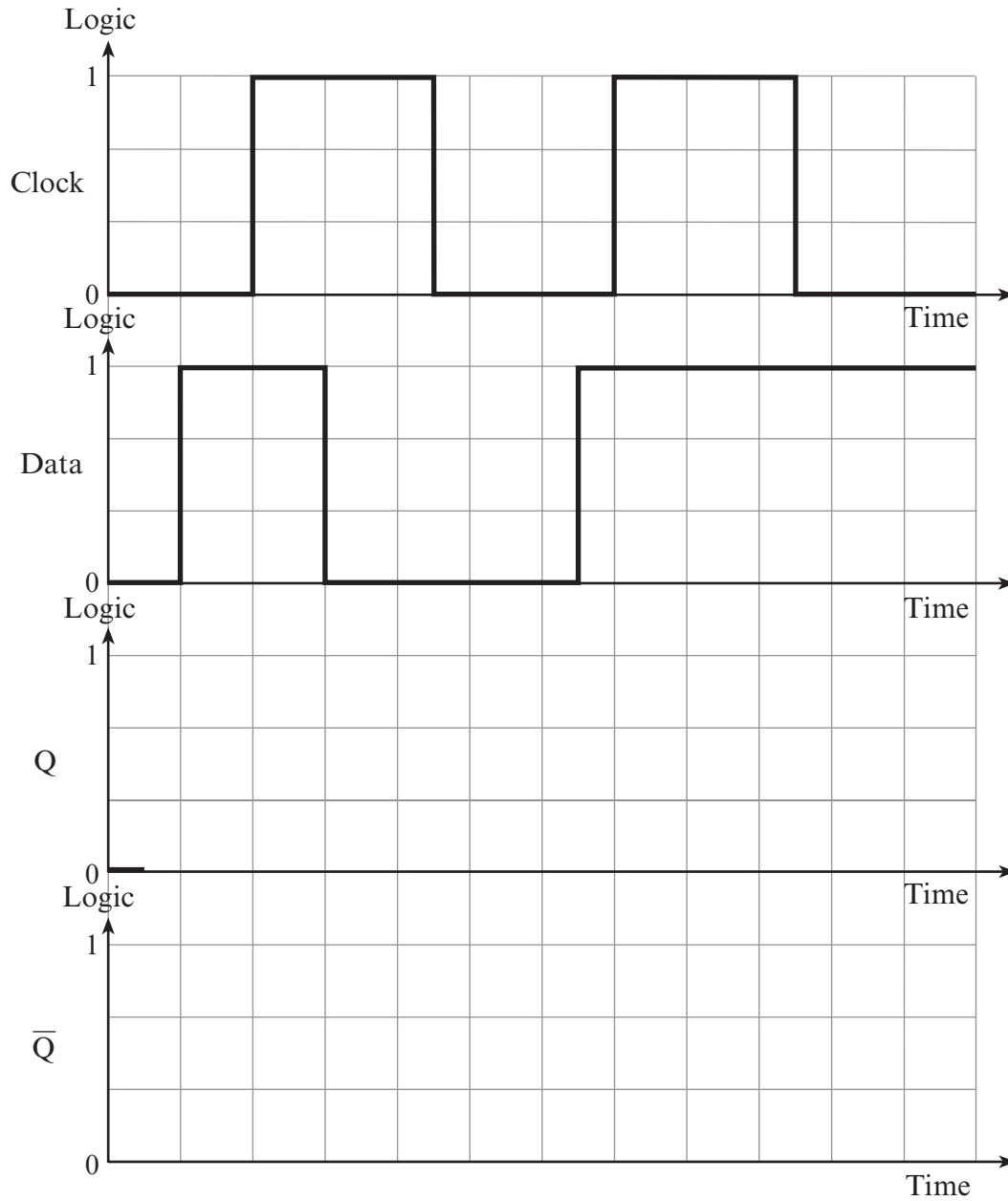







**BLANK PAGE**

 6. A latch sub-system is triggered at time  $T_1$  and reset at time  $T_2$ .

The graphs below show the signal that triggers the latch and the reset signal.




   Select the graph that shows the behaviour of the Q output of the latch during this period. [1]  
(Tick (✓) the correct answer.)



 7. A D-type flip-flop will be set up as a one-bit counter.

Part of the circuit diagram is shown opposite:




Select the **two** connections needed to complete the one-bit counter.  
(Tick (✓) the correct answers.)

[2]

- ☐ The clock input is connected to the pulse source.
- ☐ The data input is connected to the pulse source.
- ☐ The clock input is connected to the Q output.
- ☐ The data input is connected to the Q output.
- ☐ The clock input is connected to the  $\bar{Q}$  output.
- ☐ The data input is connected to the  $\bar{Q}$  output.

 8. Here is the block diagram for a single digit decimal counting system.



(a) Choose the best sub-system for block **X** from the following list:  
(Tick (✓) the correct answer.)

[1]


- ☐ monostable
- ☐ transducer driver
- ☐ latch
- ☐ decoder / driver

(b) Which of the following statements is true about 4-bit BCD counters?  
(Tick (✓) the correct answer.)

[1]

- ☐ The highest decimal number that can be produced is 15.
- ☐ In a decimal counting system, an OR gate must be used to reset it.
- ☐ It cannot be used to count pulses from mechanical switches.
- ☐ The highest binary number that can be produced is 1001.

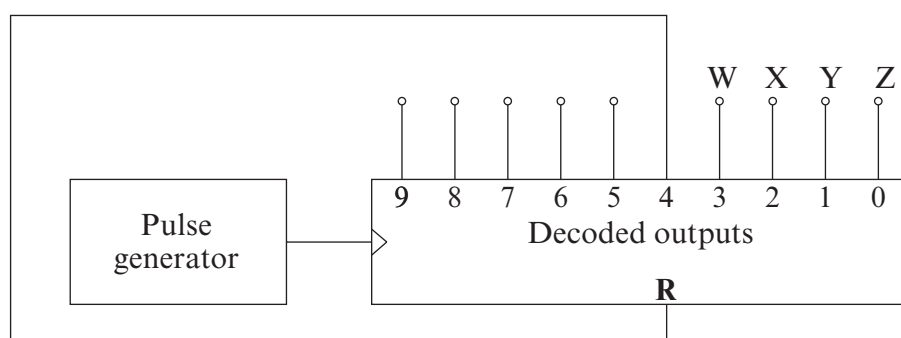9. The diagram shows part of a lighting sequence, controlled by a decade counter. W, X, Y and Z are connected to LEDs.




Reset input **R** is *active-high*, so the counter resets when **R** receives a logic 1 signal.

Complete the table by writing either '**On**' or '**Off**' to show the state of the LEDs as the sequence progresses. [2]

Pulse	LEDs			
	Z	Y	X	W
0	On	Off	Off	Off
1				
2				
3				
4				

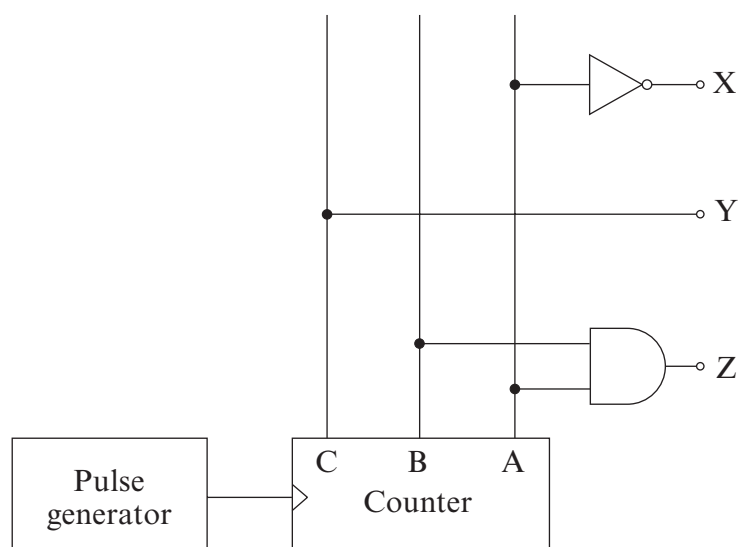10. The circuit diagram shows part of a lighting controller.




Complete the table by adding:

- either “1” or “0” in each box of the X, Y and Z columns; [3]
- either “1” or “0” in the last row of columns C, B and A (for pulse 6). [1]

Pulses from pulse generator	Counter outputs			X	Y	Z
	C	B	A			
0	0	0	0			
1	0	0	1			
2	0	1	0			
3	0	1	1			
4	1	0	0			
5	1	0	1			
6						

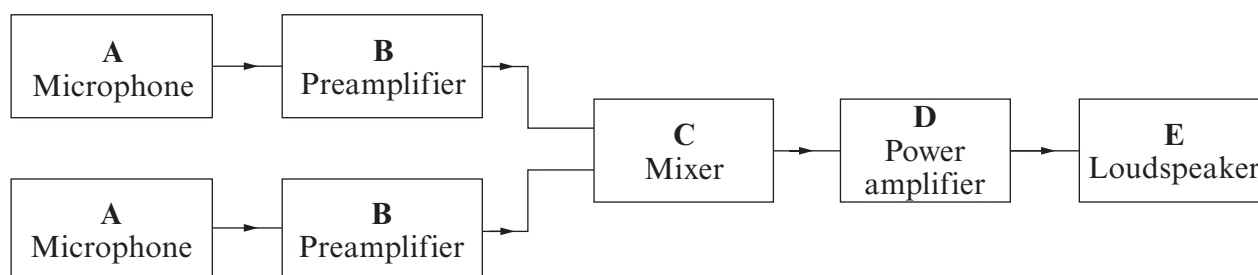11. The block diagram represents a typical amplifier system.  
It uses five different sub-systems, labelled A to E.



Select the blocks designed to:


- (a) boost the current delivered to the sub-system that follows it; [1]

Answer .....

- (b) boost the signal voltage obtained from the previous sub-system. [1]

Answer .....

 12. A voltage amplifier produces an output signal with amplitude 200 mV when the input signal has an amplitude of 10 mV.




- (a) What is the voltage gain of the amplifier? [1]

Answer .....

- (b) Select the pair of resistors that would give the non-inverting amplifier a voltage gain of 12. (Tick (✓) the correct answer.) [1]

	Resistor A	Resistor B
<input type="checkbox"/>	1 k $\Omega$	11 k $\Omega$
<input type="checkbox"/>	11 k $\Omega$	1 k $\Omega$
<input type="checkbox"/>	12 k $\Omega$	1 k $\Omega$
<input type="checkbox"/>	1 k $\Omega$	12 k $\Omega$


 


13. A non-inverting amplifier has a voltage gain of 8.

The upper graph shows the signal applied to the input of the amplifier.


Draw the corresponding output signal.

[1]

  



14.

 

For the signal shown, what is:

(a) the amplitude? (Tick (✓) the correct answer.)

[1]

☐ 10 V

☐ 5 V

☐ 5 s

☐ 10 s

(b) the period? (Tick (✓) the correct answer.)

[1]

☐ 10 V

☐ 5 V

☐ 5 s


☐ 10 s

(c) the frequency?

[1]

**Answer** ..... Hz

 15. A motor-driven paddle is used to mix paint. The valves are normally closed. Liquids enter through inlet valves **A** and **B**, and are mixed before leaving through outlet valve **O**. The system is controlled by data stored in a memory IC. The valves and motor operate on a logic 1 signal. The data stored in part of the memory is given below.



A2	A1	A0	D3	D2	D1	D0
0	0	0	0	0	1	0
0	0	1	1	1	1	0
0	1	0	0	1	1	0
0	1	1	0	0	0	0
1	0	0	0	0	1	1
1	0	1	0	0	0	1
1	1	0	0	0	1	1
1	1	1	Reset			

- (a) The counter is reset before each mixing cycle. Describe the stages of the process between counter reset and the outlet valve opening. (*No timing information is needed.*) [2]

.....

.....

.....

.....


- (b) The pulse generator outputs pulses with a period of 2 s.  
For how long is the outlet valve open in each mixing cycle? [1]

**Answer** ..... s

- (c) The memory IC used for this task has three address bits.  
How many address locations are there in this memory IC? [1]

**Answer** .....

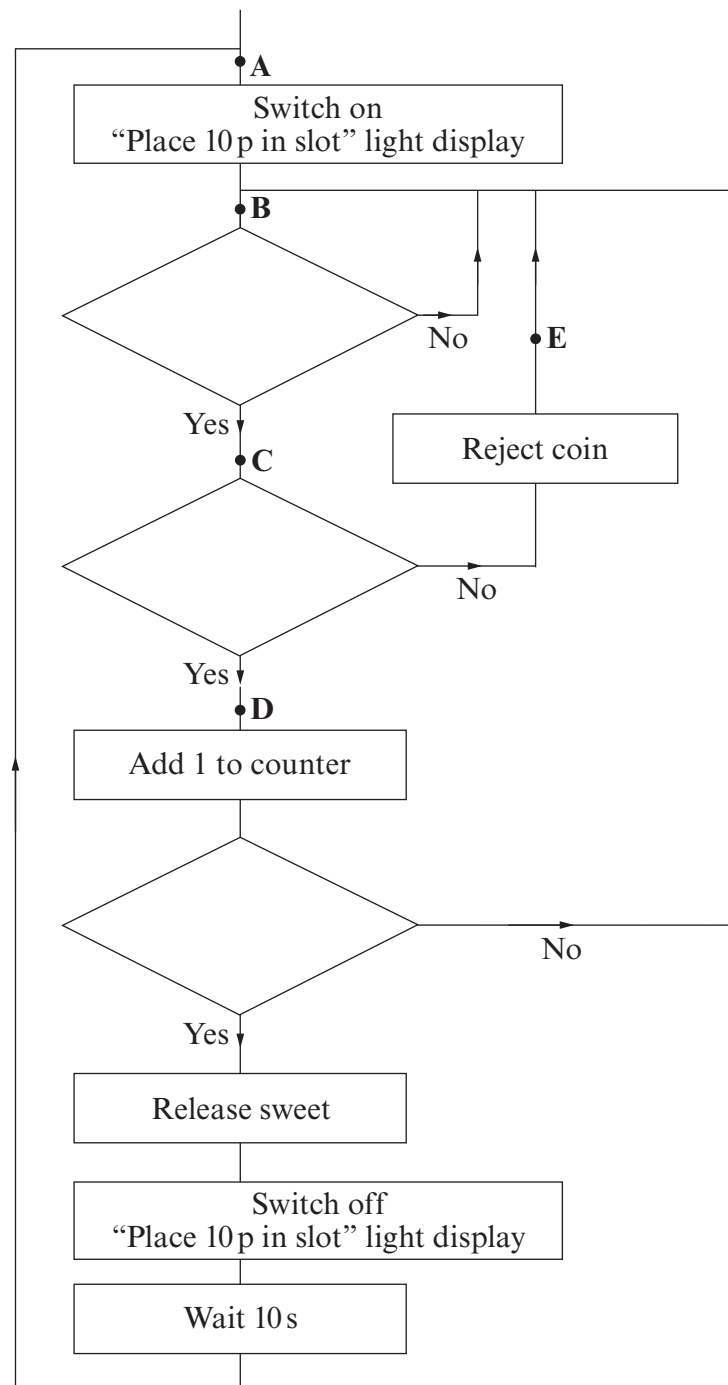16. Here is part of the flowchart for a dispensing machine for sweets.



(a) Add the following labels to the correct boxes:

- “Is it 10 p?”
- “Counter = 5?”
- “Coin detected?”

[3]

(b) How much does a sweet cost?

[1]

**Answer** ..... p

(c) At which point in the flowchart, **A**, **B**, **C**, **D** or **E**, should the instruction “Reset the counter” be added?

[1]

**Answer** .....

17. (a) A comparator can be used as an interface between a light sensor and a digital system. Here are four statements about the comparator used in this way. Select the correct **one**. (Tick (✓) the correct answer.) [1]

- ☐ It has a single switching threshold fixed at 0.7V.
- ☐ It has a single switching threshold at a voltage which can be varied.
- ☐ It has two fixed switching thresholds.
- ☐ It has two switching thresholds at voltages which can be varied.

- (b) Usually, it is better to use a Schmitt inverter. Which statement gives the benefit of the Schmitt inverter over the comparator in this application? (Tick (✓) the correct answer.) [1]

- ☐ It stops contact bounce in the light sensor.
- ☐ It stops rapid output switching when the light level fluctuates slightly.
- ☐ It improves the rise-time of the signal.
- ☐ It boosts the current to the output device.

18. In a 555 monostable circuit, the time delay  $T$  is given by the formula:

$$T = 1.1 RC$$

Calculate the time delay produced when:

$$R = 1 \text{ M}\Omega.$$

$$C = 10 \text{ }\mu\text{F}.$$


[1]

.....

.....

**Answer** ..... s

 19. Here is an incomplete circuit diagram for a latch.



(a) The D-input must be connected to:


- ☐ the clock input;
- ☐ the  $\bar{Q}$  output;
- ☐ the 12V power rail;
- ☐ the 0V power rail.

[1]

(b) The latch resets when pin R receives a logic 1 signal.

Which **two** switch units will reset the latch when the switch is pressed?  
(Tick (✓) the correct answers.)

[2]

 


20. A *rising-edge triggered* 2-bit up counter is connected to a pulse generator. Output A is the least-significant bit (LSB). Initially, it is reset.

The top graph shows the pulses received from the pulse generator.

Draw the resulting signals at the outputs.

[3]

 



21. The following data sheet provides information about a Schmitt Inverter:


When connected to a 5V power supply:

- Logic 0 = 0V
- Logic 1 = 5V
- The output changes from logic 1 to logic 0 when a **rising** input voltage reaches 3V
- The output changes from logic 0 to logic 1 when a **falling** input voltage reaches 1V


An engineer tests it by applying the signal shown in the upper graph to the input.

Draw the expected output signal.

[4]

 

 22. The circuit diagram for the interface to a bulb is shown below.



- (a) The signal from the logic gate switches from 0.5V (logic 0) to 8.0V (logic 1).

Complete the table to show the corresponding values of voltage  $V_1$ .

[2]

Logic gate output	$V_1$
0.5V	..... V
8.0V	..... V

- (b) The bulb in the lamp unit is rated at 12V, 100mA.

The transistor has a current gain ( $h_{FE}$ ) of 50.

Calculate the base current when the transistor is just saturated.

[1]

**Answer** ..... mA


23. The output signal of an amplifier is clipped.

What is the reason for this? (Tick (✓) the correct answer.)

[1]

- ☐ The amplitude of the input signal is too big for the power supply.
- ☐ The frequency of the output signal exceeds the bandwidth of the amplifier.
- ☐ The voltage gain formula does not apply to digital signals.
- ☐ The output signal is not inverted.

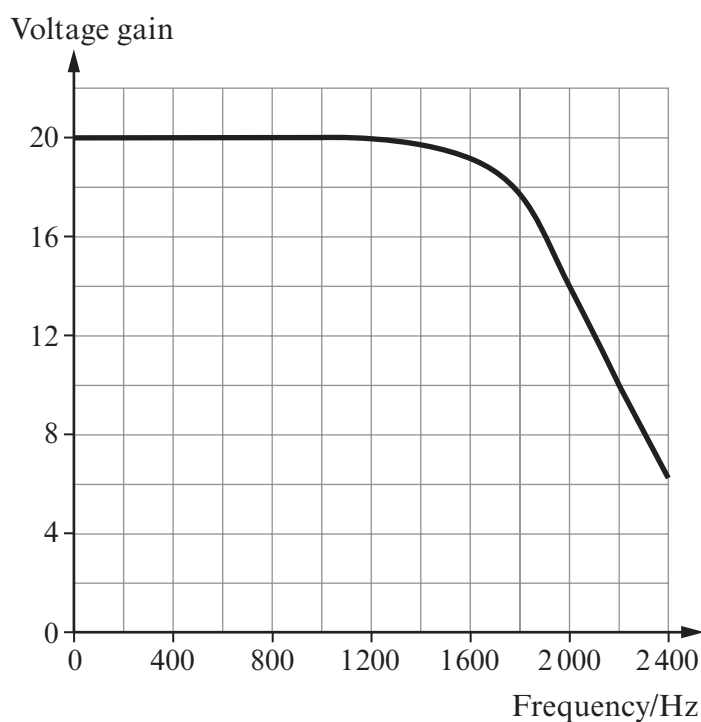24. The graph shows the effect of changing the signal frequency on an amplifier's voltage gain.



What is the bandwidth of the amplifier? (Tick (✓) the correct answer.)

[1]

- ☐ 1 000 Hz
- ☐ 2 000 Hz
- ☐ 2 200 Hz
- ☐ 2 400 Hz


**TURN OVER FOR THE LAST QUESTION**

25. Audio mixers are used to combine signals from a number of different sources.

The mixer in the diagram is tested by applying the following signals.

Input A = 1.0V

Input B = 2.0V

 

(a) Which **one** of the following shows the correct formula and values to calculate the output voltage? (Tick (✓) the correct answer.) [1]

☐  $V_{\text{OUT}} = -20\left(\frac{1}{10} + \frac{2}{5}\right)$

☐  $V_{\text{OUT}} = -10\left(\frac{1}{20} + \frac{2}{5}\right)$

☐  $V_{\text{OUT}} = -5\left(\frac{1}{20} + \frac{2}{10}\right)$

☐  $V_{\text{OUT}} = -5\left(\frac{1}{10} + \frac{2}{20}\right)$

(b) Calculate the output voltage.

[1]

.....

.....

Answer ..... V

**END OF PAPER**