

Surname	Centre Number	Candidate Number
Other Names		0



GCSE

4161/01



ELECTRONICS

UNIT E1: Paper replacement test

TUESDAY, 13 JUNE 2017 – AFTERNOON

1 hour

For Examiner's use only		
Question	Maximum Mark	Mark Awarded
1.	6	
2.	4	
3.	4	
4.	2	
5.	3	
6.	3	
7.	2	
8.	4	
9.	5	
10.	2	
11.	3	
12.	2	
13.	3	
14.	2	
15.	3	
16.	3	
17.	5	
18.	4	
Total	60	

ADDITIONAL MATERIALS

In addition to this paper you may require a calculator and a ruler.

INSTRUCTIONS TO CANDIDATES

Use black ink or black ball-point pen.

Write your name, centre number and candidate number in the spaces at the top of this page.

Answer **all** questions in the spaces provided in this booklet.

INFORMATION FOR CANDIDATES

The number of marks is given in brackets at the end of each question or part-question.

INFORMATION SHEET FOR UNIT E1

This information may be of use in answering the questions.

1. Resistor Colour Codes

BLACK	0	GREEN	5
BROWN	1	BLUE	6
RED	2	VIOLET	7
ORANGE	3	GREY	8
YELLOW	4	WHITE	9

The fourth band colour gives the tolerance as follows:

GOLD \pm 5%

SILVER \pm 10%

2. Preferred Values for Resistors – E24 series


10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91.

3. **Resistance** = $\frac{\text{voltage}}{\text{current}}$; $R = \frac{V}{I}$.

4. **Effective resistance**, R , of two resistors R_1 and R_2 in series is given by $R = R_1 + R_2$.

5. **Effective resistance**, R , of two resistors R_1 and R_2 in parallel is given by $R = \frac{R_1 R_2}{R_1 + R_2}$.

6. Voltage Divider

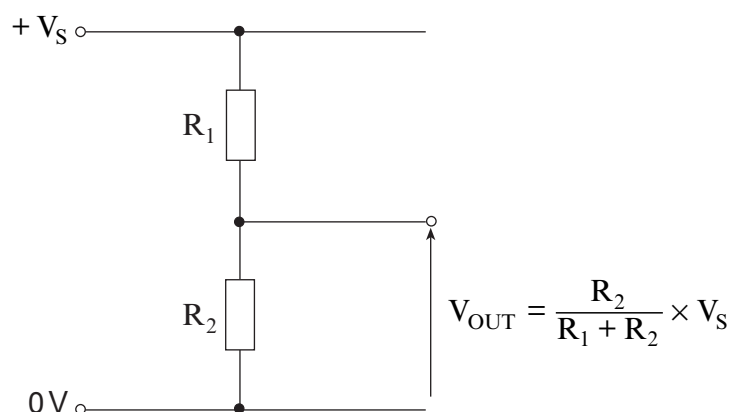

7. **Power** = voltage \times current; $P = VI = I^2 R = \frac{V^2}{R}$.

8. **LED** The forward voltage drop across a LED is 2V.

9. **NPN Transistors** (i) Current gain = $\frac{\text{Collector current}}{\text{Base current}}$; $h_{FE} = \frac{I_C}{I_B}$.

(ii) The forward voltage drop across the base emitter junction is 0.7 V.


Answer **all** questions.


1. (a) Here is a list of electronic components.

Resistor Lamp Push-to-make switch Thyristor
Push-to-break switch LED Buzzer

Complete each box with the correct name for **each** component.

[3]

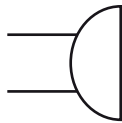

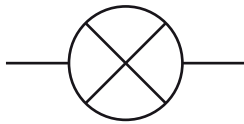



- (b) The following is a list of different electronic sub-systems.


NOT gate Latch unit Sound sensing unit Delay unit Pulse generator
Magnetic switch unit Motor unit Lamp unit Comparator

Write each sub-system into the correct column in the table below.

[3]

Input sub-system	Processing sub-system	Output sub-system

2. Study the following circuit.

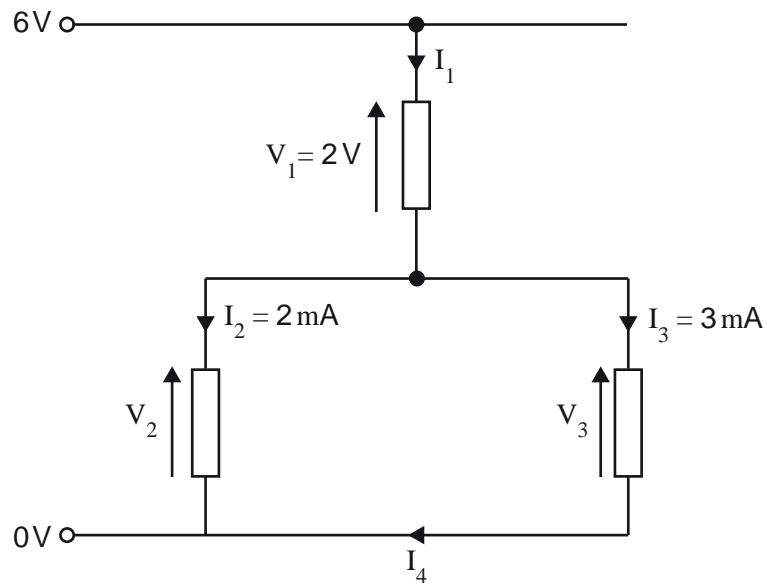


Select the correct answers to the following questions.

0	1	2	3	4	5	6	7	8	9	10	11	12	13
---	---	---	---	---	---	---	---	---	---	----	----	----	----

- (a) What is the value of V_2 ? V [1]
- (b) What is the value of I_1 ? mA [1]
- (c) What is the value of V_3 ? V [1]
- (d) What is the value of I_4 ? mA [1]

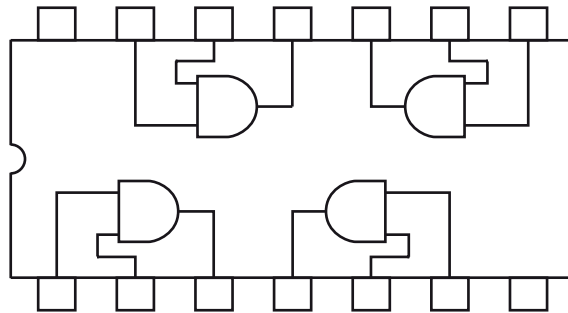3. Here is the pinout for a logic gate IC.




On the diagram write:

- (a) the letter 'Q' on all output pins; [1]
- (b) the symbol '+' on the positive supply pin; [1]
- (c) the number '9' on pin 9. [1]
- (d) What type of logic gate is shown in the diagram? [1]

4161
010005



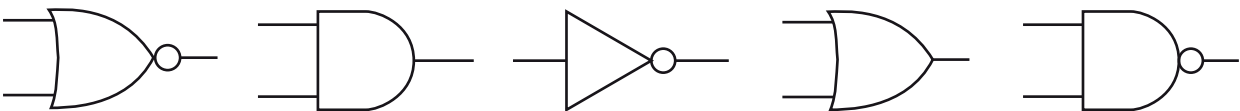
4. Draw the correct logic gate to match the name in the table below. [2]



Logic gate name	Symbol
NOR gate	
NOT gate	




5. (a) The following diagram shows the circuit symbol for a transistor.
(Tick (✓) the correctly labelled symbol.)

[1]

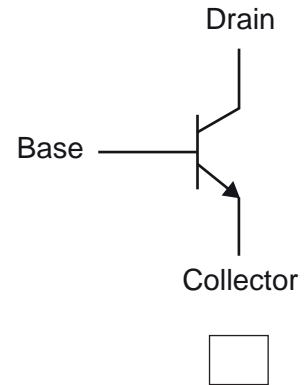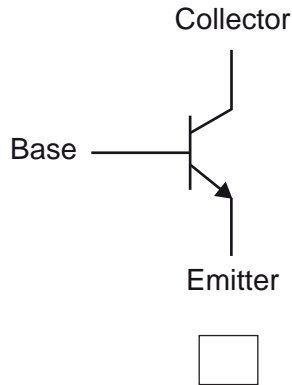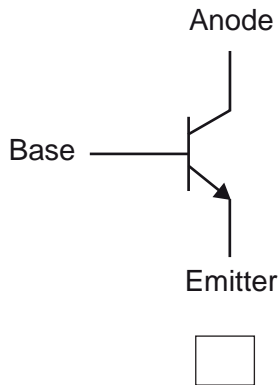




- (b) The following diagram shows the circuit symbol for a MOSFET.
(Tick (✓) the correctly labelled symbol.)

[1]

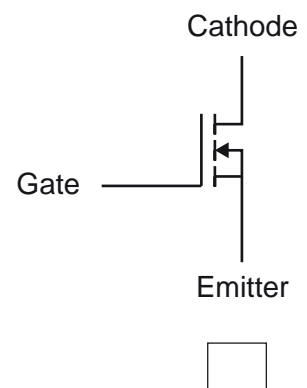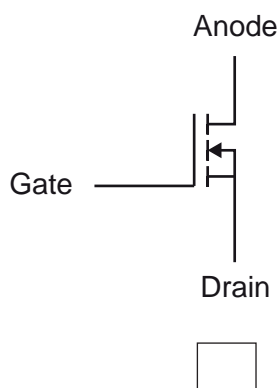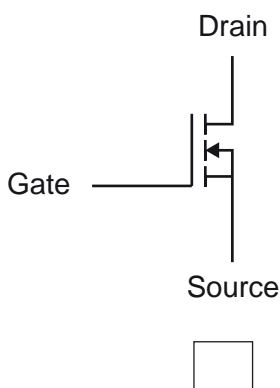


- (c) The following diagram shows the circuit symbol for a thyristor.
(Tick (✓) the correctly labelled symbol.)

[1]

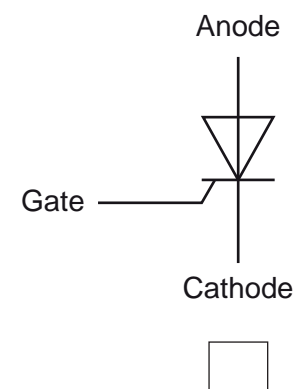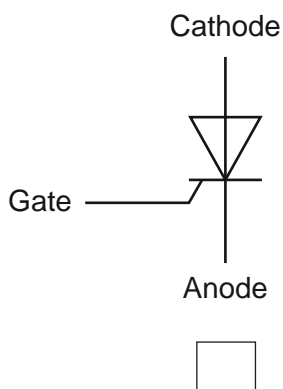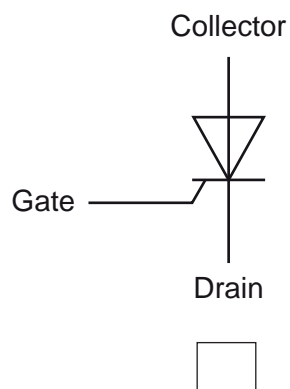

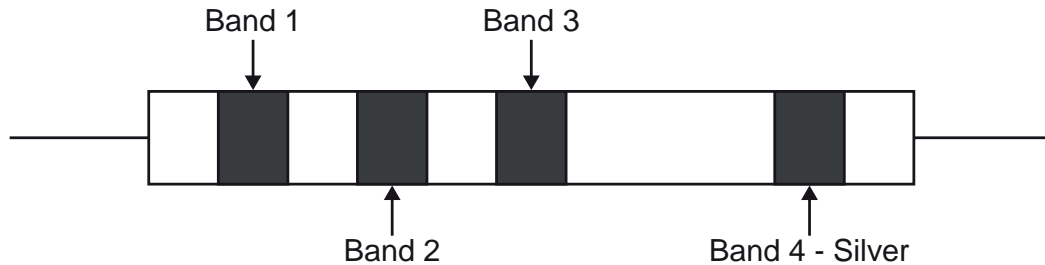6. The diagram shows a $56\Omega \pm 10\%$ resistor.




Write down the correct colour of bands 1, 2 and 3 present on this resistor.

[3]

Band 1 Band 2 Band 3

7. The diagram shows a motor.

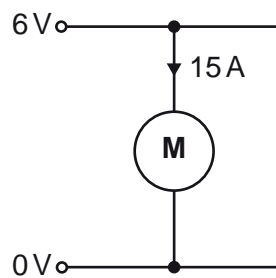

- (a) Select the correct equation to calculate the power used in the motor in watts (W). (Tick (✓) the correct answer.)

[1]

☐ $P = \frac{6}{15}$

☐ $P = \frac{15}{6}$

☐ $P = 6 \times 1500$

☐ $P = 6 \times 15$

☐ $P = \frac{6}{1.5}$


☐ $P = \frac{15000}{6}$

- (b) Calculate the power used in the motor.

[1]

..... W

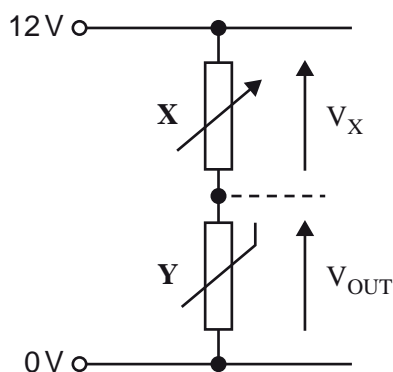8. Here is an analogue sensing circuit at room temperature.



(a) Circle the name of the component labelled X. [1]

LDR Resistor Thermistor Variable resistor

(b) $V_{OUT} = 3V$. Circle the correct voltage across the component X. [1]

0V 1V 2V 3V 4V 5V 6V 7V 8V 9V 10V 11V 12V

(c) (i) What would happen to the resistance of component Y if an ice cube was placed on top of it? (Tick (✓) the correct answer.) [1]

☐

The resistance of component Y would increase

☐

The resistance of component Y would stay the same

☐

The resistance of component Y would decrease

☐

The resistance of component Y will halve

(ii) What effect would this have on the output voltage V_{OUT} ? (Tick (✓) the correct answer.) [1]

☐

V_{OUT} would increase

☐

V_{OUT} would decrease

☐

V_{OUT} would stay the same

☐

V_{OUT} would become 0V

9. A luxury car has heated front seats for both the driver and front passenger.

The driver's seat heater will only operate if:

- the driver is sitting on the driver's seat
- the engine ignition is switched on
- the outside temperature is below a set temperature.


The passenger's seat heater will only operate if:

- there is someone sitting in the driver's seat
- the engine ignition is switched on
- the outside temperature is below a set temperature
- there is someone sitting in the passenger seat.

A number of sensing sub-systems are available for use, with the following specifications:

- a light sensor that outputs a Logic 1 when in daylight and Logic 0 when it is dark
- a temperature sensor that outputs a Logic 1 when it is cold and Logic 0 when it is warm
- a pressure sensor that outputs Logic 0 when it is not under pressure and Logic 1 when it is under pressure
- a moisture sensor that outputs a Logic 0 when wet and Logic 1 when dry.

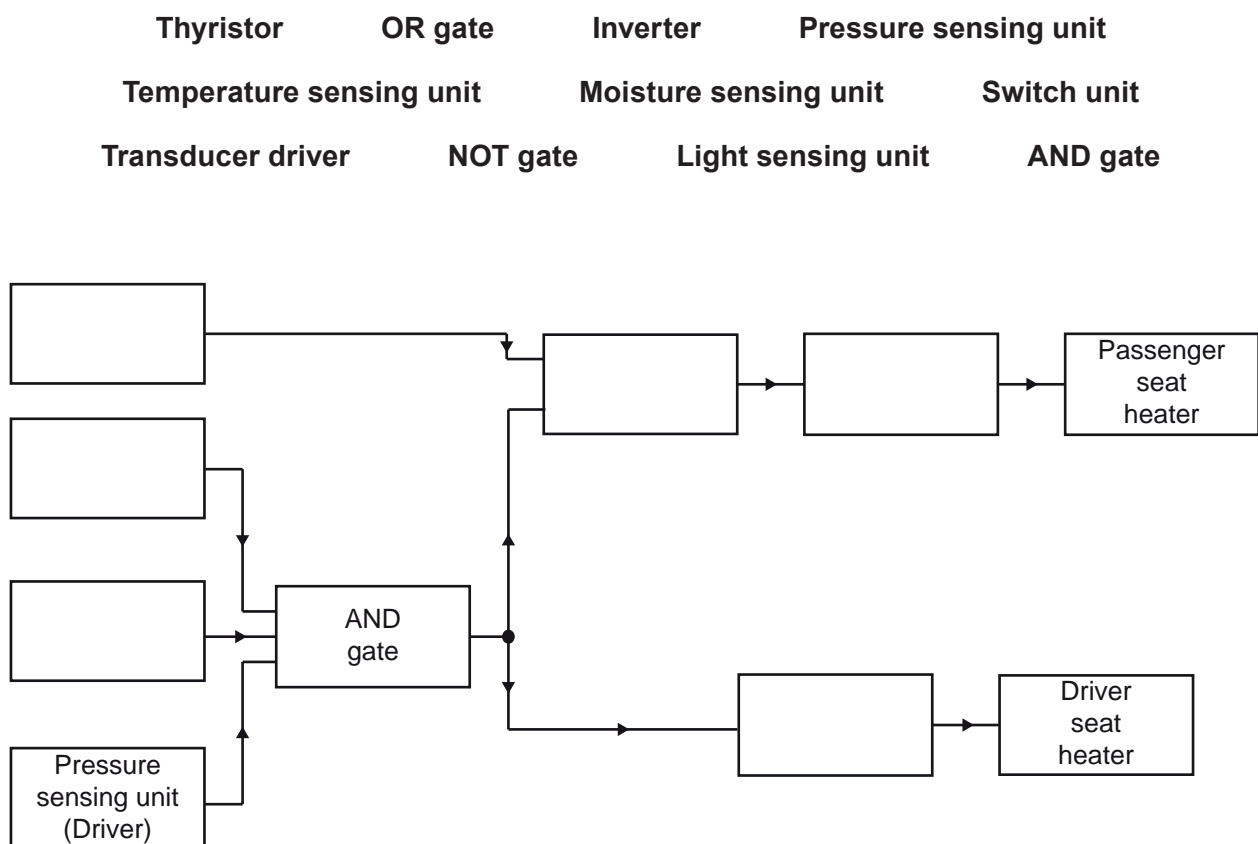Complete the block diagram for the car seat heating system using the information about each type of sensor above and the other sub-systems in the list below: [5]



10. (a) Circle the logic gate that has the following truth table.

[1]

Inputs		Output
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

AND gate NAND gate NOR gate NOT gate OR gate

- (b) Circle the logic gate that outputs a logic 1 signal **only** when both inputs are at logic 1.

[1]



AND gate NAND gate NOR gate NOT gate OR gate

11. A logic system has the following truth table.

Inputs		Outputs		
A	B	X	Y	Q
0	0	0	1	1
0	1	0	0	0
1	0	1	1	1
1	1	1	0	1


Draw the correct logic gates / connections to the following circuit to produce the truth table given above.

[3]

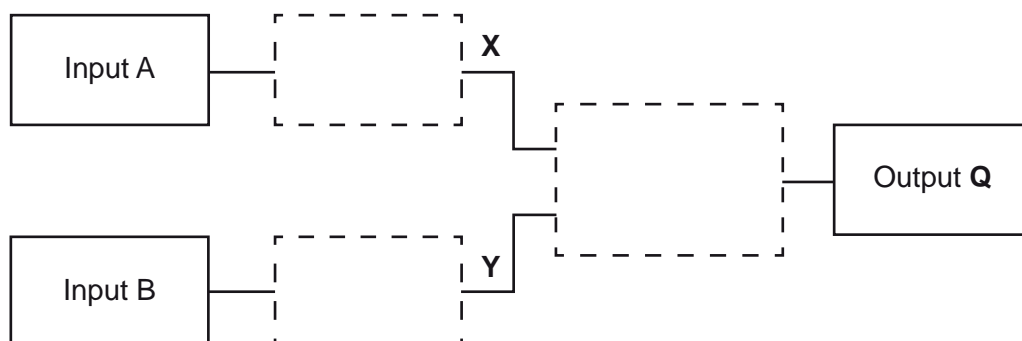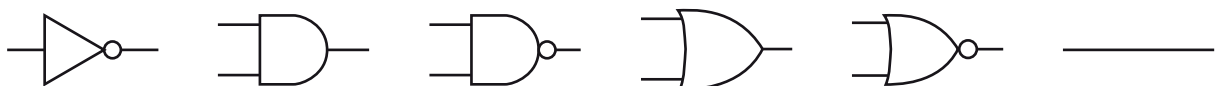

12. The logic circuit below contains some NAND gates that are redundant. Circle all the redundant NAND gates.


[2]

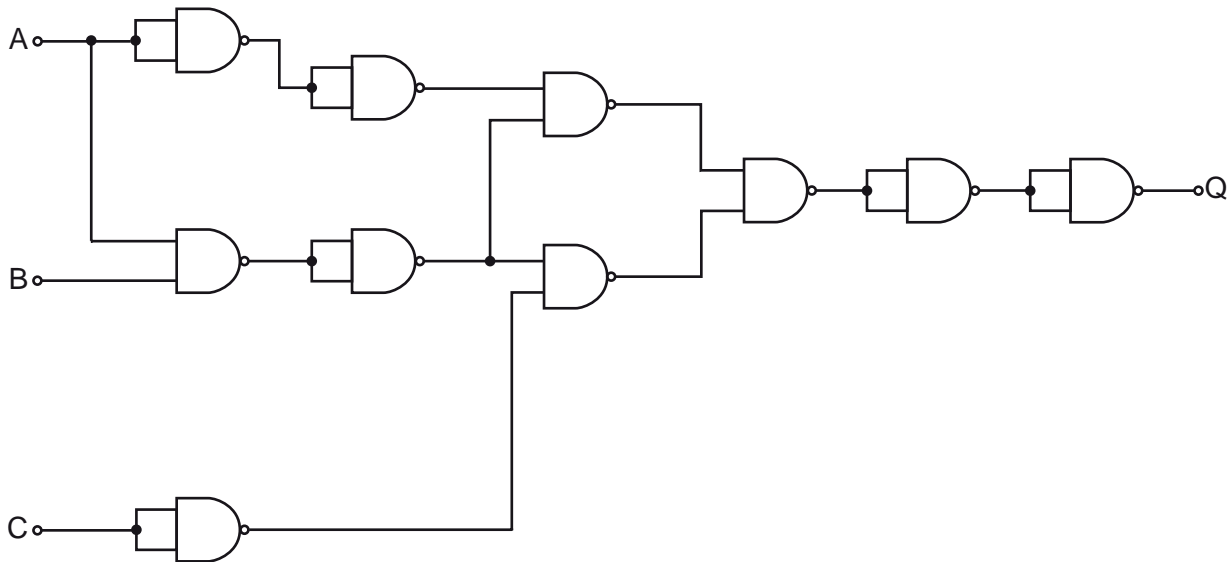

13. The diagrams below show three different combinations of resistors.

Calculate the effective resistance of each combination in $k\Omega$.

[3]

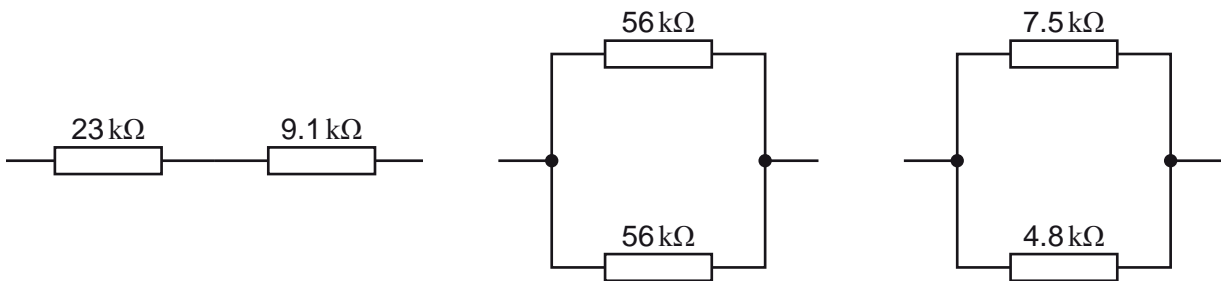

.....

.....

.....

.....

.....

.....

.....

.....

.....

..... $k\Omega$ $k\Omega$ $k\Omega$

14. Select the correct truth table that represents the function described by each Boolean equation. (Tick (✓) the correct answer.)

(a) $Q = A \cdot \bar{B}$

[1]

Inputs		Output
A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

☐

Inputs		Output
A	B	Q
0	0	1
0	1	0
1	0	1
1	1	0

☐

Inputs		Output
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

☐

Inputs		Output
A	B	Q
0	0	0
0	1	0
1	0	1
1	1	0

☐

(b) $Q = \bar{A} + B$

[1]

Inputs		Output
A	B	Q
0	0	0
0	1	1
1	0	0
1	1	1

☐

Inputs		Output
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

☐


Inputs		Output
A	B	Q
0	0	1
0	1	1
1	0	0
1	1	1

☐

Inputs		Output
A	B	Q
0	0	1
0	1	0
1	0	1
1	1	0

☐

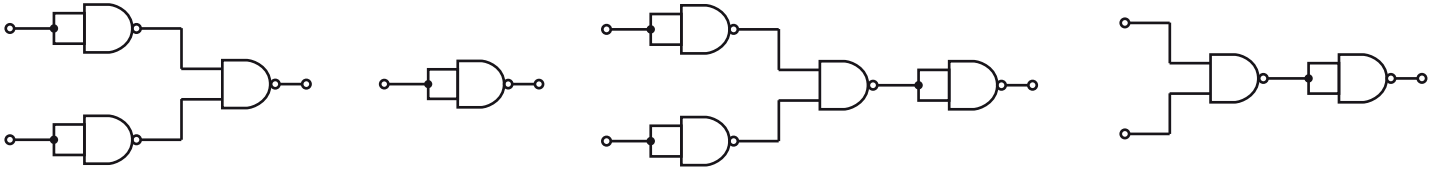15. The following show the NAND equivalent circuits for a number of standard gates.



Draw the NAND equivalent circuit to match the standard gate given below.

[3]

Standard gate

NAND equivalent circuit


NOR gate

AND gate

NOT gate

16. The following circuit is **part of** a larger electronic system.

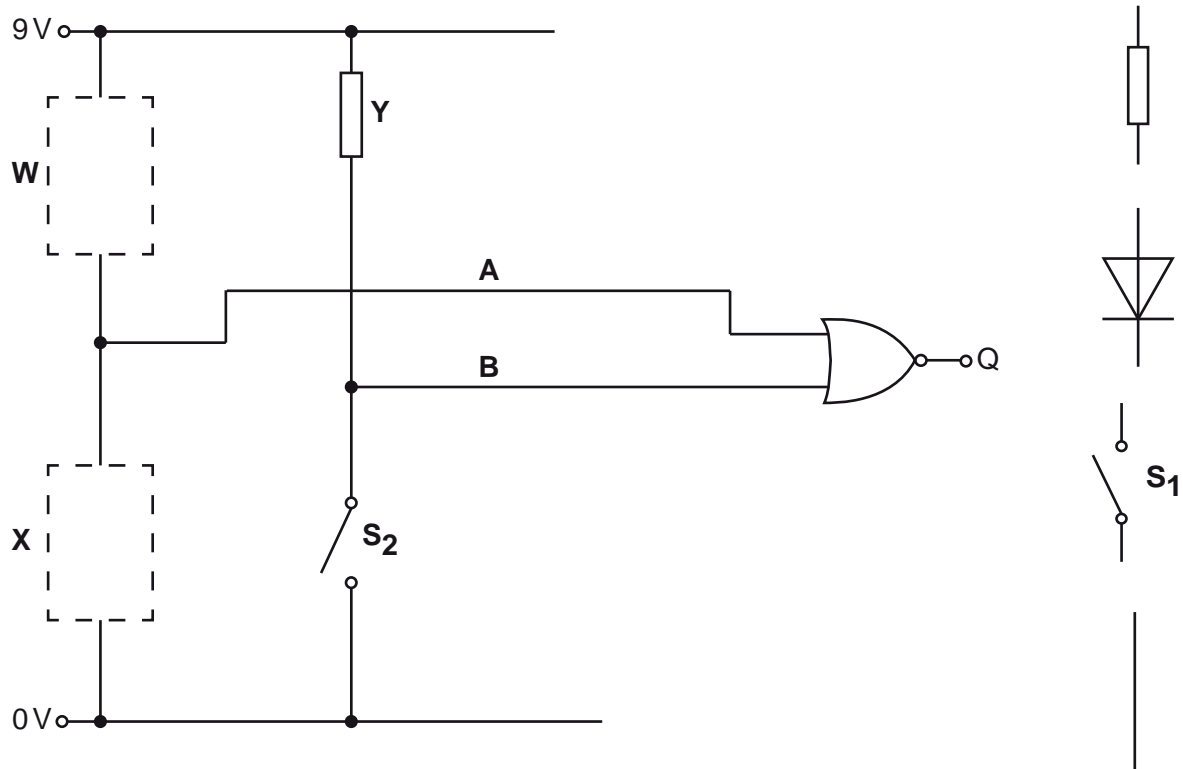- (a) Input A of the logic system needs to be at logic 1 when switch S_1 is pressed. Draw the correct components in boxes W and X. [1]



- (b) What is the purpose of the component labelled 'Y' in the circuit above? [1]

.....

.....


.....

- (c) What combination(s) of switch settings produce a logic 1 output Q from the circuit. (Tick (✓) all that apply.) [1]

- ☐ S_1 open & S_2 open
- ☐ S_1 closed & S_2 open
- ☐ S_1 open & S_2 closed
- ☐ S_1 closed & S_2 closed

BLANK PAGE

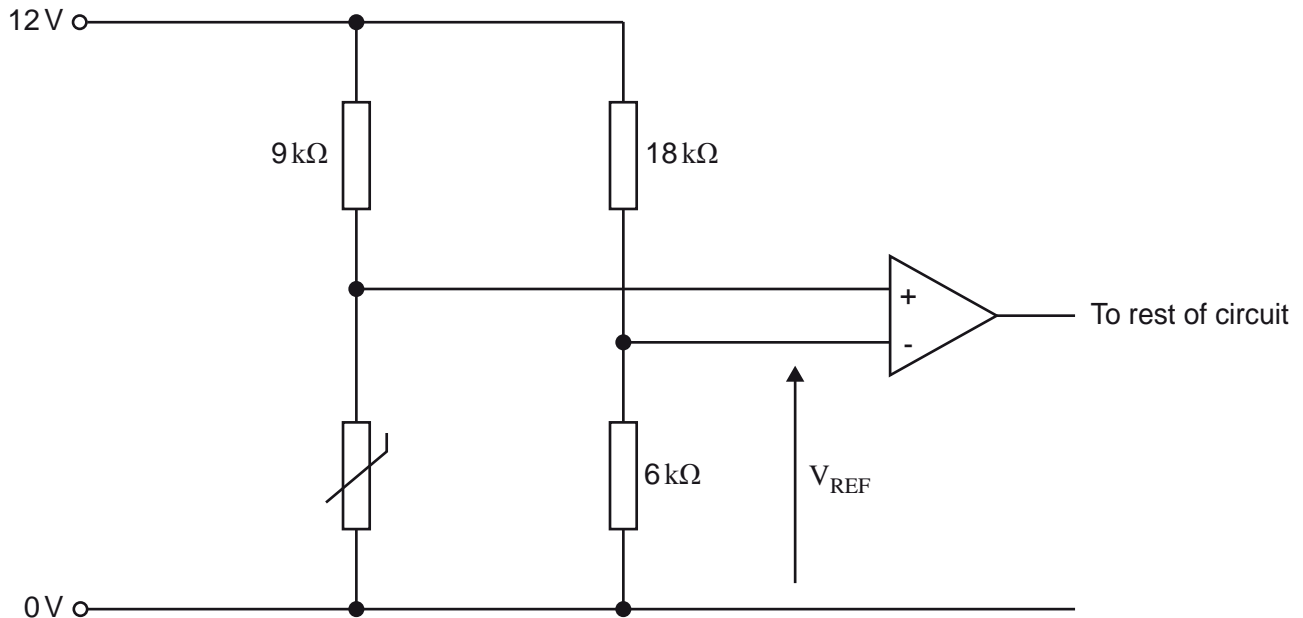17. The following **incomplete** circuit diagram shows a comparator used to switch on a greenhouse heater when the temperature gets too cold.



- (a) Select the correct equation to calculate the voltage V_{REF} .
(Tick (✓) the correct answer.)

[1]

☐ $V_{REF} = \frac{9}{18+6} \times 12$

☐ $V_{REF} = \frac{6}{18+9} \times 12$

☐ $V_{REF} = \frac{6}{6+18} \times 12$

☐ $V_{REF} = \frac{18}{6+18} \times 12$



- (b) Calculate the voltage V_{REF} at the inverting input.

[1]

..... V

- (c) Complete the circuit diagram below to make a non-latching output circuit for the comparator using the components shown below. [2]

Examiner only

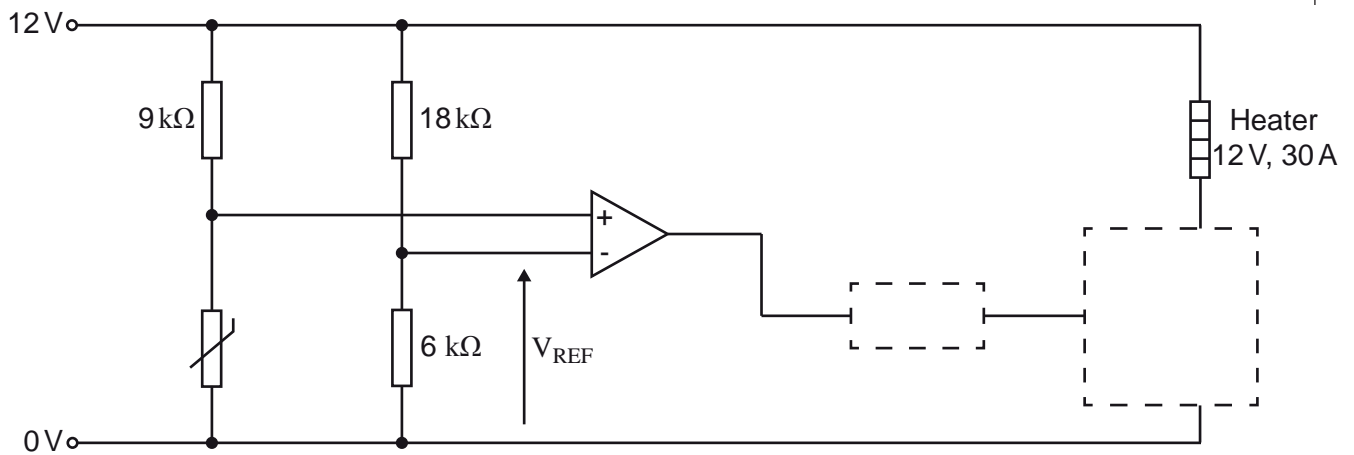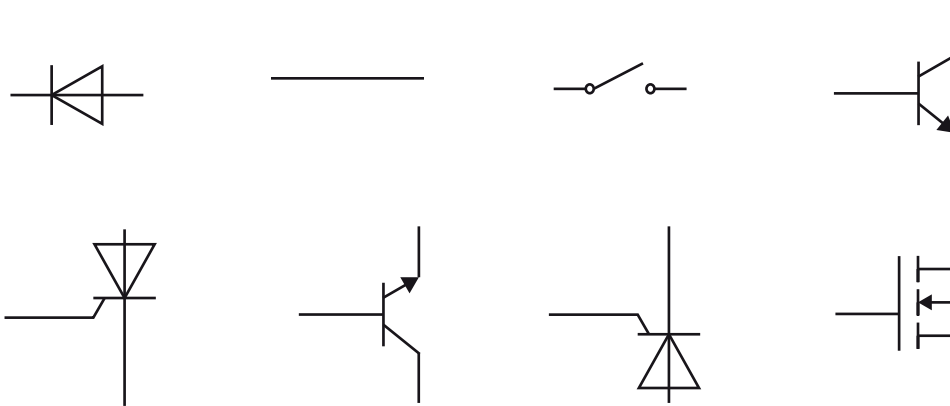


- (d) What modification could be made to the circuit so that the temperature that the heater switches on could be changed? [1]

.....

.....

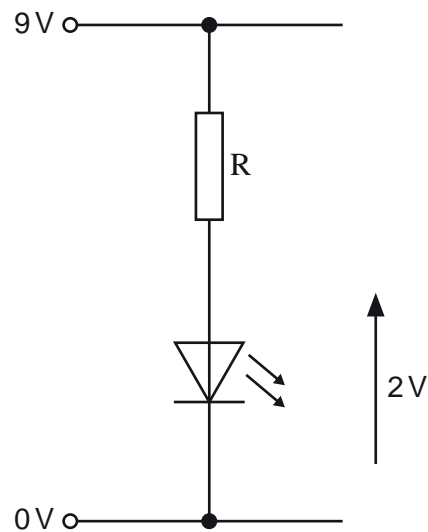18. A high power LED is to be used as a power on indicator as shown below.



(a) What is the voltage drop across the resistor R?

[1]

..... V

(b) Select the correct equation to calculate the ideal resistance of resistor R (in $k\Omega$) to provide a current of 25 mA through the LED.
(Tick (✓) the correct answer.)

[1]

☐ $R = 9 \times 25$

☐ $R = \frac{2}{25}$

☐ $R = \frac{7}{25}$

☐ $R = 7 \times 25$

☐ $R = 9 \times 2$

☐ $R = \frac{9}{25}$

☐ $R = \frac{9}{2}$

☐ $R = 9 \times 23$

(c) What is the ideal resistance of resistor R? $k\Omega$

[1]

(d) Use the E24 resistor series on the information sheet to select the preferred value for resistor R **in ohms** to ensure that the current through the LED is just **less** than 25 mA.

[1]

..... Ω

END OF PAPER

BLANK PAGE