

Surname	Centre Number	Candidate Number
Other Names		0



GCSE

4162/01



S17-4162-01

ELECTRONICS

UNIT E2: Paper replacement test

MONDAY, 19 JUNE 2017 – AFTERNOON

1 hour

For Examiner's use only		
Question	Maximum Mark	Mark Awarded
1.	2	
2.	4	
3.	2	
4.	2	
5.	5	
6.	3	
7.	6	
8.	5	
9.	3	
10.	2	
11.	5	
12.	3	
13.	6	
14.	6	
15.	6	
Total	60	

ADDITIONAL MATERIALS

In addition to this paper you may require a calculator and a ruler.

INSTRUCTIONS TO CANDIDATES

Use black ink or black ball-point pen.

Write your name, centre number and candidate number in the spaces at the top of this page.

Answer **all** questions in the spaces provided in this booklet.

INFORMATION FOR CANDIDATES

The number of marks is given in brackets at the end of each question or part-question.

INFORMATION SHEET FOR UNIT E2

This information may be of use in answering the questions.

1. Resistor Colour Codes

BLACK	0	GREEN	5
BROWN	1	BLUE	6
RED	2	VIOLET	7
ORANGE	3	GREY	8
YELLOW	4	WHITE	9

The fourth band colour gives the tolerance as follows:

GOLD \pm **5%**

SILVER \pm **10%**

2. Preferred Values for Resistors – E24 series


10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91.

3. **Resistance** = $\frac{\text{voltage}}{\text{current}}$; $R = \frac{V}{I}$.

4. **Effective resistance**, R , of two resistors R_1 and R_2 in series is given by $R = R_1 + R_2$.

5. **Effective resistance**, R , of two resistors R_1 and R_2 in parallel is given by $R = \frac{R_1 R_2}{R_1 + R_2}$.

6. Voltage Divider

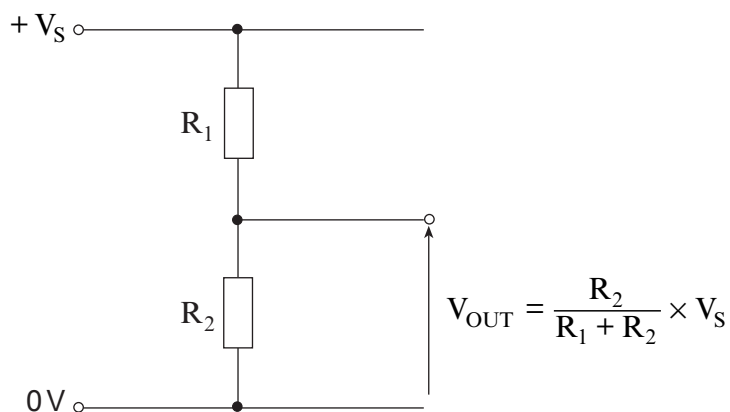

7. **Power** = voltage \times current; $P = VI = I^2 R = \frac{V^2}{R}$.

8. **LED** The forward voltage drop across a LED is 2 V.

9. **NPN Transistors** (i) Current gain = $\frac{\text{Collector current}}{\text{Base current}}$; $h_{FE} = \frac{I_C}{I_B}$.

(ii) The forward voltage drop across the base emitter junction is 0.7 V.

10. Amplifiers

Voltage gain: $A = \frac{V_{OUT}}{V_{IN}}$


Non-inverting amplifier: $A = 1 + \frac{R_F}{R_1}$

Inverting amplifier: $A = -\frac{R_F}{R_{IN}}$

Summing amplifier: $V_{OUT} = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots \right)$

Answer **all** questions.

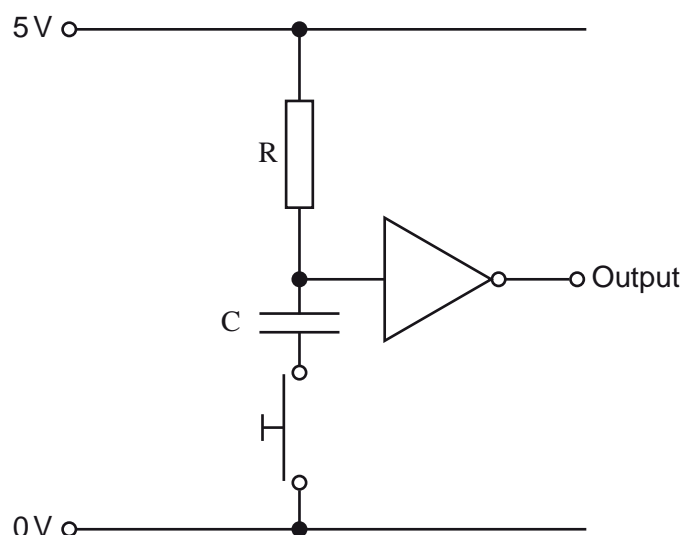1. The diagram shows a capacitor-resistor network, which can be used to produce a time delay.



- (a) Which **one** of the following would **increase** this time delay?
(Tick (✓) the correct answer.)

[1]


- ☐ Double the value of R and keep the value of C unchanged
- ☐ Double the value of R and halve the value of C
- ☐ Double the value of C and halve the value of R
- ☐ Halve the value of R and keep the value of C unchanged
- ☐ Halve the value of C and keep the value of R unchanged

- (b) Why is a NOT gate included in this circuit?
(Tick (✓) the correct answer.)

[1]

- ☐ It reduces the time delay
- ☐ It increases the current taken from the capacitor-resistor network
- ☐ It keeps the time delay unchanged when current flows from the output
- ☐ It produces a low voltage at the output when the switch is pressed




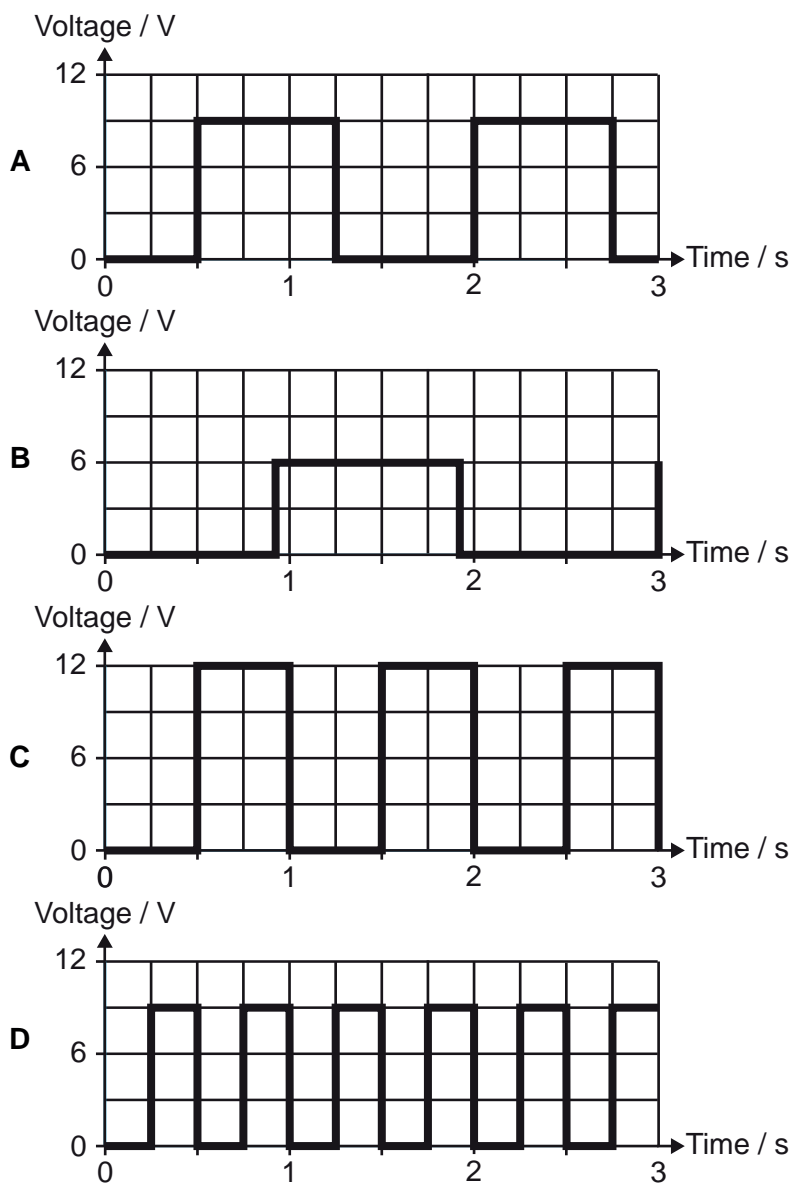
2. (a) Here are four signals produced by astable circuits.



- (i) Which has the longest period? [1]
- (ii) Which has a period of 1 s? [1]
- (iii) Which has an amplitude of 6 V? [1]


- (b) Which of the following is the circuit diagram for a 555 monostable circuit?
(Tick (✓) the correct answer.)

[1]

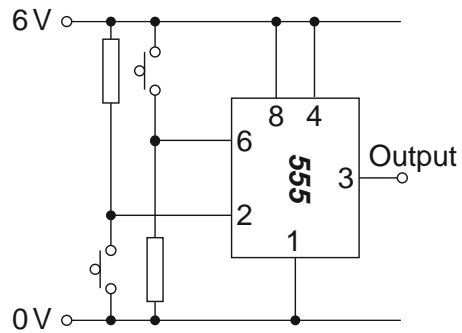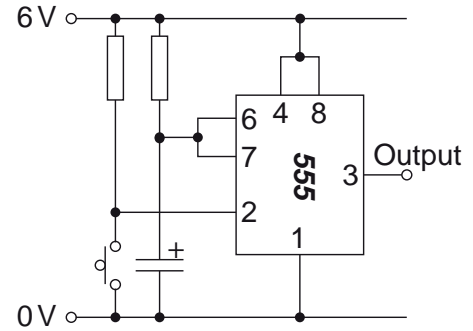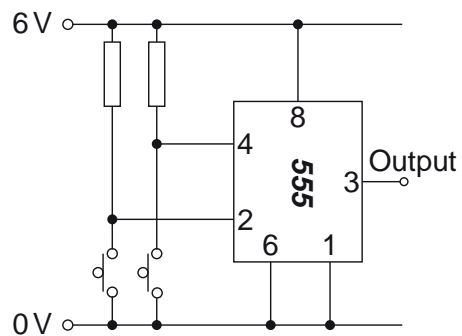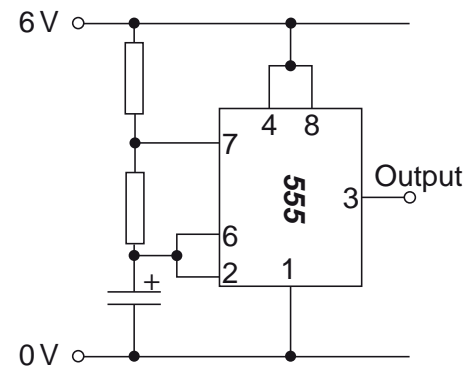
☐

☐

☐

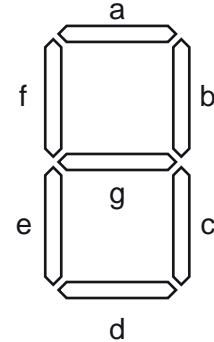☐

3. (a) The segments of a 7-segment display light when they receive logic 1 signals. By adding a '0' or '1' in each box complete the truth table so that the 7-segment display shows the letter 'F'. [1]

Segments							Character
a	b	c	d	e	f	g	
							F



- (b) The display changes to show the number '3'. Which truth table shows the signals controlling it? (Tick (✓) the correct answer.) [1]

☐

a	b	c	d	e	f	g
1	0	0	1	1	1	1

☐

a	b	c	d	e	f	g
0	0	0	0	1	1	0


☐

a	b	c	d	e	f	g
0	1	1	0	0	0	0

☐

a	b	c	d	e	f	g
1	1	1	1	0	0	1

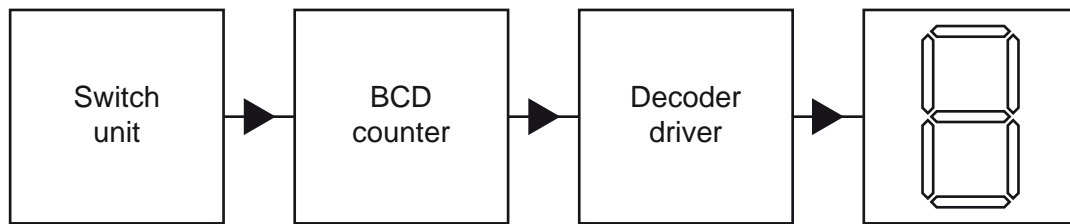4. This is the block diagram for a single digit decimal counting system.




(a) Why is it better to use a BCD (binary-coded decimal) counter than a binary counter?
(Tick (✓) the correct answer.)

[1]

- ☐ It counts up faster
- ☐ It resets automatically on the tenth pulse
- ☐ It outputs letters and numbers to the 7-segment display
- ☐ Binary is easier for humans to understand

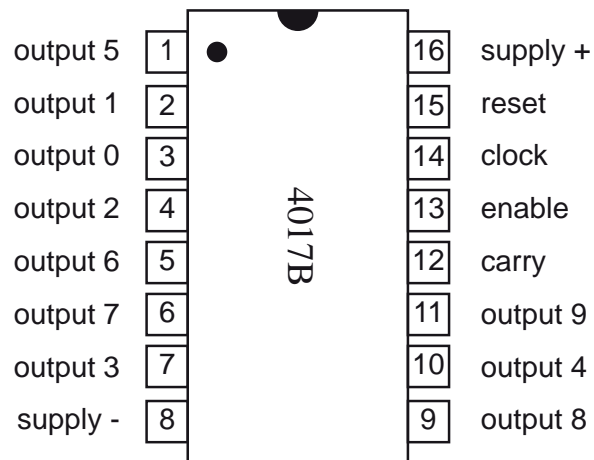(b) The pinout for a decade counter is shown below.



Why is this type of counter unsuitable for the single digit decimal counting system?
(Tick (✓) the correct answer.)

[1]

☐

A decade counter counts up in tens, not in units

☐

A decade counter cannot reset automatically


☐

Each output of the counter goes high in turn

☐

Every tenth count, it outputs a pulse from its clock pin

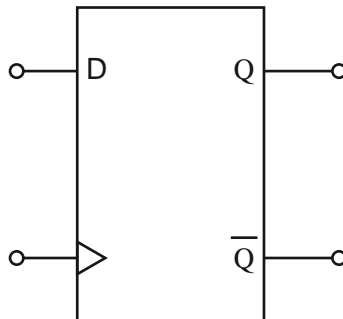5. (a) Complete the following statements about the action of the rising-edge D-type flip-flop by inserting either 0 or 1 in the boxes below. [2]




The Q output of a D-type flip-flop is initially at logic 0.
The Data input is set to logic 1.

When the clock input changes from to
the \bar{Q} output changes from to

- (b) A rising-edge triggered D-type flip-flop is set up as a latch. It receives the clock signal shown in the top graph.

Use the axes provided to show the corresponding Q and \bar{Q} outputs. [3]


The Q output starts at logic 0.

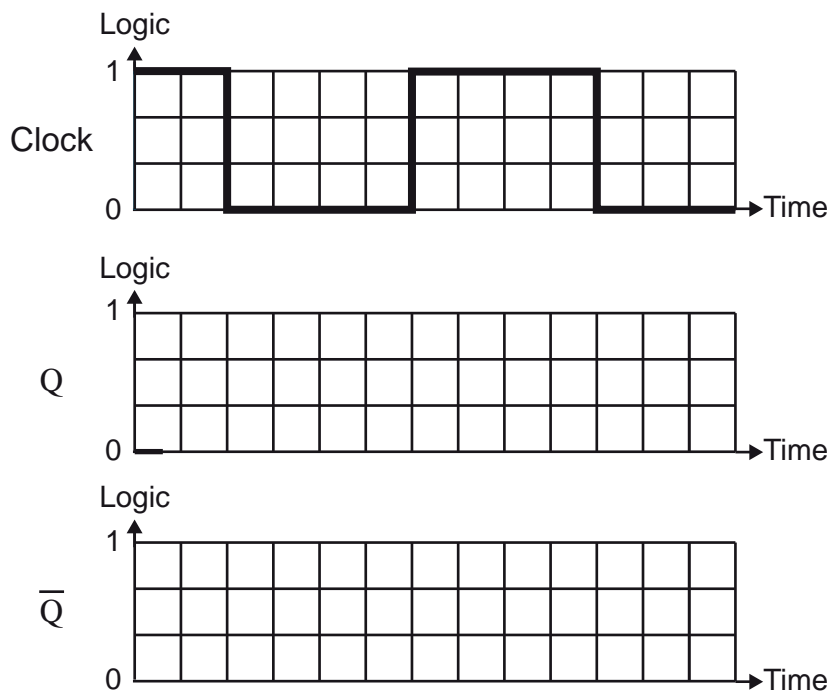

6. A D-type flip-flop can be set up as a 'divide-by-two' subsystem.

- (a) Which **one** of the following shows the connections needed to do this?
(Tick (✓) the correct answer.)


[1]

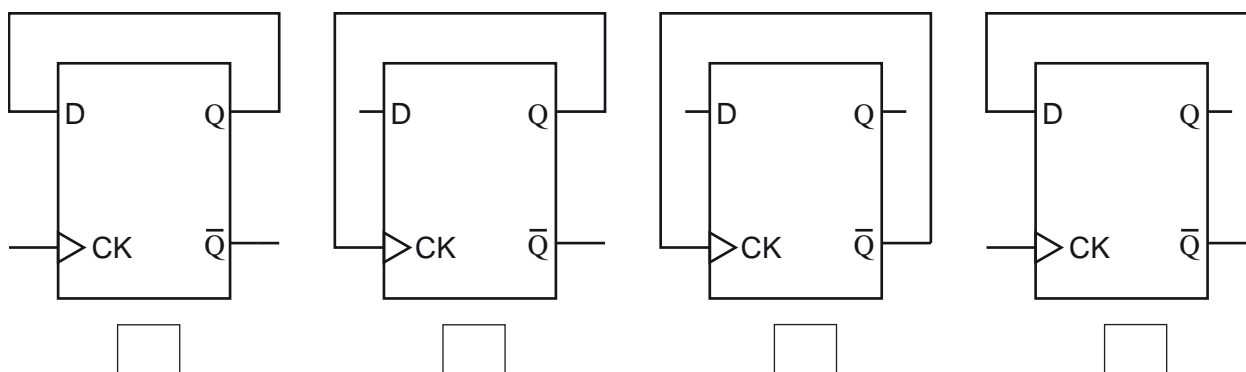


- (b) Complete the graph for the Q output of the 'divide-by-two' sub-system when it receives the clock signals shown.

[2]


Initially the Q output is at logic 0.

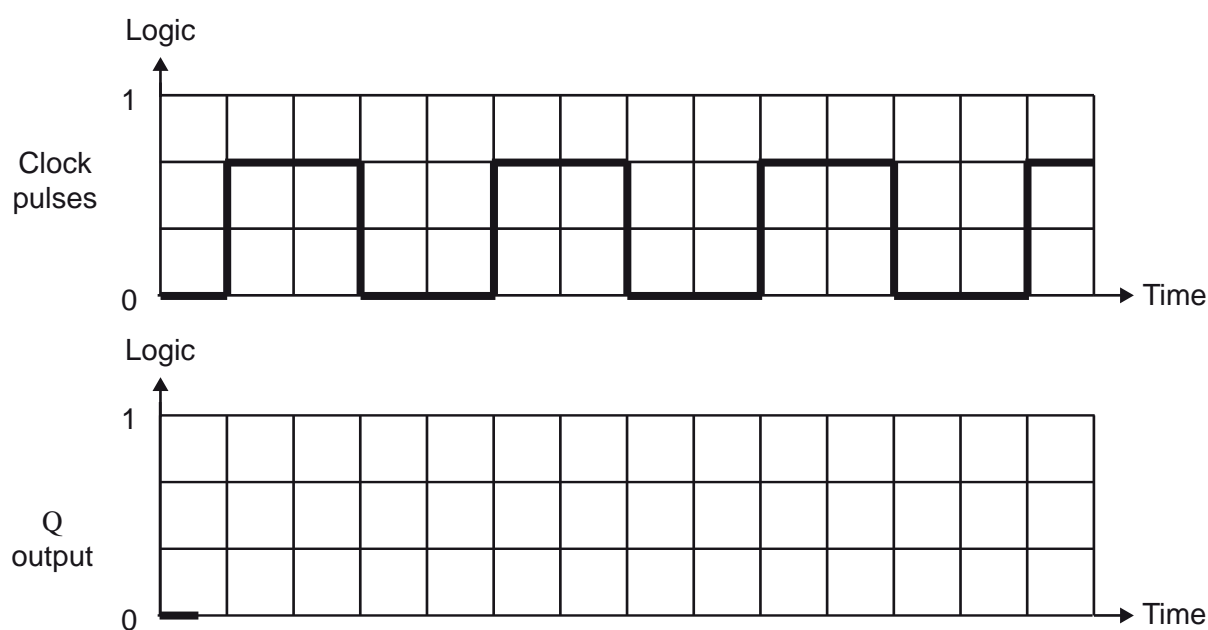

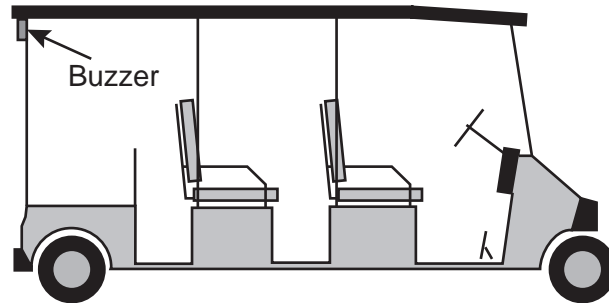7. At an airport, an electric buggy is used to transport people and their luggage. It has a warning buzzer which sounds when it reverses.



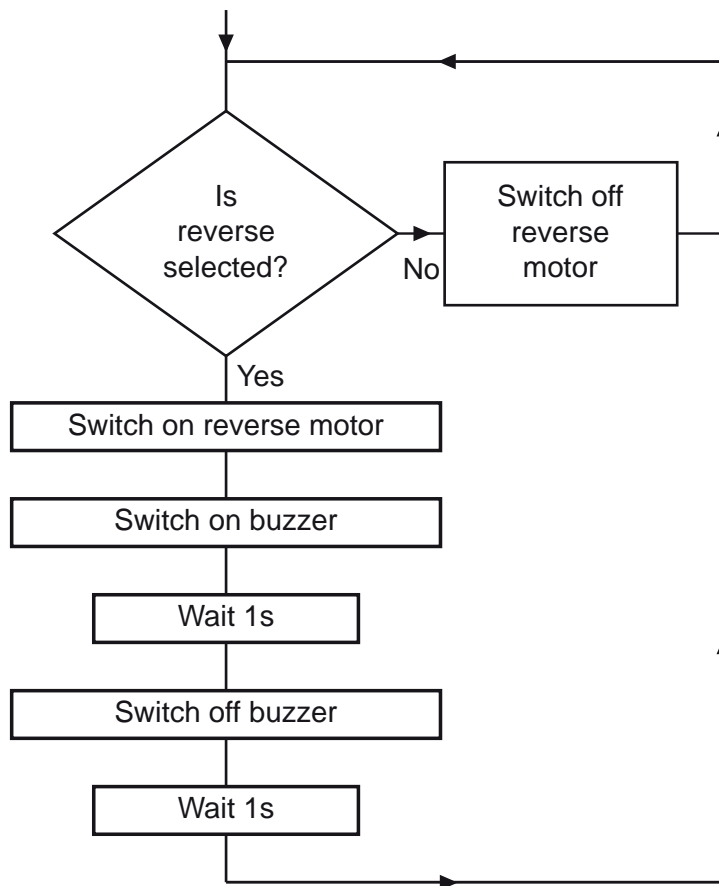- (a) The flowchart that controls reversing is shown below. Reverse is selected for **three** seconds only.



Describe what happens over the **five** seconds after reverse is selected.

[3]

.....


.....

.....

.....

.....

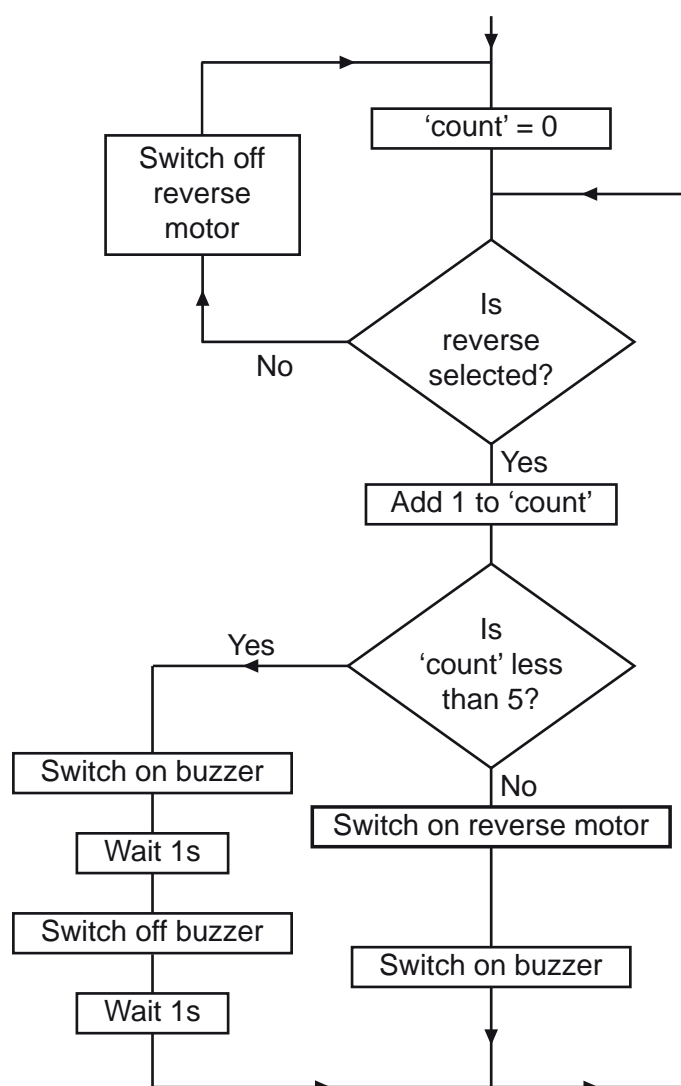(b) The flowchart program is modified as shown.



- (i) Reverse gear is selected. How many times does the buzzer pulse before the buggy moves? [1]

..... times

- (ii) During testing, while the buggy is moving backwards, the gear lever is moved out of reverse. The buggy stops moving. Two other things happen. State **one** which is necessary and **one** which is a problem. [2]

Necessary

.....

Problem

.....

8. A public address system contains two microphones, two preamplifiers, a power amplifier, a mixer and a loudspeaker.

(a) Complete the answers/sentences by drawing a circle around the correct word in the brackets:

(i) In this system, electrical signals are converted into sound by the [1]
(preamplifier / power amplifier / mixer / loudspeaker).

(ii) Which sub-system is used to combine the signals that start in the microphones? [1]
(preamplifier / power amplifier / mixer / loudspeaker)

(iii) Which boosts the voltage signal from a source such as a microphone? [1]
(preamplifier / power amplifier / mixer / loudspeaker)

(b) Circle the correct answer. The range of frequencies that an amplifier can successfully amplify is known as its: [1]

input voltage / power supply voltage / gain / bandwidth





(c) A public address system uses a voltage amplifier to boost a signal from 20 mV to 240 mV.
What is the voltage gain of this amplifier? [1]

.....

BLANK PAGE

9. (a) Which of the following is the circuit diagram for a non-inverting voltage amplifier?
(Tick (✓) the correct answer.)

[1]

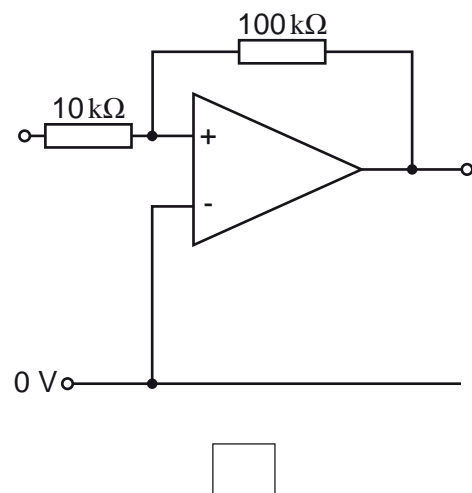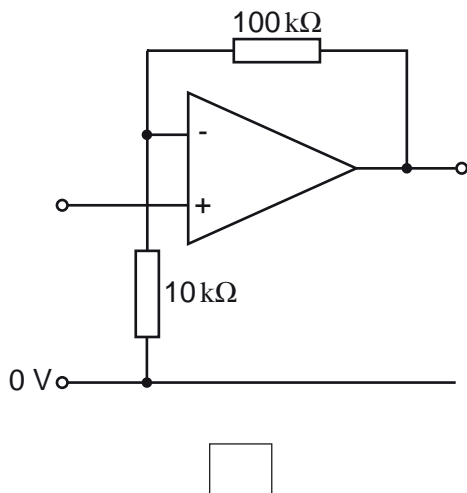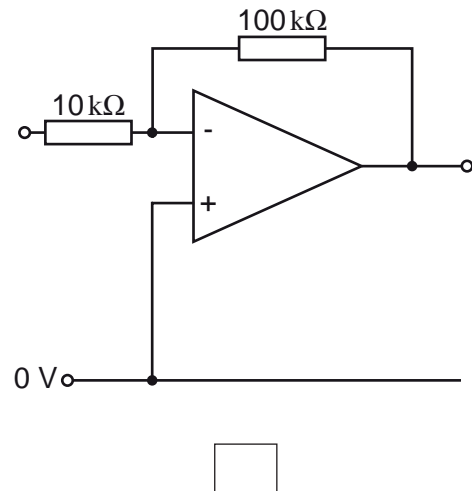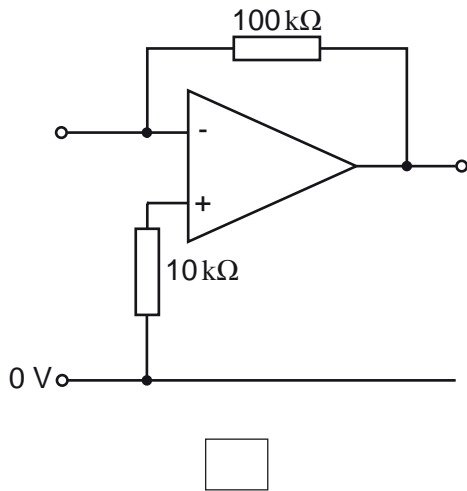


- (b) What is the voltage gain of the non-inverting amplifier?

[1]

.....

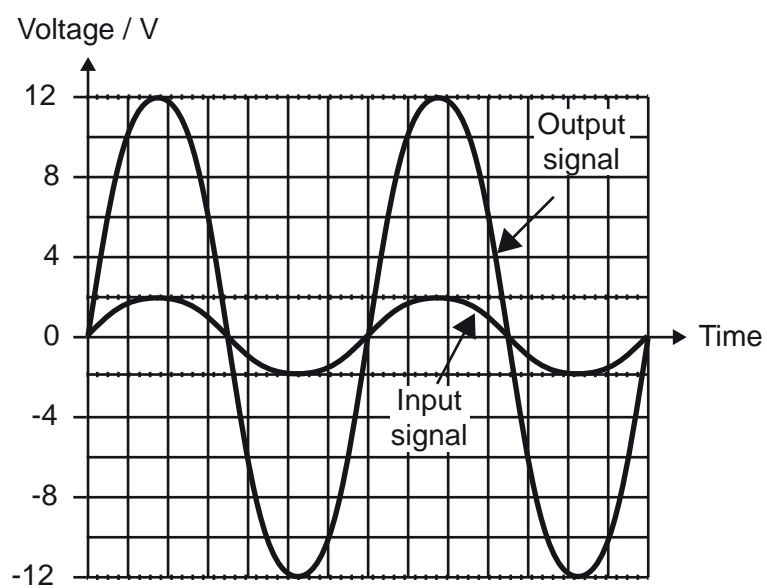
- (c) The graphs show the input and output signals for a **different** amplifier.




What is the voltage gain of this amplifier?

[1]

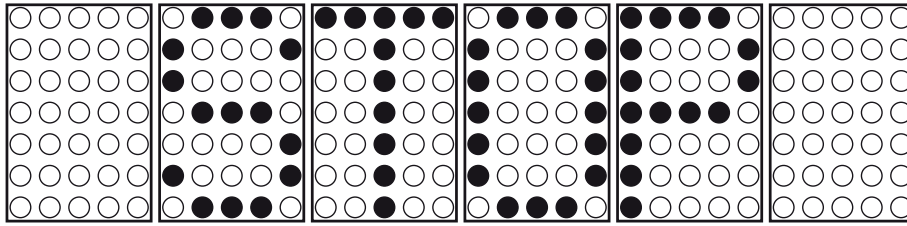10. A warning sign is made up of a number of sections and is used to display messages such as "STOP".



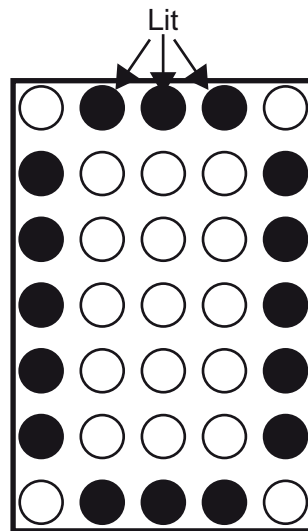
Each section has 7 rows each containing 5 LEDs. The LEDs are controlled individually, using a memory IC that stores all 26 letters of the English alphabet. The one below is lighting the LEDs needed to show the letter 'O'.



- (a) How many address locations are used to store the alphabet? [1]

- (b) How many data bits must each location have in order to control the LEDs? [1]

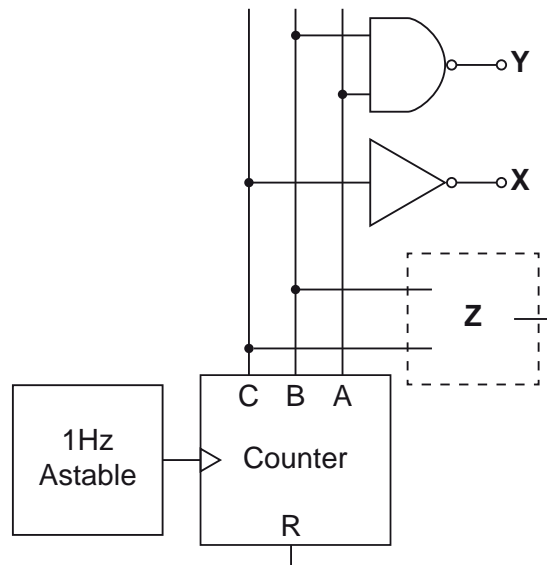11. The circuit diagram shows part of a sequence generator.
The purpose of the table is to summarise the behaviour of the system.



Pulse	Counter outputs			Sequence generator outputs	
	C	B	A	X	Y
0	0	0	0		
1	0	0	1		
2	0	1	0		
3	0	1	1		
4	1	0	0		
5					
6	Reset				

- (a) Complete the 'C', 'B' and 'A' columns by adding either a '0' or a '1' to show the effect of pulse 5. [1]
- (b) Complete the 'X' and 'Y' columns by adding either a '0' or a '1'. [2]
- (c) For how many seconds after the counter is reset does output C remain at logic 0? Circle the correct answer. [1]

1 2 4 6

- (d) The system resets on pulse 6. What type of logic gate is needed in box 'Z' to do this? Circle the correct answer. [1]

NOT AND NAND OR NOR

12. When connected to a 5 V power supply, the output of a Schmitt inverter:



- changes from logic 1 to logic 0 when a **rising** input voltage reaches 3 V;
- changes from logic 0 to logic 1 when a **falling** input voltage reaches 1 V.

For this system, a signal at 0.5 V represents logic 0 and a signal at 5 V represents logic 1.

The Schmitt Inverter receives the signal shown in the upper graph.


Draw the expected output signal.

[3]

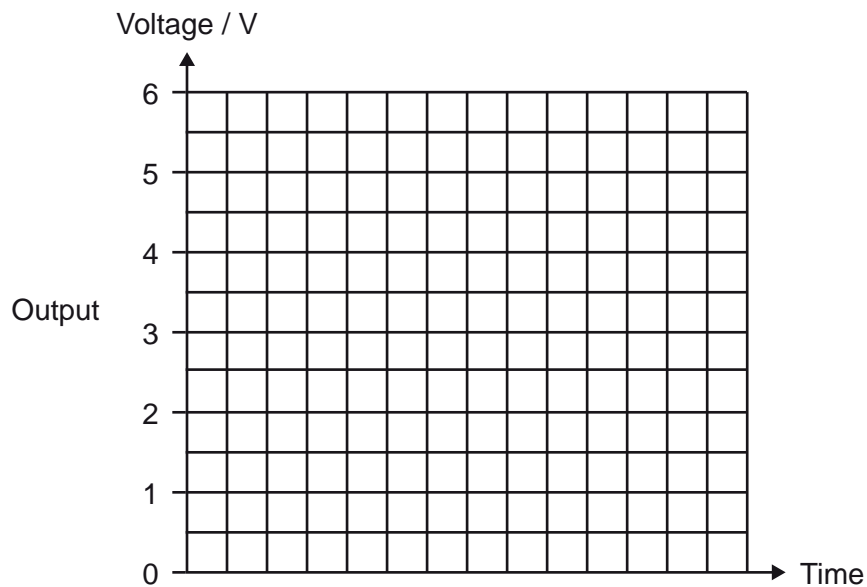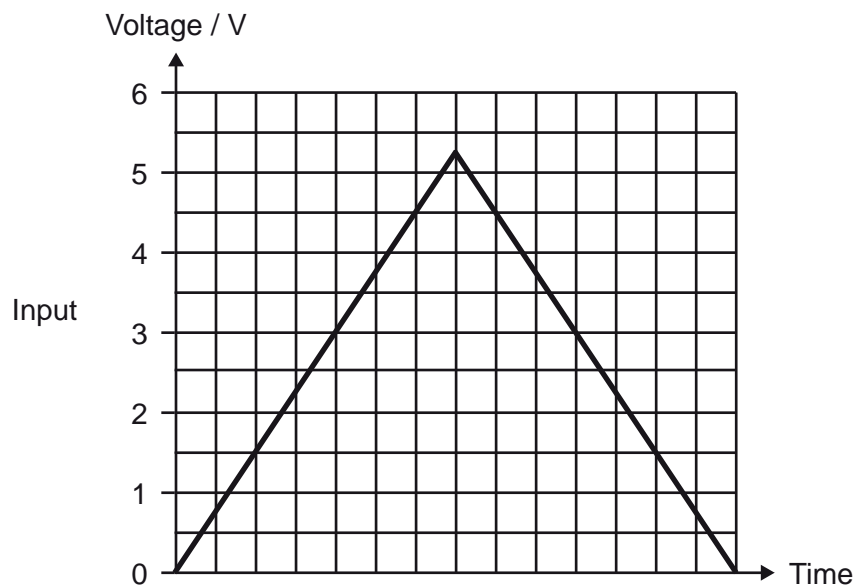

BLANK PAGE

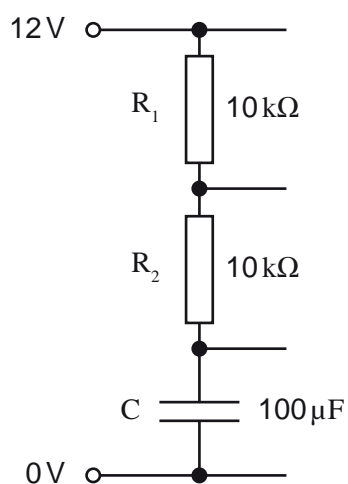13. (a) An astable circuit includes the following R-C network:



- (i) Convert $10\text{ k}\Omega$ to ohms.

[1]

..... ohms

- (ii) Convert $100\text{ }\mu\text{F}$ to farads. Circle the correct answer.

[1]

0.000001 / 0.00001 / 0.0001 / 100 / 100 000 000

- (iii) The pulse frequency, f , produced by the astable is given by the formula:


$$f = \frac{1.4}{(R_1 + 2R_2) \times C}$$

Calculate the pulse frequency produced by the astable.

[1]

Pulse frequency = Hz

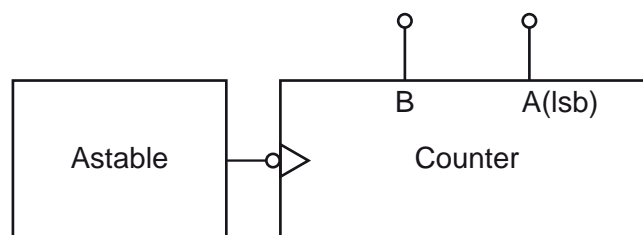
- (b) A 2-bit counting system uses an astable circuit.



The counter is initially reset and is falling-edge triggered.
Output A is the least-significant bit (lsb).


The upper graph shows pulses arriving at the input of the counter.
Draw the resulting signals at outputs A and B.

[3]

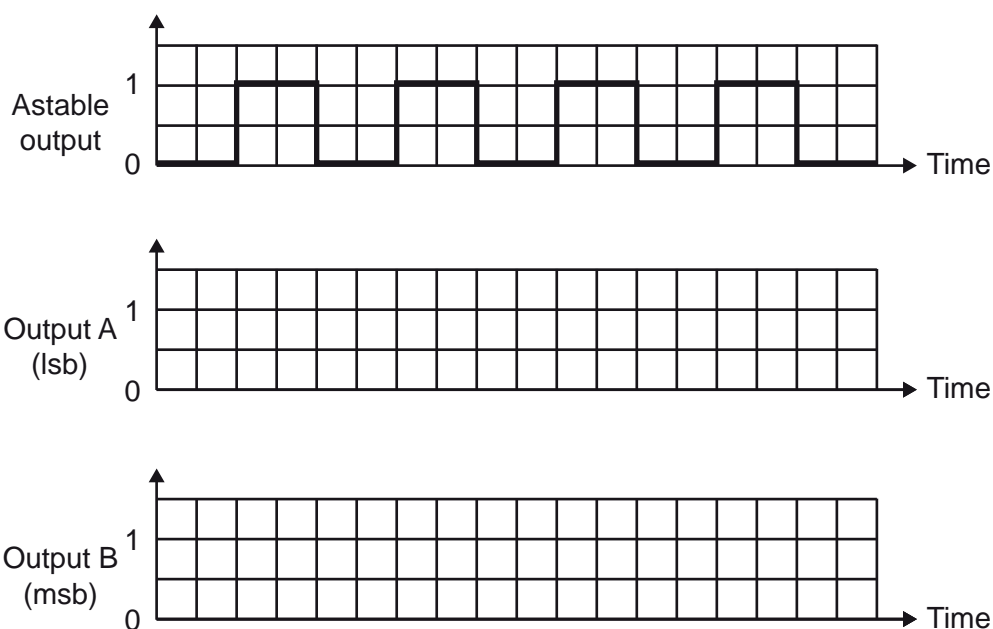


14. An **inverting** amplifier has a voltage gain of **-5**.

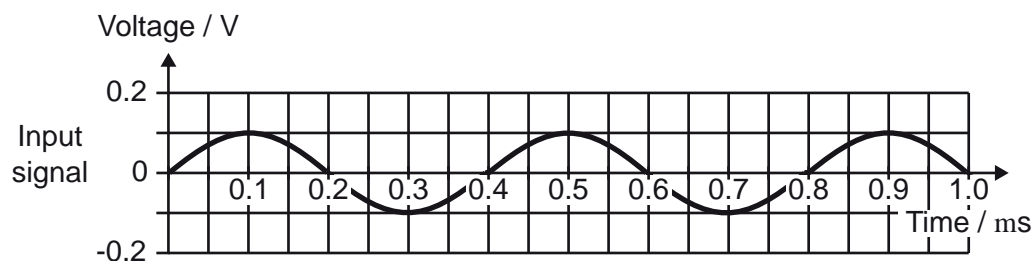(a) The graph shows the signal applied to the input of this amplifier.





On the axes below draw a wave that shows the corresponding **output** signal.

[3]

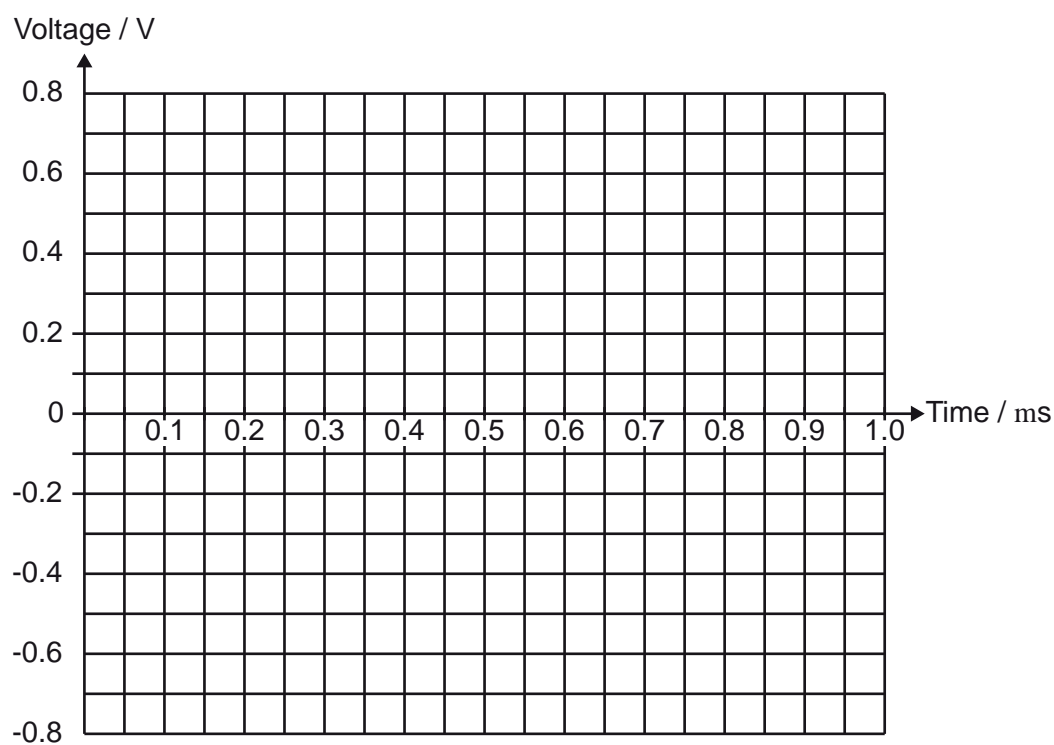

- (b) Draw the correct components into the circuit diagram for this inverting amplifier with a voltage gain of -5. [3]

Examiner
only

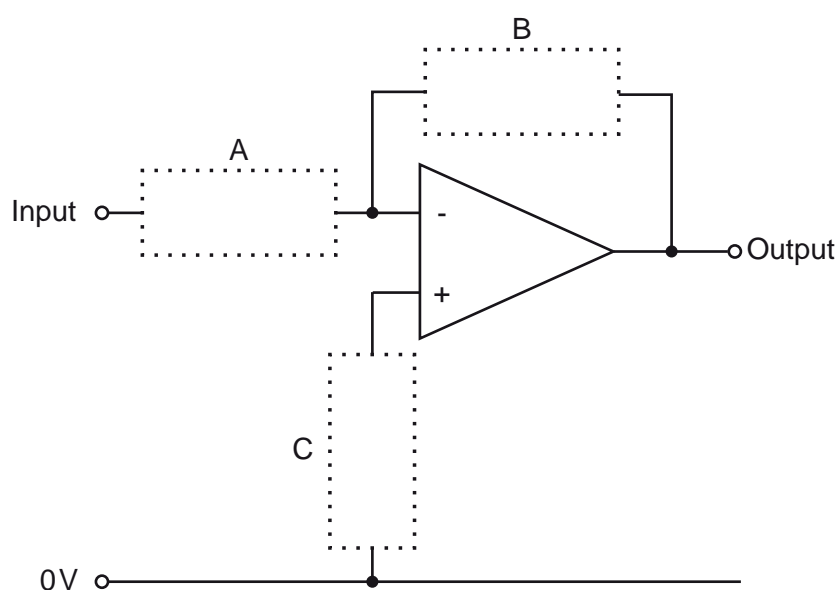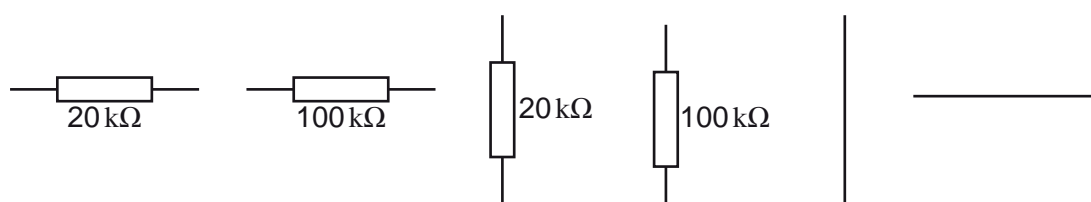

15. (a) A transistor switches on a fan motor automatically when the room gets too hot.



Part of the circuit for this system is shown below.

Complete it by drawing suitable components.


[3]

The system must:

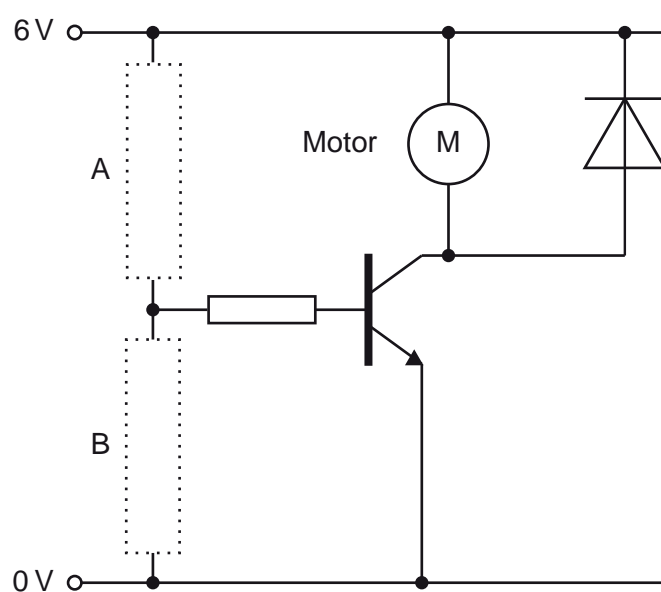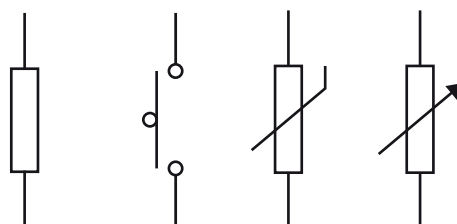- switch on the motor when the temperature gets too hot;
- allow the user to adjust the switch-on temperature.



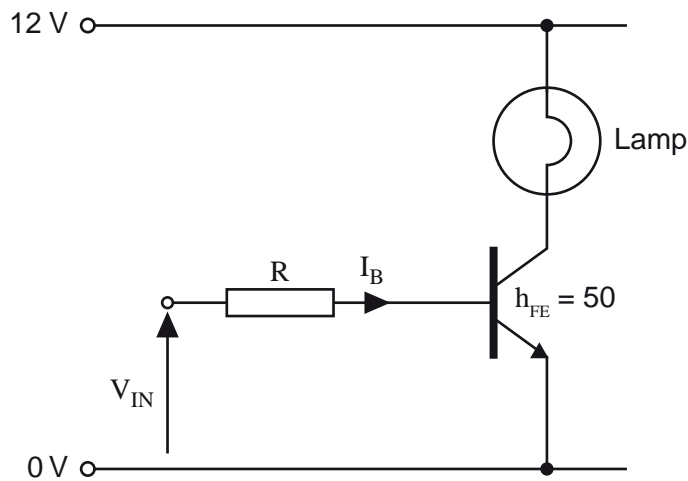- (b) A **different** transistor switch is used to interface a logic system to a lamp unit. Assume that the transistor is just saturated.



- (i) When the logic system outputs logic 1, $V_{IN} = 10.7\text{ V}$. This produces a base current, I_B , of 2 mA .

What is the voltage across resistor R?

[1]

Voltage = V

- (ii) What is the resistance of the base resistor, R?

[1]

Resistance = $\text{k}\Omega$

- (iii) The transistor has a current gain (h_{FE}) of 50. Calculate the collector current when the base current, I_B , is 2 mA .

[1]

Current = mA

END OF PAPER