

Surname	Centre Number	Candidate Number
Other Names		0



GCSE

4161/01



ELECTRONICS

UNIT E1: Paper replacement test

WEDNESDAY, 13 JUNE 2018 – AFTERNOON

1 hour

For Examiner's use only		
Question	Maximum Mark	Mark Awarded
1.	6	
2.	4	
3.	3	
4.	2	
5.	1	
6.	3	
7.	2	
8.	4	
9.	6	
10.	2	
11.	4	
12.	2	
13.	3	
14.	2	
15.	3	
16.	4	
17.	5	
18.	4	
Total	60	

ADDITIONAL MATERIALS

A calculator and a ruler.

INSTRUCTIONS TO CANDIDATES

Use black ink or black ball-point pen.

Write your name, centre number and candidate number in the spaces at the top of this page.

Answer **all** questions in the spaces provided in this booklet.

INFORMATION FOR CANDIDATES

The number of marks is given in brackets at the end of each question or part-question.

INFORMATION SHEET FOR UNIT E1

This information may be of use in answering the questions.

1. Resistor Colour Codes

BLACK	0	GREEN	5
BROWN	1	BLUE	6
RED	2	VIOLET	7
ORANGE	3	GREY	8
YELLOW	4	WHITE	9

The fourth band colour gives the tolerance as follows:

GOLD \pm **5%**

SILVER \pm **10%**

2. Preferred Values for Resistors – E24 series


10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91.

3. **Resistance** = $\frac{\text{voltage}}{\text{current}}$; $R = \frac{V}{I}$.

4. **Effective resistance**, R , of two resistors R_1 and R_2 in series is given by $R = R_1 + R_2$.

5. **Effective resistance**, R , of two resistors R_1 and R_2 in parallel is given by $R = \frac{R_1 R_2}{R_1 + R_2}$.

6. Voltage Divider

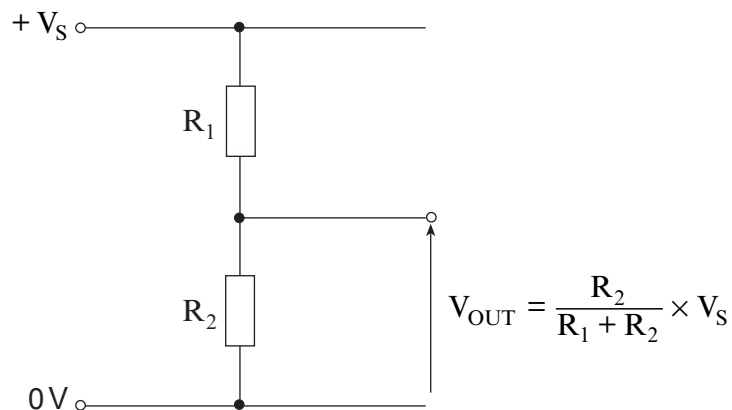

7. **Power** = voltage \times current; $P = VI = I^2R = \frac{V^2}{R}$.

8. **LED** The forward voltage drop across a LED is 2V.

9. **NPN Transistors** (i) Current gain = $\frac{\text{Collector current}}{\text{Base current}}$; $h_{FE} = \frac{I_C}{I_B}$.

(ii) The forward voltage drop across the base emitter junction is 0.7 V.


Answer **all** questions.


1. (a) Here is a list of electronic components.


- | | | |
|-----------|----------------------|---------------------|
| Diode | LED | Push-to-make switch |
| Thyristor | Push-to-break switch | Transistor |

Select the correct name for **each** component.

[3]

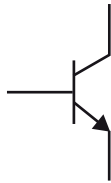

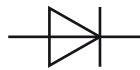

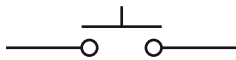

(b) Different electronic sub-systems are listed below.


- | | | |
|--------------------------|------------------------|-------------|
| OR gate | Transistor switch unit | Buzzer unit |
| Temperature sensing unit | Delay unit | Switch unit |
| Light sensing unit | Solenoid unit | Lamp unit |

Write each subsystem into the correct column in the table below.

[3]

Input sub-system	Processing sub-system	Output sub-system

2. Study the following circuit.

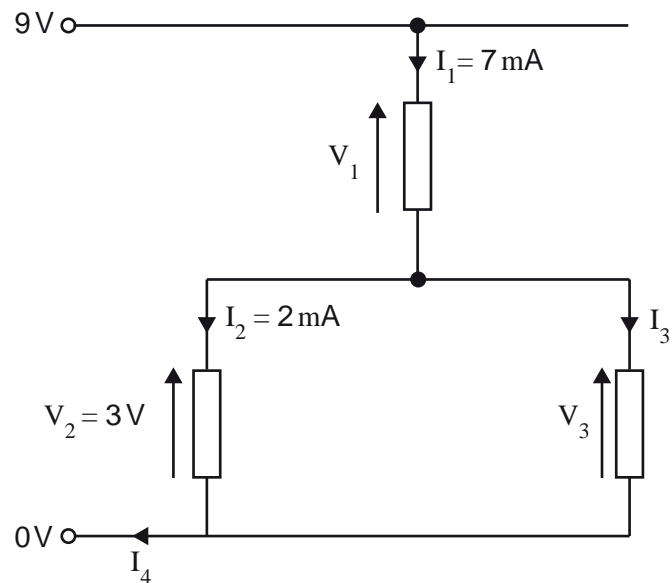

Circle the correct answers to the following questions.

(a) What is the value of V_1 ? [1]

0V 1V 2V 3V 4V 5V 6V 7V 8V 9V 10V 11V 12V 13V

(b) What is the value of I_3 ? [1]

0mA 1mA 2mA 3mA 4mA 5mA 6mA 7mA 8mA 9mA 10mA 11mA 12mA 13mA

(c) What is the value of V_3 ? [1]

0V 1V 2V 3V 4V 5V 6V 7V 8V 9V 10V 11V 12V 13V


(d) What is the value of I_4 ? [1]

0mA 1mA 2mA 3mA 4mA 5mA 6mA 7mA 8mA 9mA 10mA 11mA 12mA 13mA

3. Here is the pinout for a logic gate IC.

(a) Number all the pins on the diagram. [1]

1 2 3 4 5 6 7 8 9 10 11 12 13 14

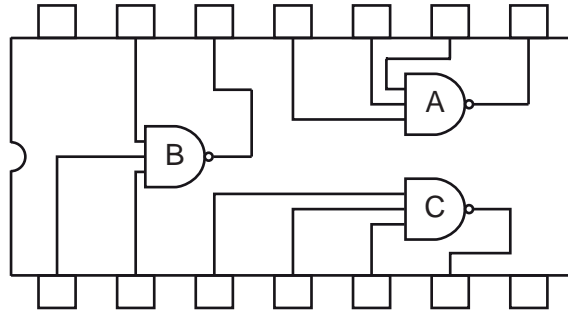


(b) Tick (✓) the box(es) for the input pin(s) for gate B. [1]

<input type="checkbox"/>	1	<input type="checkbox"/>	2	<input type="checkbox"/>	3	<input type="checkbox"/>	4	<input type="checkbox"/>	5	<input type="checkbox"/>	6	<input type="checkbox"/>	7
<input type="checkbox"/>	8	<input type="checkbox"/>	9	<input type="checkbox"/>	10	<input type="checkbox"/>	11	<input type="checkbox"/>	12	<input type="checkbox"/>	13	<input type="checkbox"/>	14

(c) Tick (✓) the box(es) for the output pin(s) for gate A. [1]

<input type="checkbox"/>	1	<input type="checkbox"/>	2	<input type="checkbox"/>	3	<input type="checkbox"/>	4	<input type="checkbox"/>	5	<input type="checkbox"/>	6	<input type="checkbox"/>	7
<input type="checkbox"/>	8	<input type="checkbox"/>	9	<input type="checkbox"/>	10	<input type="checkbox"/>	11	<input type="checkbox"/>	12	<input type="checkbox"/>	13	<input type="checkbox"/>	14

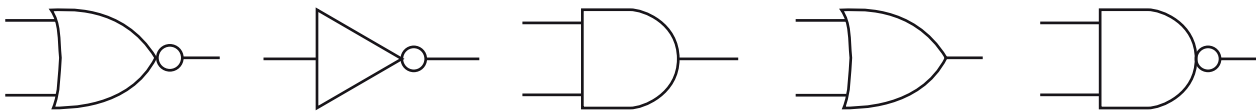
4. Draw the correct logic gate to match the name in the table below. [2]




Logic gate name	Symbol
AND gate	
NOR gate	

5. The following diagram shows the circuit symbol for a MOSFET. Tick (✓) the correctly labelled symbol.

[1]

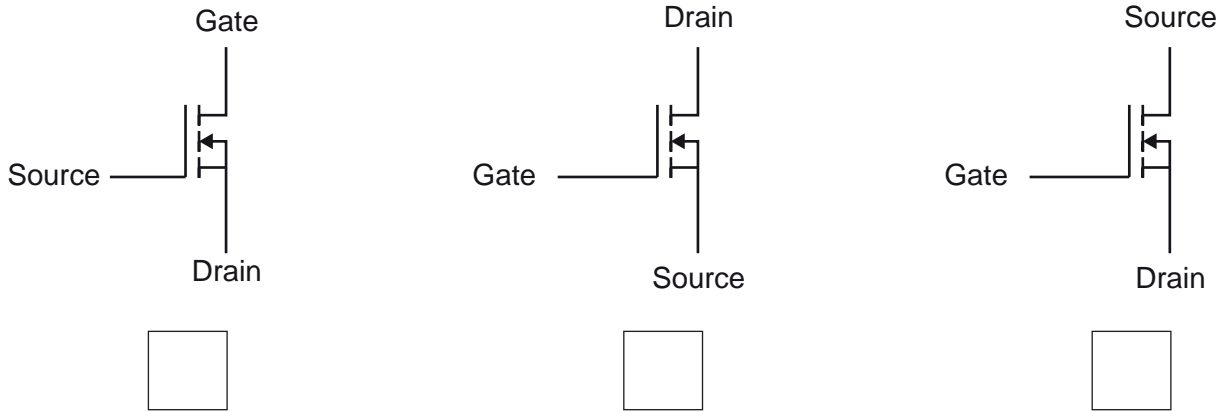

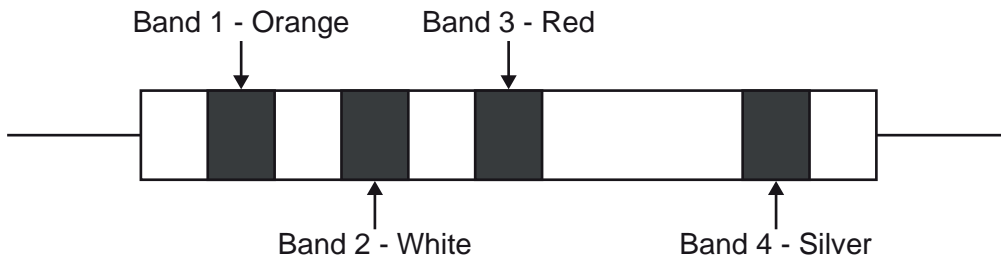6. The diagram shows a resistor from the E24 series.




Circle the correct values for each band to show the value of this resistor in ohms.

[3]

Band 1	Band 2	Band 3
0	0	No Zeros
1	1	0
2	2	00
3	3	000
4	4	0000
5	5	00000
6	6	000000
7	7	
8	8	
9	9	

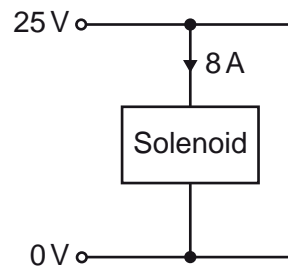7. The circuit shows a solenoid connected to a power supply.



- (a) Select the correct equation to calculate the power used in the solenoid in watts (W). [1]

$$P = \frac{8}{25}$$

$$P = \frac{25}{8}$$

$$P = 25 \times 8000$$

$$P = 25 \times 8$$

$$P = \frac{8}{2.5}$$

$$P = \frac{25000}{8}$$

- (b) Calculate the power used in the solenoid.


[1]

.....

.....

.....

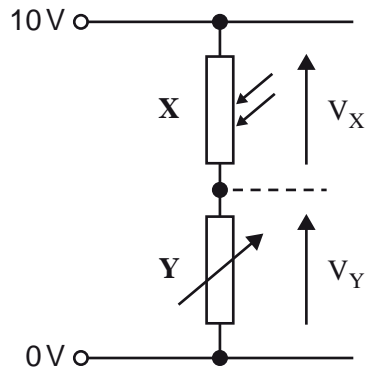8. The following analogue sensing circuit is used as part of a security system.



- (a) Circle the name of the component labelled **X**. [1]

LDR Resistor Thermistor Variable resistor

- (b) $V_Y = 2V$. Circle the correct voltage across the component **X**. [1]

0V 1V 2V 3V 4V 5V 6V 7V 8V 9V 10V

- (c) (i) What would happen to the value of V_Y if the resistance of component **Y** was increased? [1]

- V_Y would increase
- V_Y would decrease
- V_Y would stay the same
- V_Y would become 0V

- (ii) If the resistance value of component **Y** and the power supply voltage remain fixed, what would cause the output voltage V_Y to decrease? [1]

.....

.....

.....

9. A garden centre grows a number of plants from seed before making them available for sale. It is important that the soil remains moist while these seeds grow into young plants. A system is needed to monitor the condition of the soil during daylight hours. It continuously pulses a warning LED on and off when the soil is too dry.

A number of sensing sub-systems are available for use, with the following specifications:


- a light sensor that outputs a Logic 1 when in daylight and Logic 0 when it is dark
- a temperature sensor that outputs a Logic 1 when it is cold and Logic 0 when it is warm
- a moisture sensor that outputs a Logic 1 when wet and Logic 0 when dry.

Complete the block diagram for the monitoring system.

Each sub-system may be used more than once.

[6]

- | | | | |
|---------------------------------|------------------------------|---------------------------|------------------------------|
| Thyristor | OR gate | Delay unit | Pressure sensing unit |
| Temperature sensing unit | Moisture sensing unit | Pulse generator | |
| Transistor switch unit | NOT Gate | Light sensing unit | AND gate |

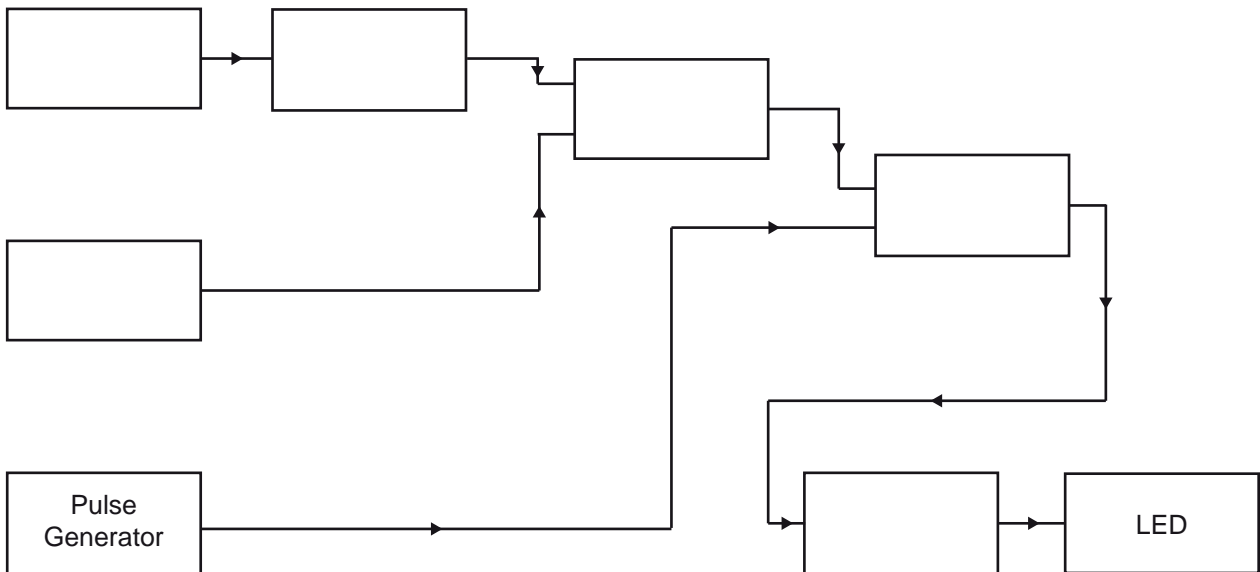

4161
010009

10. (a) Circle the logic gate that has the following truth table.

[1]

Inputs		Output
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

AND gate NAND gate NOR gate NOT gate OR gate



- (b) Circle the logic gate that outputs a logic 0 signal **only** when both inputs are at logic 0. [1]

AND gate NAND gate NOR gate NOT gate OR gate

11. A logic system has the following truth table.

INPUTS		OUTPUTS		
A	B	X	Y	Q
0	0	1	1	0
0	1	1	0	0
1	0	0	1	0
1	1	0	0	1

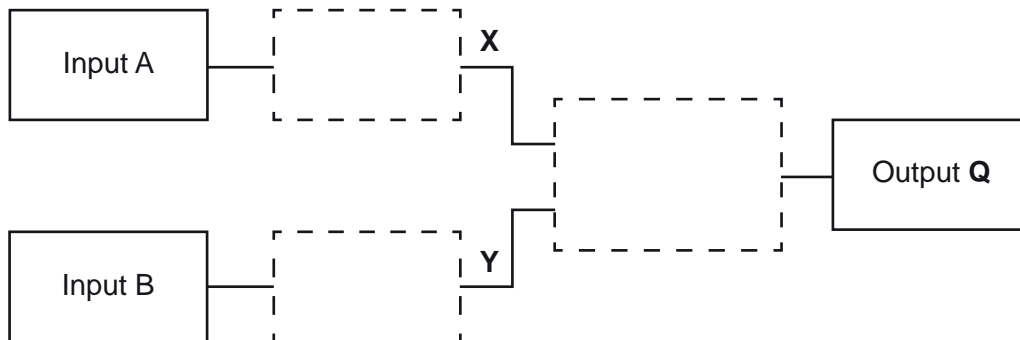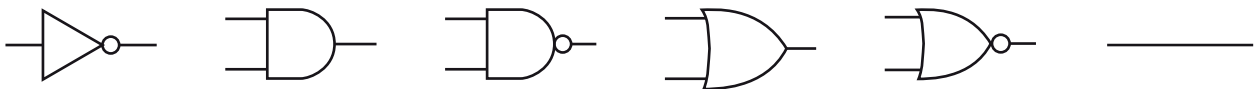(a) Draw the correct logic gates / connections in the following circuit to produce the truth table given above. [3]




(b) Circle the single gate that can be used to replace the combination above: [1]

- AND gate NAND gate NOR gate NOT gate OR gate

12. The logic circuit below contains some NAND gates that are redundant.

Tick (✓) all the redundant NAND gates.


[2]

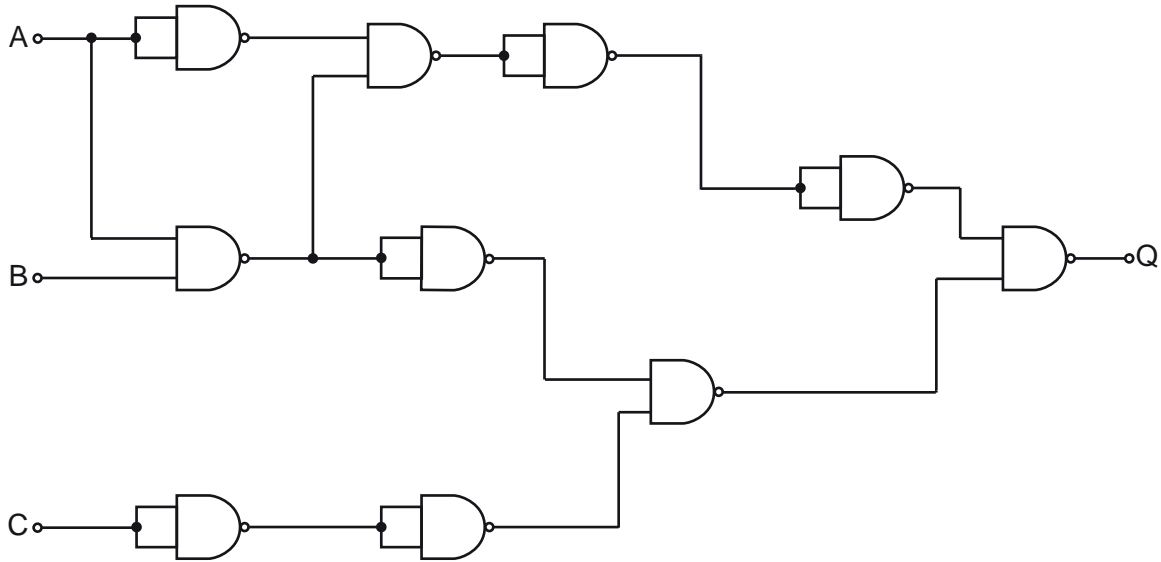

13. The diagrams below show three different combinations of resistors.

Calculate the effective resistance of each combination in $k\Omega$.

[3]

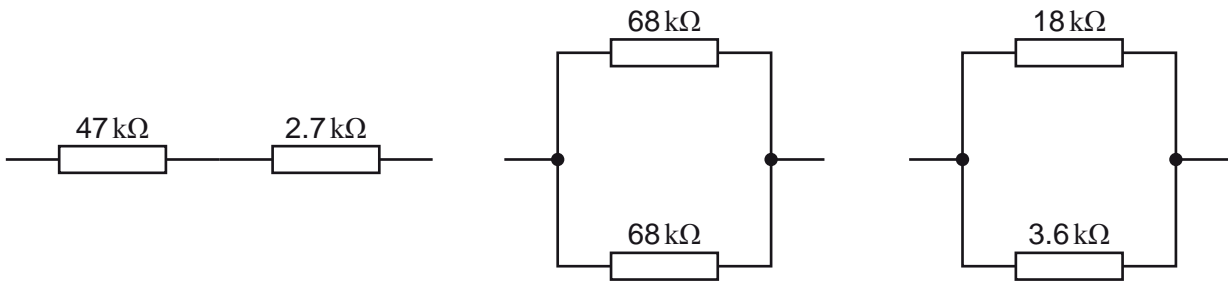

.....

 $k\Omega$

.....

 $k\Omega$

.....

 $k\Omega$

14. Select the correct truth table that represents the function described by each Boolean equation. Tick (✓) the correct answer.

(a) $Q = \bar{A}.B$

[1]

Inputs		Output
A	B	Q
0	0	0
0	1	1
1	0	0
1	1	0

Inputs		Output
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

Inputs		Output
A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

Inputs		Output
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

(b) $Q = \bar{A}.B$

[1]


Inputs		Output
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

Inputs		Output
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	1

Inputs		Output
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

Inputs		Output
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

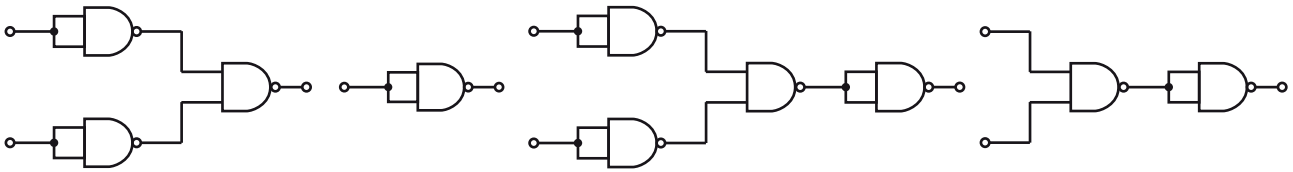15. The following show the NAND equivalent circuits for a number of standard gates.




Draw the NAND equivalent circuit to match the standard gate given below.

[3]

Standard gate

NAND equivalent circuit

NOT gate

 


NOR gate



AND gate



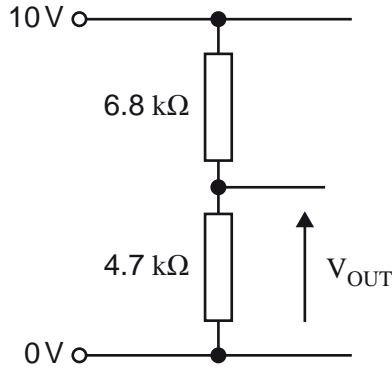16. (a) The following circuit can be used to provide a reference voltage to a comparator.



(i) Select the correct equation to calculate the voltage V_{OUT} . [1]

- | | | | |
|--------------------------|--|--------------------------|--|
| <input type="checkbox"/> | $V_{OUT} = \frac{11.5}{6.8 + 4.7} \times 10$ | <input type="checkbox"/> | $V_{OUT} = \frac{6.8}{10 + 4.7} \times 10$ |
| <input type="checkbox"/> | $V_{OUT} = \frac{4.7}{6.8 + 4.7} \times 10$ | <input type="checkbox"/> | $V_{OUT} = \frac{10}{4.7} \times 11.5$ |


(ii) Calculate the voltage V_{OUT} . [1]

.....

.....

.....

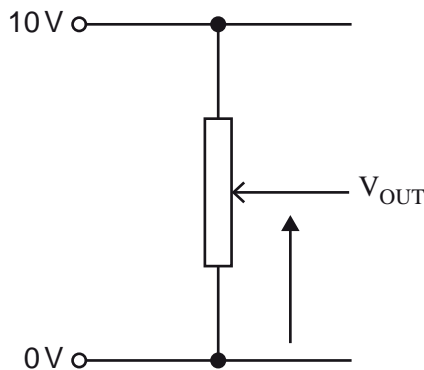(b) The following circuit using a variable resistor can also be used to provide a reference voltage for a comparator.




Give **two** advantages of the circuit shown in (b) compared with the one in (a). [2]

.....

.....

.....

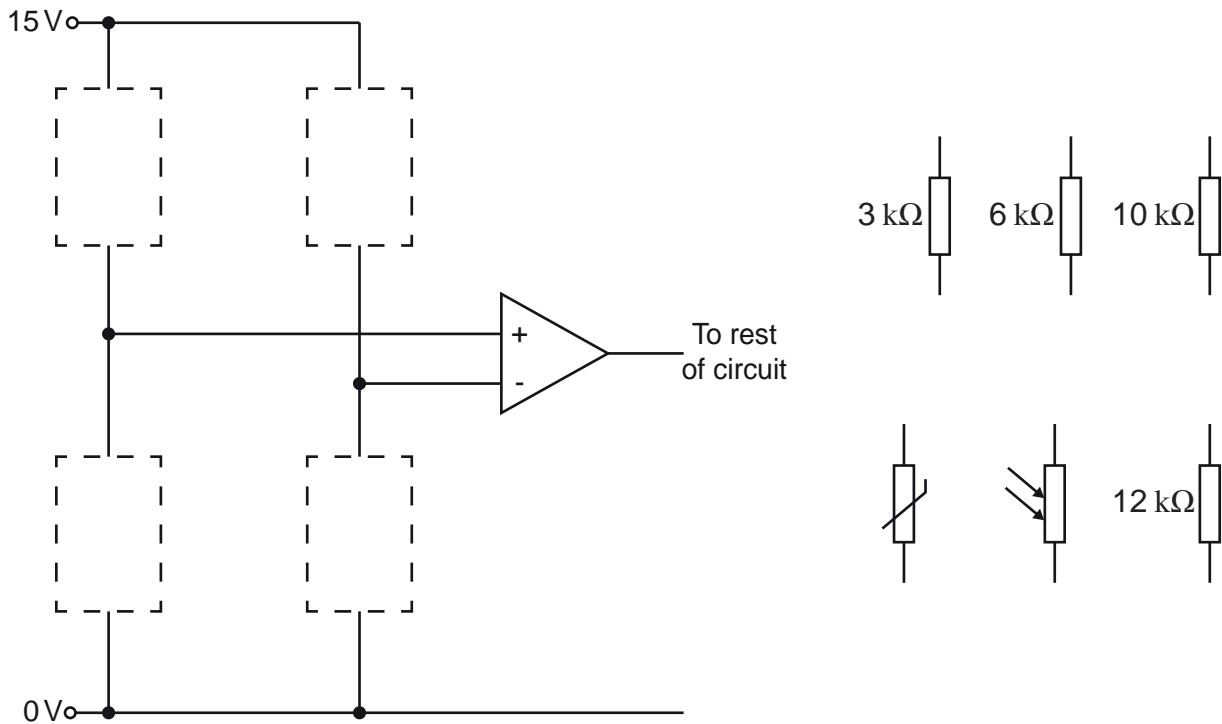17. The following **incomplete** circuit diagram shows a comparator to be used to switch on a warehouse heating system when the temperature gets too cold.




- (a) Draw the components necessary onto the circuit diagram to provide a voltage of 3V at the inverting input of the op-amp. [2]
- (b) Draw the components necessary onto the circuit diagram to provide a rising voltage at the non-inverting input when the temperature falls. [2]
- (c) How would you alter the circuit so that the temperature at which it switched on could be adjusted? [1]

.....

.....

.....

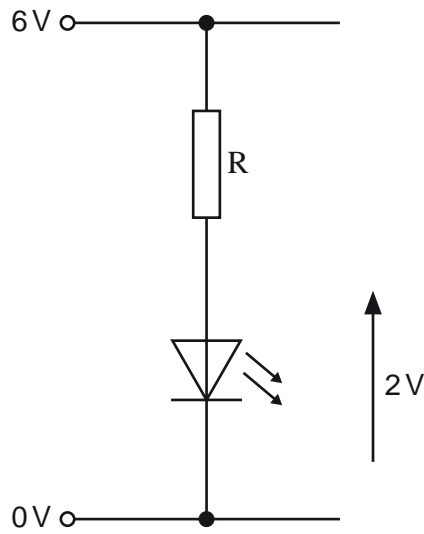18. A LED is used as a power on indicator as shown below.



(a) What is the voltage drop across the resistor R? [1]

..... V

(b) Select the correct equation to calculate the ideal resistance of resistor R (in $k\Omega$) to provide a current of 25 mA through the LED. Tick (\checkmark) the correct answer. [1]

- | | | | |
|--------------------------|--------------------|--------------------------|--------------------|
| <input type="checkbox"/> | $R = 6 \times 25$ | <input type="checkbox"/> | $R = \frac{2}{25}$ |
| <input type="checkbox"/> | $R = \frac{4}{25}$ | <input type="checkbox"/> | $R = 4 \times 25$ |
| <input type="checkbox"/> | $R = 6 \times 2$ | <input type="checkbox"/> | $R = \frac{6}{25}$ |
| <input type="checkbox"/> | $R = \frac{6}{2}$ | <input type="checkbox"/> | $R = 6 \times 23$ |

(c) What is the ideal resistance of resistor R? $k\Omega$ [1]

(d) Use the E24 resistor series on the information sheet to select the preferred value for resistor R **in ohms** to ensure that the current through the LED is just **less** than 25 mA. [1]

..... Ω

END OF PAPER

BLANK PAGE

BLANK PAGE