

Surname	Centre Number	Candidate Number
Other Names		0



**GCSE**

4162/01



**ELECTRONICS**

**UNIT E2: Paper replacement test**

FRIDAY, 15 JUNE 2018 – AFTERNOON

1 hour

For Examiner's use only		
Question	Maximum Mark	Mark Awarded
1.	5	
2.	3	
3.	3	
4.	4	
5.	3	
6.	2	
7.	4	
8.	2	
9.	4	
10.	2	
11.	5	
12.	3	
13.	3	
14.	5	
15.	4	
16.	5	
17.	3	
<b>Total</b>	<b>60</b>	

**ADDITIONAL MATERIALS**

A calculator and a ruler.

**INSTRUCTIONS TO CANDIDATES**

Use black ink or black ball-point pen.

Write your name, centre number and candidate number in the spaces at the top of this page.

Answer **all** questions in the spaces provided in this booklet.

**INFORMATION FOR CANDIDATES**

The number of marks is given in brackets at the end of each question or part-question.

## INFORMATION SHEET FOR UNIT E2

This information may be of use in answering the questions.

### 1. Resistor Colour Codes

<b>BLACK</b>	<b>0</b>	<b>GREEN</b>	<b>5</b>
<b>BROWN</b>	<b>1</b>	<b>BLUE</b>	<b>6</b>
<b>RED</b>	<b>2</b>	<b>VIOLET</b>	<b>7</b>
<b>ORANGE</b>	<b>3</b>	<b>GREY</b>	<b>8</b>
<b>YELLOW</b>	<b>4</b>	<b>WHITE</b>	<b>9</b>

The fourth band colour gives the tolerance as follows:

**GOLD**      $\pm$     **5%**

**SILVER**    $\pm$     **10%**

### 2. Preferred Values for Resistors – E24 series


10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91.

3. **Resistance** =  $\frac{\text{voltage}}{\text{current}}$  ;  $R = \frac{V}{I}$ .

4. **Effective resistance**,  $R$ , of two resistors  $R_1$  and  $R_2$  in series is given by  $R = R_1 + R_2$ .

5. **Effective resistance**,  $R$ , of two resistors  $R_1$  and  $R_2$  in parallel is given by  $R = \frac{R_1 R_2}{R_1 + R_2}$ .

### 6. Voltage Divider

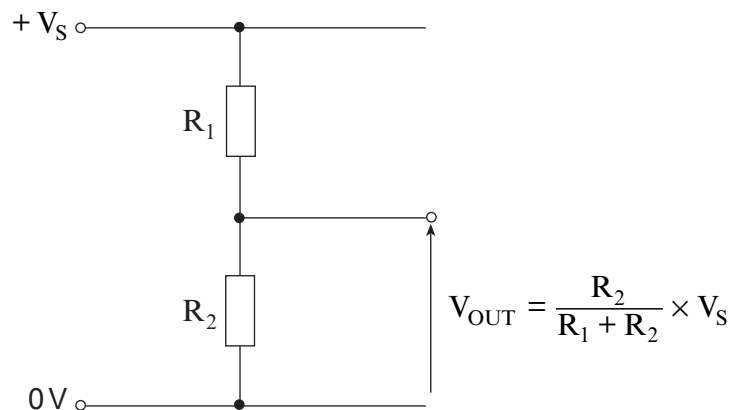

7. **Power** = voltage  $\times$  current;  $P = VI = I^2R = \frac{V^2}{R}$ .

8. **LED** The forward voltage drop across a LED is 2V.

9. **NPN Transistors**    (i) Current gain =  $\frac{\text{Collector current}}{\text{Base current}}$ ;  $h_{FE} = \frac{I_C}{I_B}$ .

(ii) The forward voltage drop across the base emitter junction is 0.7V.

**10. Amplifiers**

Voltage gain:  $A = \frac{V_{OUT}}{V_{IN}}$

Non-inverting amplifier:  $A = 1 + \frac{R_F}{R_1}$

Inverting amplifier:  $A = -\frac{R_F}{R_{IN}}$

Summing amplifier:  $V_{OUT} = -R_F \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots \right)$

Answer **all** questions.

1. (a) The boxes on the left give the names of three sub-systems.  
The boxes on the right give descriptions of four applications.  
For each sub-system, draw **one** line to link it to its correct application.

[3]


Sub-systems	Applications
<div style="border: 1px solid black; padding: 5px; width: fit-content; margin-bottom: 10px;">Monostable</div> <div style="border: 1px solid black; padding: 5px; width: fit-content; margin-bottom: 10px;">Astable</div> <div style="border: 1px solid black; padding: 5px; width: fit-content;">Latch</div>	<div style="border: 1px solid black; padding: 5px; margin-bottom: 10px;">A car indicator flashes on and off repeatedly.</div> <div style="border: 1px solid black; padding: 5px; margin-bottom: 10px;">A security light outside a house comes on for a short time when triggered.</div> <div style="border: 1px solid black; padding: 5px; margin-bottom: 10px;">The light inside a fridge comes on when the door is opened and goes off when it is closed.</div> <div style="border: 1px solid black; padding: 5px;">A burglar alarm stays on when triggered until a reset switch is pressed.</div>


- (b) Which **one** of the following statements about a monostable circuit is true?  
(Tick (✓) the correct answer.)  
When triggered, its output changes from logic 0 to logic 1... :


[1]

- ... instantly, and then stays there.
- ... for a certain time, and then resets automatically.
- ... and then changes back again, repeatedly.
- ... slowly, and then stays there.

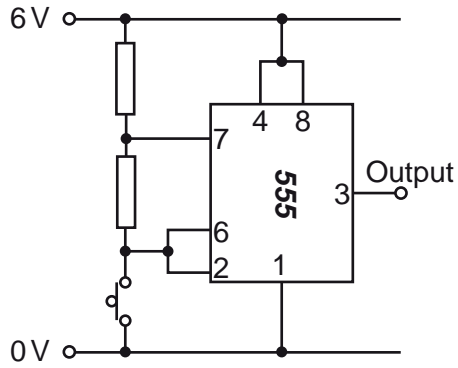
- (c) Which **one** of the following shows the circuit diagram for a monostable circuit based on a 555 timer?  
 (Tick (✓) the correct answer.) [1]



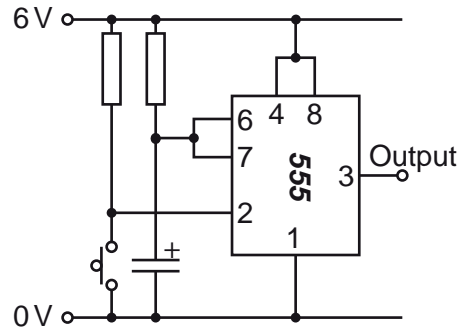

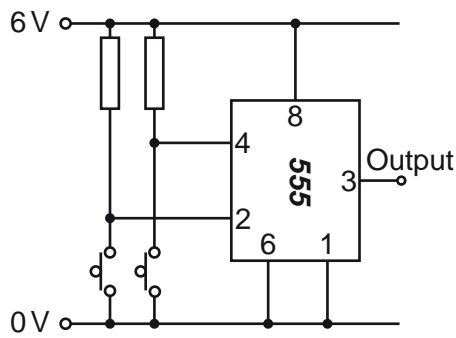

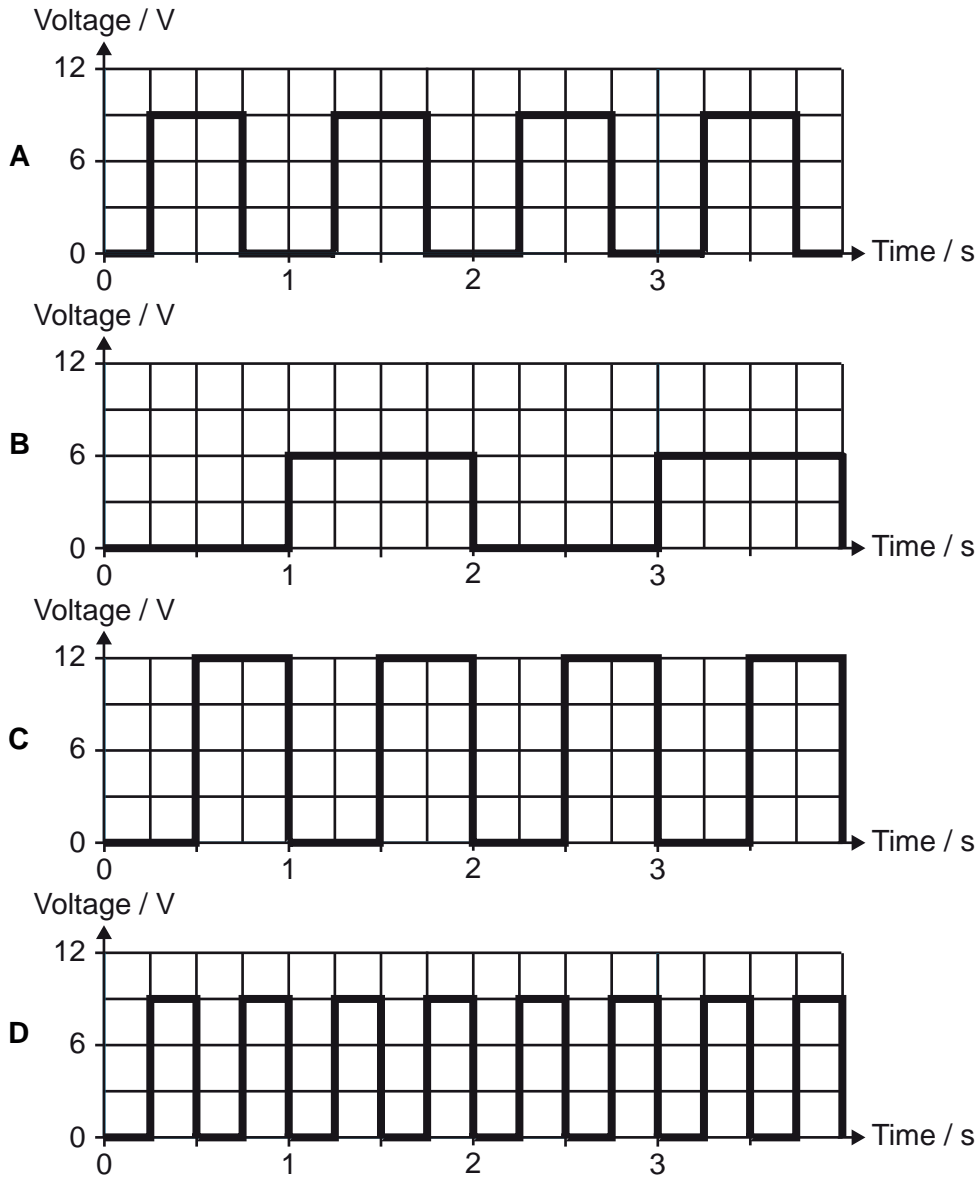2. (a) Here are four signals produced by astable circuits:



(i) Which **two** signals have the same amplitude? [1]

Answer:  and

(ii) Which **two** signals have the same period? [1]


Answer:  and

(b) An astable sub-system has a period of ten seconds. Calculate its frequency in Hz. [1]


Answer = ..... Hz

3. (a) The LED segments of a 7-segment display light when they receive logic 1 signals. The display needs to show the letter 'H'. Complete the truth table by selecting 0 or 1 for each segment to make the display. [1]

Segments							Character
a	b	c	d	e	f	g	
							H

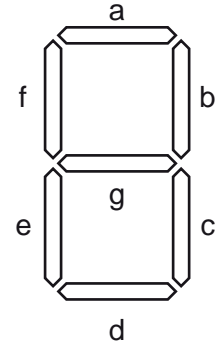

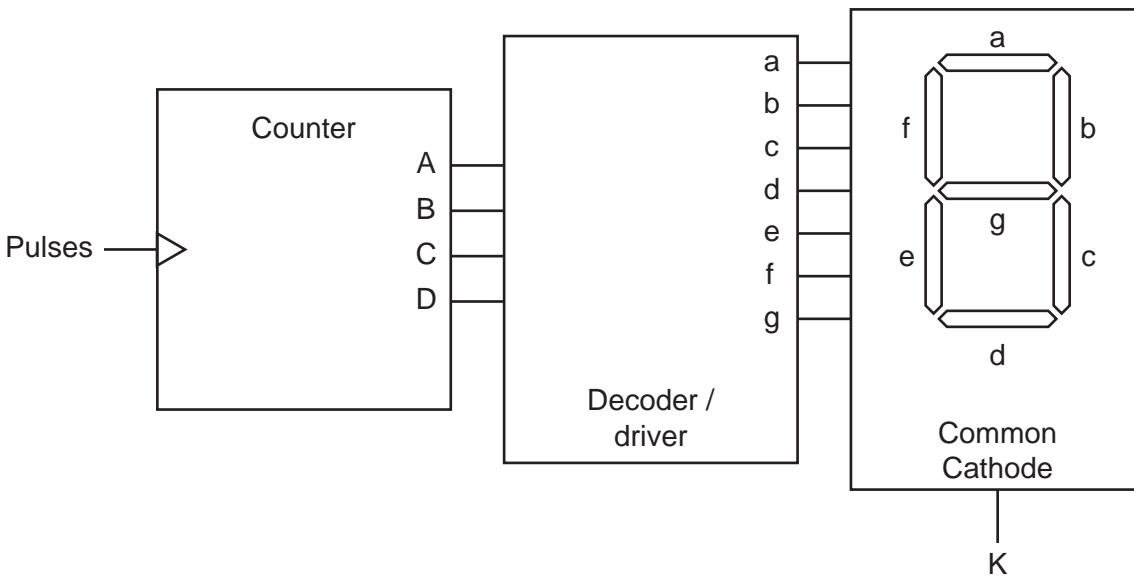- (b) The display is used in the single digit decimal counting system, shown in the diagram.



- (i) Which row in the table produces '7' on the display? (Tick (✓) the correct answer.) [1]

	Decoder / driver outputs						
	a	b	c	d	e	f	g
<input type="checkbox"/>	0	0	0	0	1	1	1
<input type="checkbox"/>	1	1	1	0	0	0	0
<input type="checkbox"/>	1	1	0	0	0	1	1
<input type="checkbox"/>	0	0	1	1	1	0	0

- (ii) What connection must be made to the common cathode pin to make the display work? Circle the correct answer. [1]


Connect pin K to

0V      5V      Reset      Clock

4. A temperature controller has two input sub-systems – a switch unit and a temperature-sensing unit.

The output of the temperature-sensing unit is interfaced to the logic gate by a Schmitt inverter.

[4]

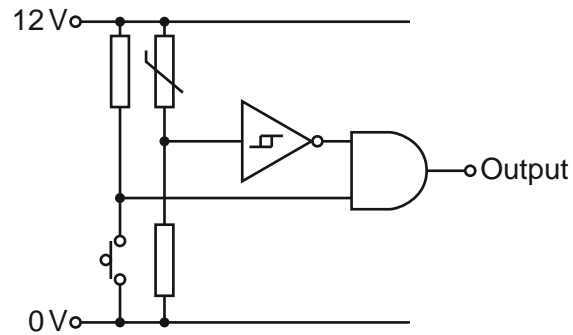


Write either 'Analogue' or 'Digital' in the box next to the signals listed in the table.

Signal	Analogue or digital?
Output of temperature-sensing unit	.....
Output of switch unit	.....
Output of Schmitt inverter	.....
Output of logic gate	.....



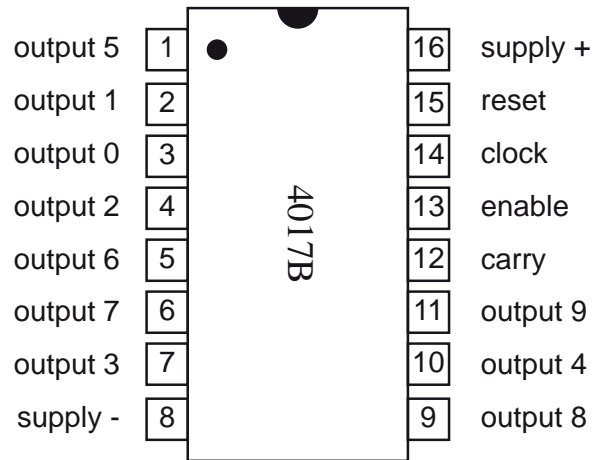5. The pinout for a decade counter is shown below.




- (a) Which statement best describes the function of the decade counter?  
(Tick (✓) the correct answer.)

[1]

- It counts up in tens, not in units.
- It resets automatically on the sixteenth pulse.
- Each output goes high in turn.
- Every tenth count, it outputs a pulse from its clock pin.

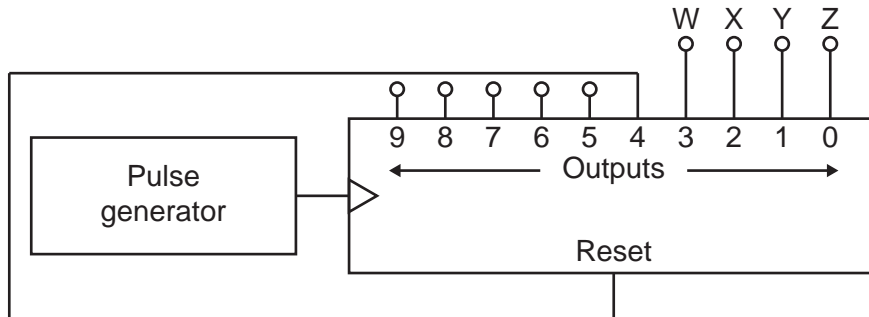- (b) The diagram shows part of a lighting sequence, controlled by a decade counter. Outputs W, X, Y and Z are connected to LEDs. The counter resets when the Reset pin receives a logic 1 signal.




Complete the table by writing **On** or **Off** for each LED to show the sequence.

[2]


Pulse	LEDs			
	Z	Y	X	W
0	On	Off	Off	Off
1				
2				
3				
4				

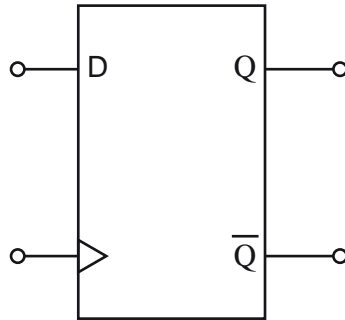6. (a) Which of the following statements best describes the behaviour of a D-type flip-flop? (Tick (✓) the correct answer.) [1]



- The  $\bar{Q}$  pin changes state every time a clock pulse triggers the flip-flop.
- The clock is triggered when the D pin changes state.
- The Q pin copies the logic level on the D pin when the flip-flop is triggered.
- The D pin copies the logic level on the clock pin when the flip-flop is triggered.

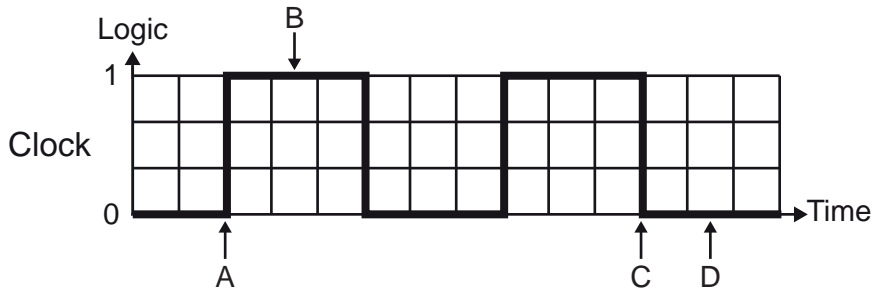- (b) A D-type flip-flop is rising-edge triggered.




On the graph, which arrow identifies a rising-edge of a clock pulse? Circle the correct answer.

- A      B      C      D

[1]

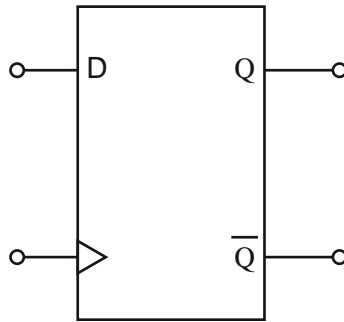
7. A rising-edge triggered D-type flip-flop can be made into a one-bit counter.




(a) Which connection should be made to create a one-bit counter?  
(Tick (✓) the correct answer.) [1]

- Q output to the D input.
- $\bar{Q}$  output to the D input.
- Q output to the clock input.
- $\bar{Q}$  output to the clock input.

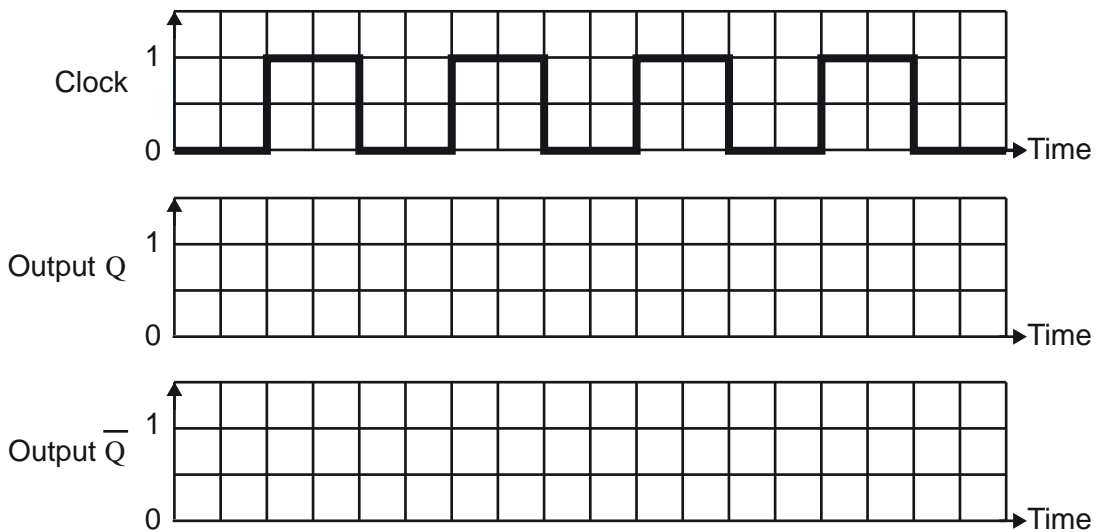(b) Initially, the one-bit counter is reset.  
Use the axes provided to draw the corresponding signals on the Q and  $\bar{Q}$  outputs. [3]



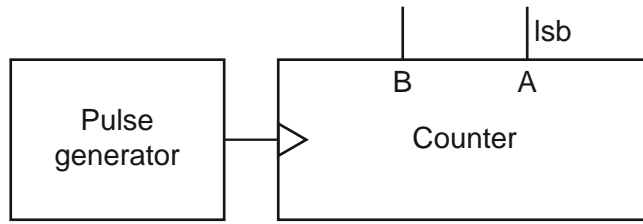
8. The diagram shows a 2-bit up-counter connected to a pulse generator. The counter is **rising-edge triggered** and is initially **reset**.



The top graph shows pulses received from the pulse generator. The middle graph shows the signal at output A, the least-significant bit.

- (a) Complete the bottom graph to show the corresponding signal at output B. (Initially, it is at logic 0.)

[1]

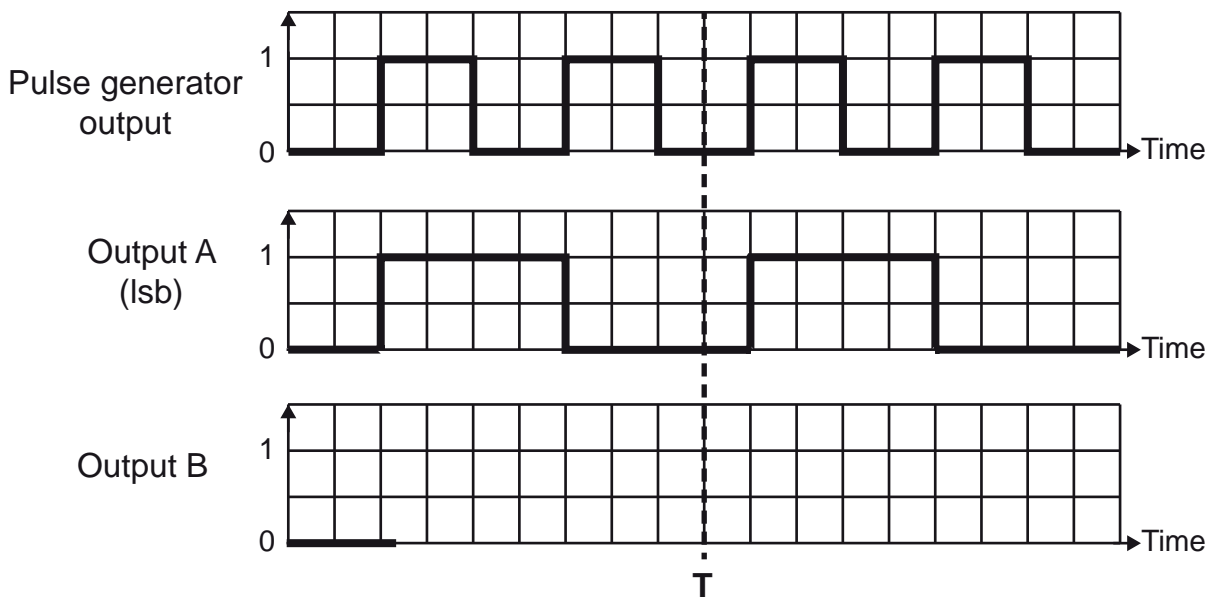

- (b) What binary number does the counter output at time T? Circle the correct answer.

[1]


00    01    10    11

9. A microcontroller is used to operate a lamp in a dark corridor, using two push-switches **P** and **Q** located at the ends of the corridor.

When switch **P** OR switch **Q** is pressed for a moment, the light comes on for ten seconds.

Complete the flowchart by writing the correct letter in the boxes.

[4]

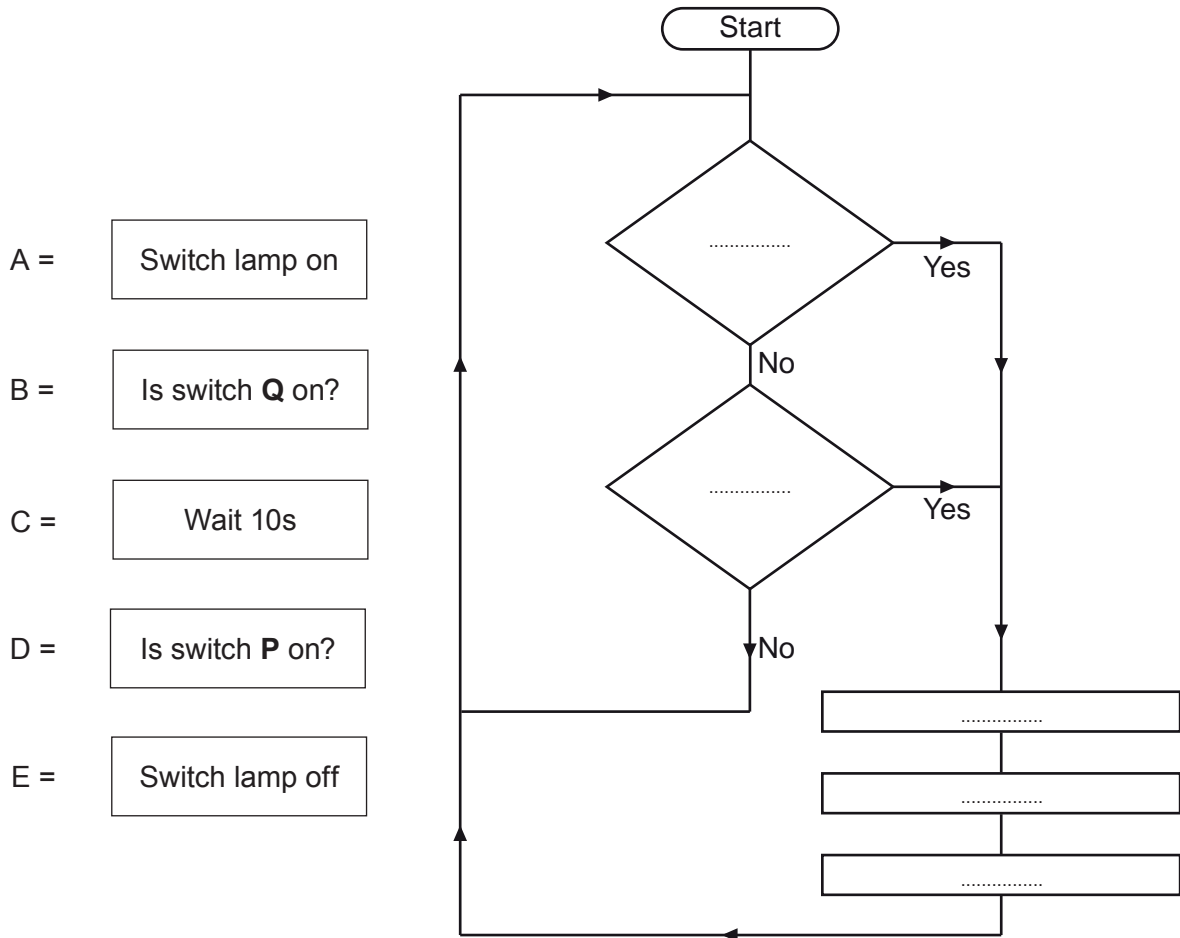

10. Comparators and Schmitt inverters can be used to interface a light-sensing unit to a logic system.


(a) Which statement about the comparator is correct? [1]  
(Tick (✓) the correct answer.)

- It has a single switching threshold fixed at 0.7 V.
- It has a single switching threshold at a voltage which can be varied.
- It has two fixed switching thresholds.
- It has two switching thresholds at voltages which can be varied.

(b) Which statement gives the advantage of a Schmitt inverter over the comparator in this application? [1]  
(Tick (✓) the correct answer.)

- It stops contact bounce in the light sensor.
- It stops rapid output switching when the light level fluctuates slightly.
- It works better in the dark.
- It boosts the current to the logic system.

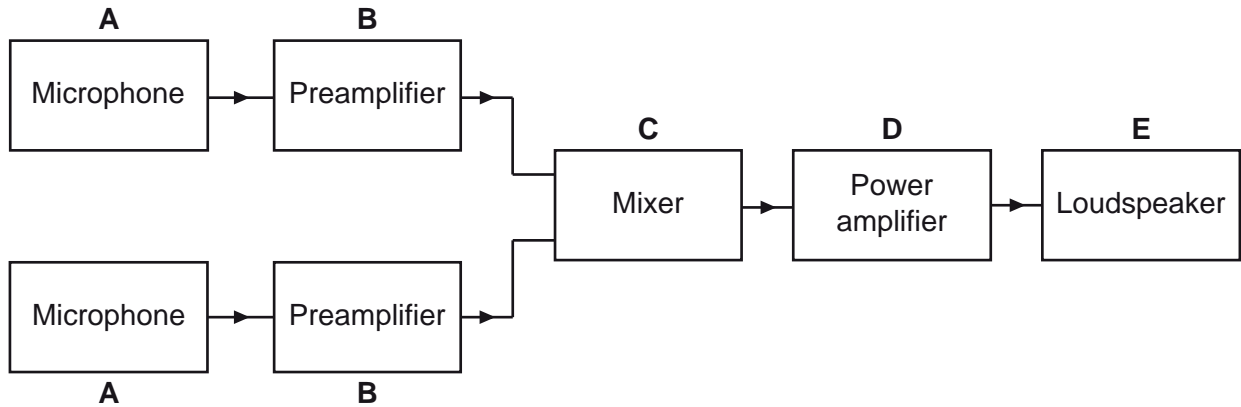11. The block diagram represents a typical public address system. It consists of different sub-systems, labelled **A** to **E**.



(a) Which sub-system:

- (i) converts electrical signals into sound;

[1]

A      B      C      D      E

- (ii) is designed specifically to boost the signal **current**;

[1]

A      B      C      D      E

- (iii) is designed specifically to boost the signal **voltage**?


[1]

A      B      C      D      E



- (b) The mixer, shown in the diagram, combines signals from the two microphones. It is tested by applying the following voltages.

Input A = 2.0V  
 Input B = 1.0V

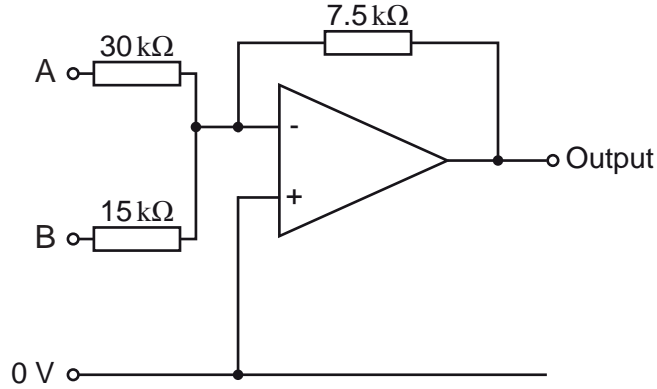

- (i) Which **one** of the following shows the correct equation to calculate the output voltage,  $V_{OUT}$ ?  
 (Tick (✓) the correct answer.) [1]

$V_{OUT} = -15\left(\frac{1}{30} + \frac{2}{7.5}\right)$

$V_{OUT} = -30\left(\frac{1}{15} + \frac{2}{7.5}\right)$

$V_{OUT} = -7.5\left(\frac{2}{30} + \frac{1}{15}\right)$

$V_{OUT} = -7.5\left(\frac{1}{30} + \frac{2}{15}\right)$

- (ii) Calculate the output voltage. [1]

.....

.....

Output voltage = ..... V


12. **A**, **B** and **C** are different voltage amplifiers.

- (a) When the input signal has an amplitude of 4 mV, amplifier **A** produces an output signal with an amplitude of 40 mV.  
What is the voltage gain of amplifier **A**? Circle the correct answer. [1]

10      36      44      160


- (b) The circuit diagram for amplifier **B** is shown below.  
What is its voltage gain? Circle the correct answer. [1]

-13      -12      12      13

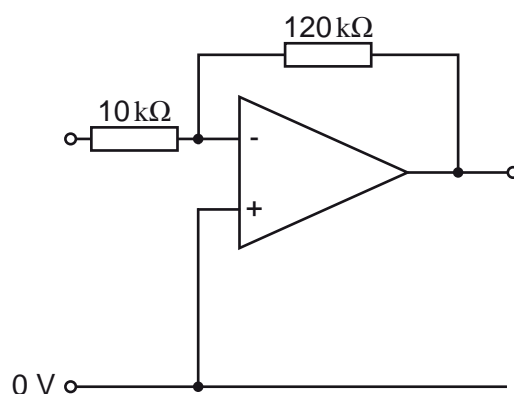


- (c) The top graph shows the signal applied to the input of amplifier **C**.  
The bottom graph shows the corresponding output signal.  
What is the voltage gain of amplifier **C**? Circle the correct answer. [1]

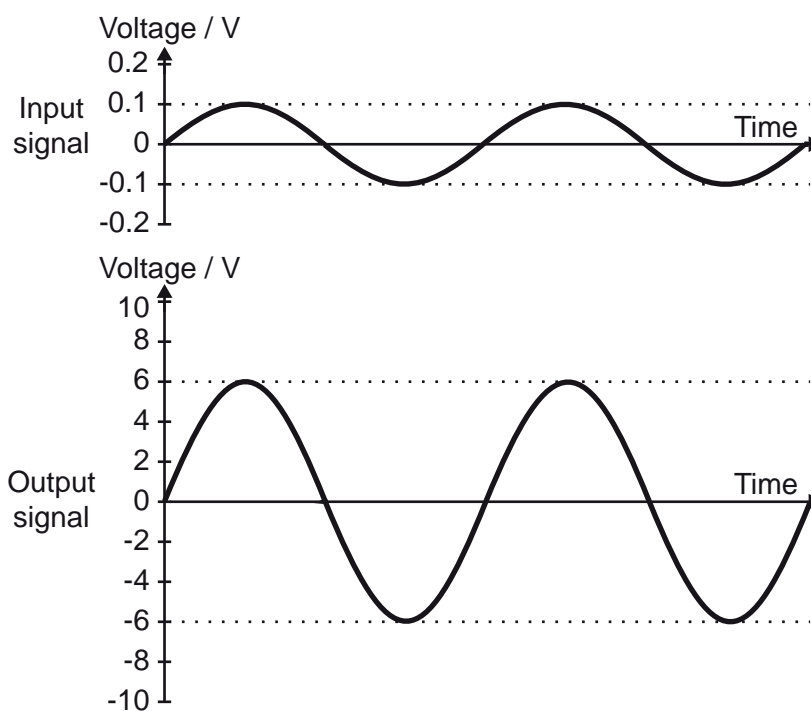6.0      6.1      12.2      60.0      120.0



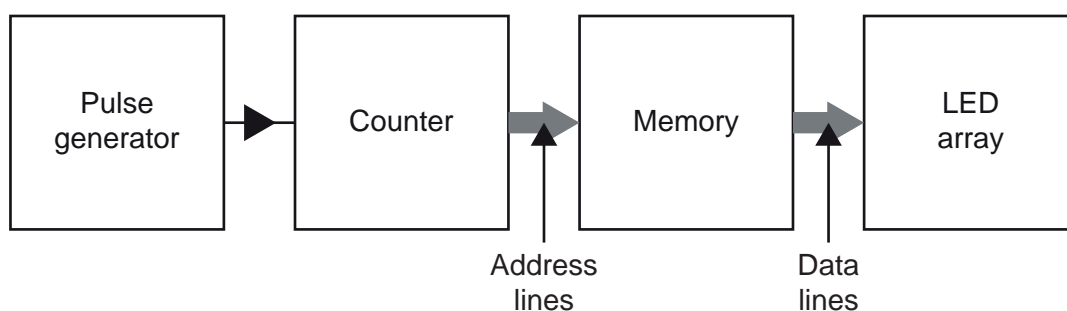13. The block diagram for a sequence controller is shown below.



The contents of the memory are given in the following table:

Address			Data			
A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
0	0	0	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	1	0	0
0	1	1	0	0	1	0
1	0	0	0	0	0	1

(a) What is the minimum number of bits that the counter must have?  
Circle the correct answer.

1      2      3      4      5

[1]

(b) Each output is connected to a single LED.  
How many LEDs are required in total?  
Circle the correct answer.

1      2      3      4      5

[1]

(c) Initially, the counter is reset.  
How many pulses are then needed to produce the output '0100'?  
Circle the correct answer.


1      2      3      4      5

[1]

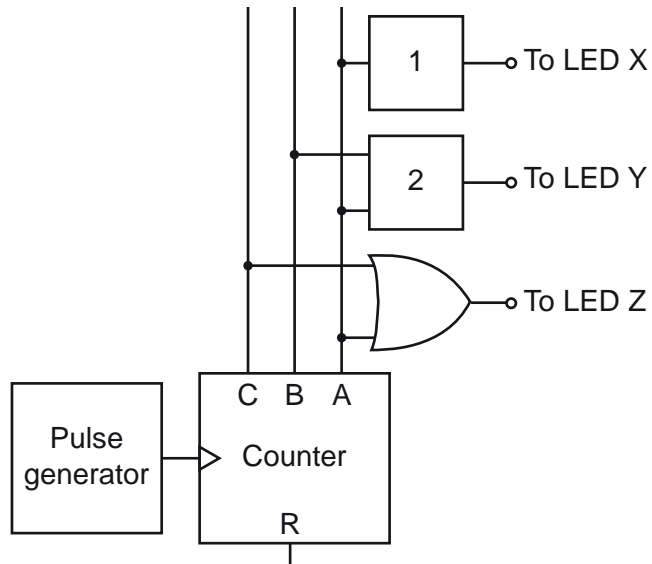14. The diagram shows part of a control system for a LED lighting sequence.

A LED lights when it receives a logic 1 signal.

The behaviour of LEDs X and Y is shown in the table.



Pulses	Counter outputs			LEDs	
	C	B	A	X	Y
0	0	0	0	On	On
1	0	0	1	Off	On
2	0	1	0	On	On
3	0	1	1	Off	Off
4	1	0	0	On	On
5	1	0	1	Off	On
6	1	1	0	On	On
7	1	1	1	Off	Off

(a) Box 1 must contain the ..... logic gate. Insert the correct answer from the list below. [1]

NOT      AND      NAND      OR      NOR


(b) Box 2 must contain the ..... logic gate. Insert the correct answer from the list below. [1]

NOT      AND      NAND      OR      NOR

(c) Which two pulses cause LED Z to switch **off**?  
Pulses ..... and ..... cause LED Z to switch **off**. Insert the correct answers from the list below. [2]

0      1      2      3      4      5      6      7

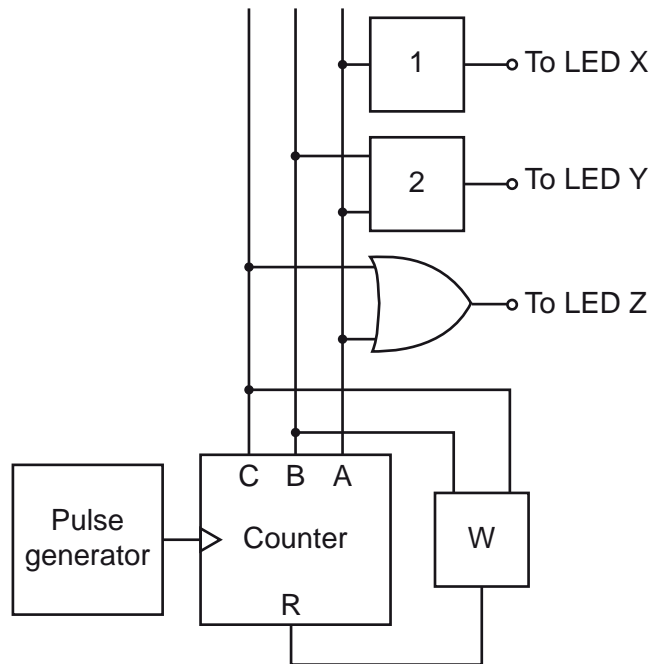(d) The next diagram includes the reset sub-system.



The counter resets when the reset pin **R** receives a logic 1 signal. The logic gate in box **W** makes the counter reset on pulse 6.

Box **W** must contain the ..... logic gate. Insert the correct answer from the list below. [1]

NOT      AND      NAND      OR      NOR

15. A Schmitt Inverter is tested using the input signal shown in the upper graph.

**Schmitt Inverter Information:**



The output:

- changes from logic 1 to logic 0 when a **rising** input voltage reaches 9V;
- changes from logic 0 to logic 1 when a **falling** input voltage reaches 6V.

A signal at 1V represents logic 0 and one at 10V represents logic 1.

Use the axes provided in the lower graph to draw the expected output signal.


[4]

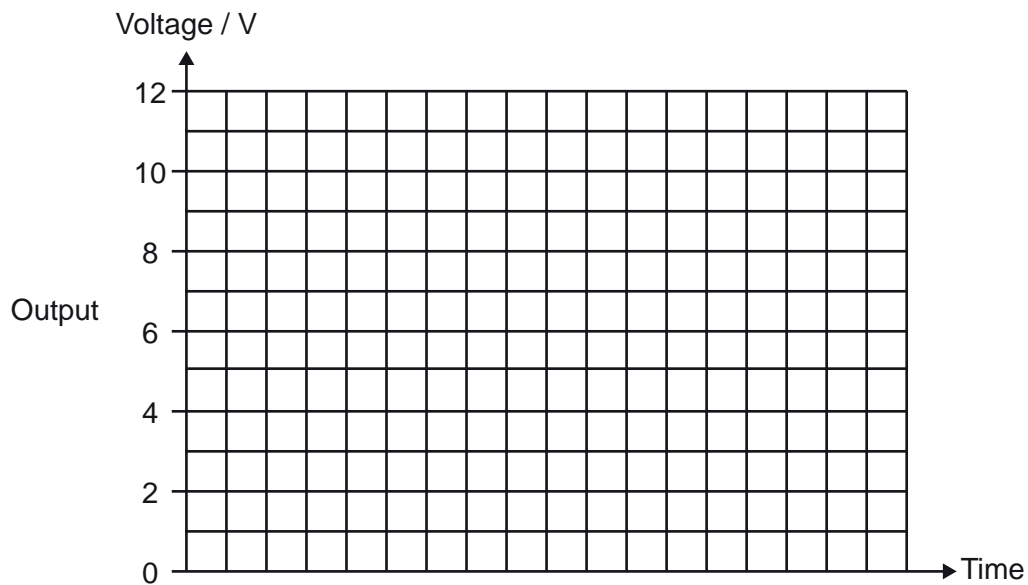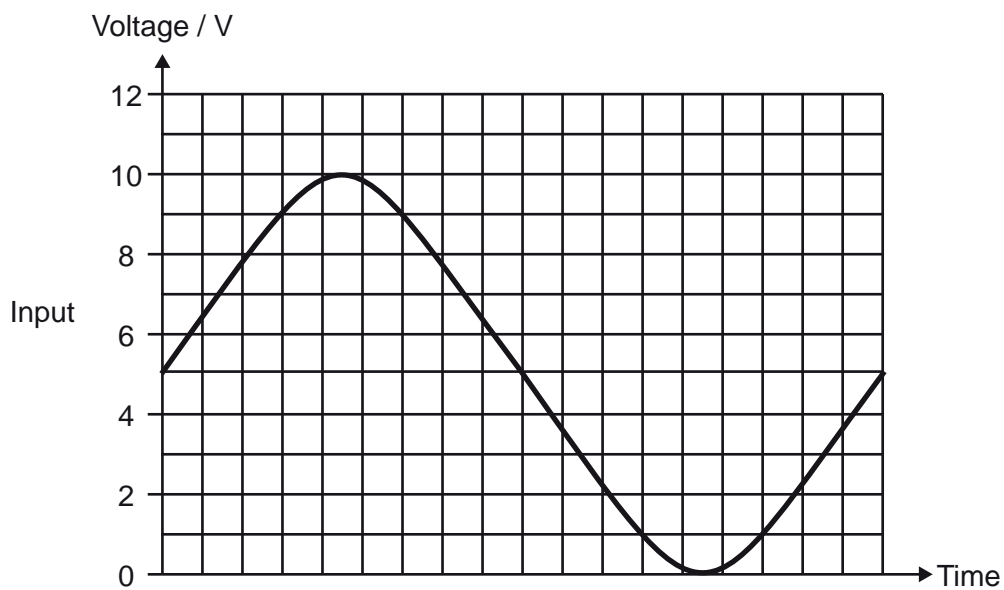

**BLANK PAGE**



16. A **non-inverting** amplifier has a voltage gain of 12.

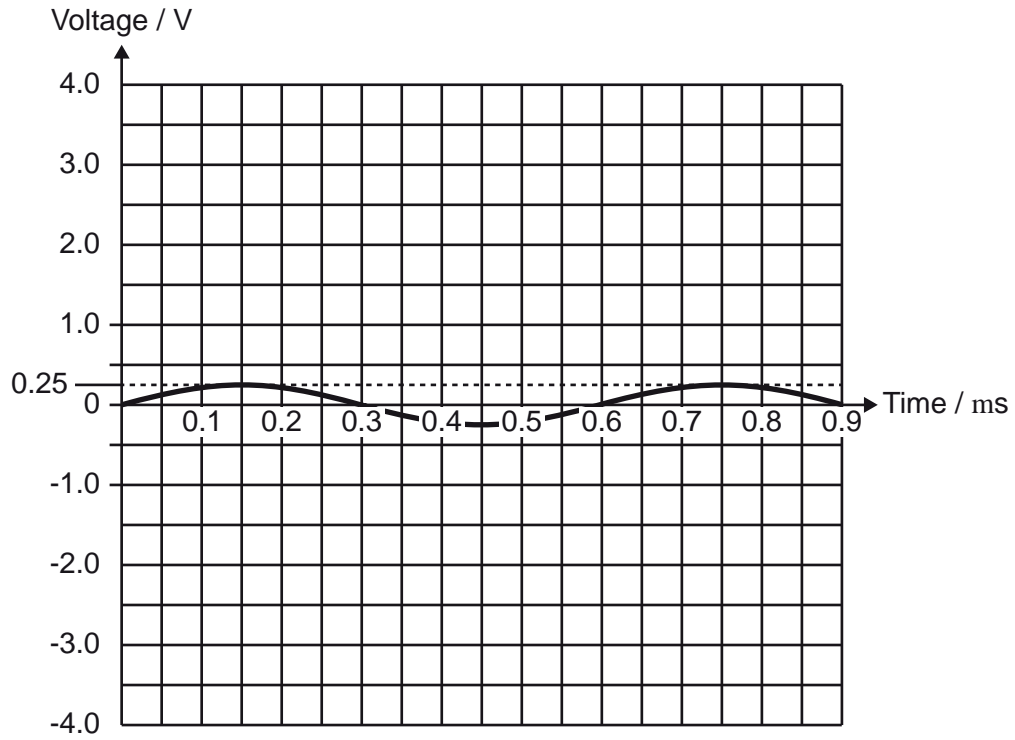- (a) The graph shows the input signal of peak value 0.25 V.  
Draw the wave that shows the corresponding output signal in the graph below. [2]






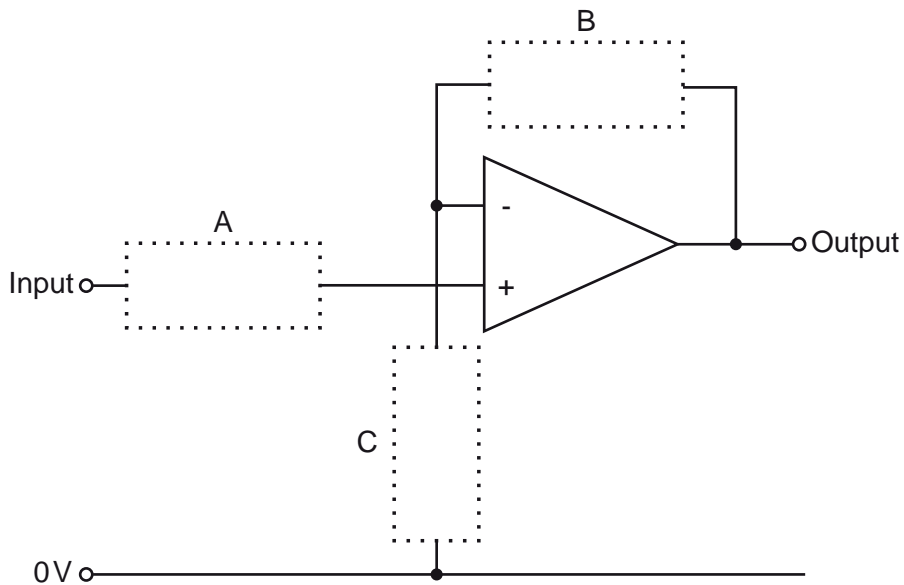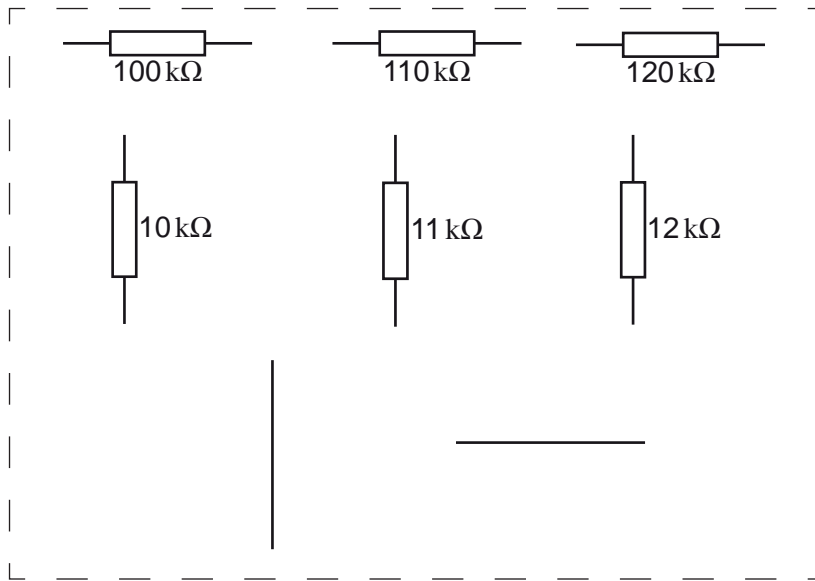(b) Draw the correct components in the circuit diagram for the non-inverting amplifier shown below having a voltage gain of 12. [3]



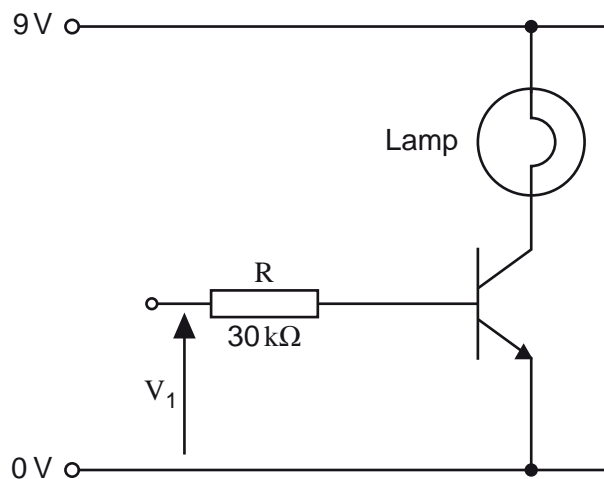17. A transistor switch is used to interface a logic system to a lamp. The transistor has a current gain of 50. The current through R is 0.2 mA.



- (a) What current flows through the lamp if the transistor is not saturated? [1]

Current through the lamp = ..... mA.

- (b) (i) Calculate the voltage across resistor, R. [1]

.....  
 .....

Voltage across R = ..... V.

- (ii) What is the voltage  $V_1$ ? [1]

$V_1$  = ..... V.

**END OF PAPER**

**BLANK PAGE**